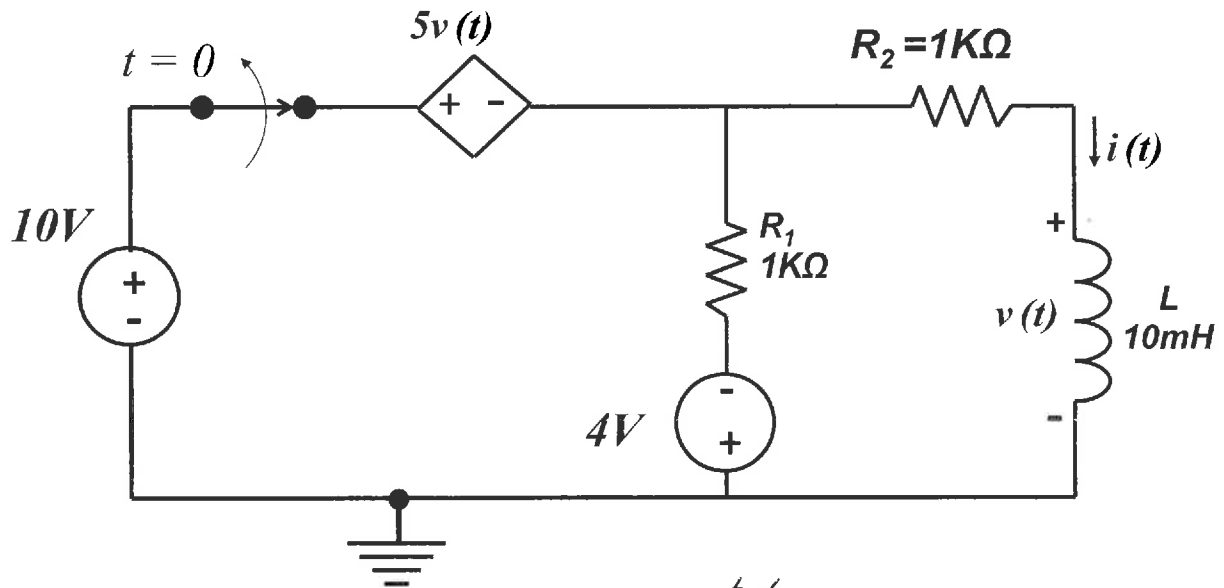


Name :

ID #

Problem # 1 (10 Points)

The switch in the circuit is opened at time $t = 0$ after long being closed. Find $i_L(t)$ at $t = 2\mu\text{sec}$ and $t = 9\mu\text{sec}$.



$$i_L(t > 0) = I_F + (I_i - I_F)e^{-t/\tau}$$

For switch is closed for long time, $v(t) = 0$, $5v(t) = 0$

\therefore 10V appears across $R_2 = 1\text{k}\Omega$

$$I_{L_i}(t=0) = \frac{10\text{V}}{1\text{k}\Omega} = 10\text{mA}$$

After switch is opened, circuit will find new steady-state condition, with: $i_L(t) = -\frac{4\text{V}}{2\text{k}\Omega} = -2\text{mA}$

$$\therefore i_L(t) = -2 + (10 + 2)e^{-t/\tau}, \quad \tau = \frac{L}{R} = \frac{10\text{mH}}{2\text{k}\Omega} = 5\mu\text{sec}$$

$$i_L(t) = -2 + 12e^{-t/5\mu\text{sec}} \text{ mA for } t > 0$$


$$\text{at } t = 2\mu\text{sec}, \quad i_L(t = 2\mu\text{sec}) = -2 + 12e^{-\frac{2}{5}} = 6.04 \text{ mA}$$

$$\text{at } t = 9\mu\text{sec}, \quad i_L(t = 9\mu\text{sec}) = -2 + 12e^{-\frac{9}{5}} = -0.016 \text{ mA}$$

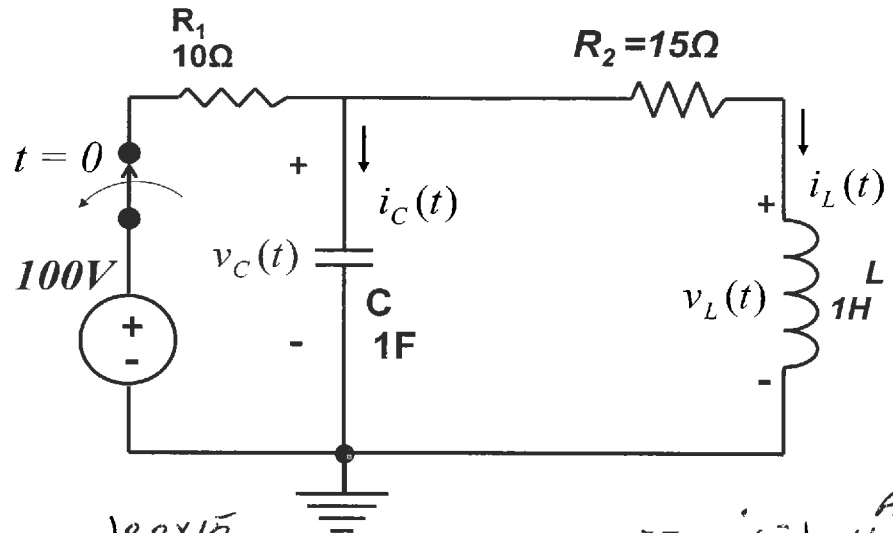Problem # 2 (10 Points)

In this circuit, switch has been closed for a long time and then is opened at $t = 0$, find

$$i_C(t = 0^+), v_C(t = 0^+), v_C(t = \infty), v'_C(t = 0^+), i_L(t = 0^+), i_L(t = \infty), i'_L(t = 0^+).$$



$$\text{At } t = 0^- \quad v_C(0^-) = \frac{100 \times 15}{10 + 15} = 4 \text{ A} \times 15 \Omega = 60 \text{ V}, \quad i'_L(0^-) = 4 \text{ A}$$

$$\text{For } t = 0^+ \quad v_C(0^+) = 60 \text{ V}, \quad i'_L(0^+) = 4 \text{ A}, \quad v_C(\infty) = 0, \quad i_L(\infty) = 0$$

$$i_C(0^+) = -i'_L(0^+) = -4 \text{ A}$$

$$i_C(0^+) = C \left. \frac{dv_C}{dt} \right|_{t=0^+}, \quad \left. \frac{dv_C}{dt} \right|_{t=0^+} = \frac{i_C(0^+)}{C} = \frac{-4 \text{ A}}{1 \text{ F}} = -4 \text{ V/sec}$$

$$\text{Also } v_L(0^+) - v_C(0^+) + i_L(0^+) R_2 = 0$$

$$v_L(0^+) - 60 \text{ V} + 4 \text{ A} \cdot 15 = 0, \quad v_L(0^+) = 0$$

$$v_L(0^+) = L \left. \frac{di_L}{dt} \right|_{t=0^+} = 0, \quad \left. \frac{di_L}{dt} \right|_{t=0^+} = 0$$