

Laboratory Five — Transient Response

Rishabh Shah
4655 4192

Partner: Matthew Remillard

November 17, 2017

Pre-Lab

I

a

$$\tau = RC = 1k\Omega \cdot 0.1 \times 10^{-6} = 1 \times 10^{-4}s$$

b

$$v_0 = 1V$$

$$v_R(t) = 1 - v_c(t)$$

$$v_c(t) = v_0(1 - e^{-\frac{t}{\tau}}) = 1 - e^{-\frac{0.001}{0.0001}} = 1V$$

Element	$v_{PPK}(V)$
$v_{C,PPK}$	1
$v_{R,PPK}$	1

Table 1: Data for Pre-Lab 1b

c

We can assume the circuit reaches steady state because there are more than five time constants in that time period.

d

The capacitor must charge, so v_c increases with time. As this occurs, the voltage across the resistor must drop, as $v_0 = v_R + v_c$.

II

a

v_c charges when $v_0 = 1V$ and discharges when $v_0 = 0V$. Since $v_0 = v_R + v_c$, v_R is 1 when v_c is 0 and v_R is 0 when v_c is 1.

b

$$v_c(t) = 1 - e^{-\frac{0.001}{0.0001}} = 1V$$

$$v_0 = v_R + v_c$$

Element	$v_{PPK}(V)$
$v_{C,PPK}$	1
$v_{R,PPK}$	2

Table 2: Data for Pre-Lab 2b

III

a

$$v_c(t) = 1 - e^{-\frac{2.5 \times 10^{-4}}{0.0001}} = 0.918V$$

The time constant has increased by a factor of 2.5, which means the circuit has not reached steady state.

b

$$f_{max} = 1000Hz$$

The circuit has not reached steady state because five time constants have not passed.

IV

a

$$\omega_0 = 422.577$$

b

Resistance ($k\Omega$)	Damping Factor α (s^{-1})	Decay Time $5/\alpha$ (s)	ω_d (rad/s)	f_d (kHz)
0.5	2500	$\frac{1}{500}$	422569	2.37×10^{-6}
1	50000	$\frac{1}{10000}$	419608	2.38×10^{-6}
8.45	422500	$\frac{1}{84500}$	8066	1.24×10^{-4}
25	1250000	$\frac{1}{250000}$	N/A	N/A

Table 3: Data for Pre-Lab 4b

c

$$R = \frac{2L}{\sqrt{LC}} = 8451\Omega$$

Lab Data

Series RC

Element	Measured Value
R_1	985.92Ω
C	$101.5nF$

Table 4: Measured values for circuit elements

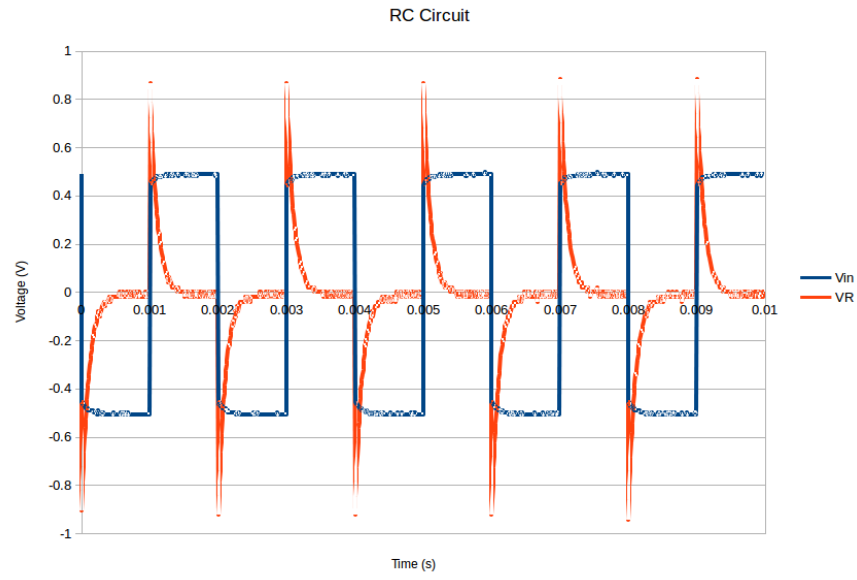


Figure 1: Plot of RC circuit measuring V_R

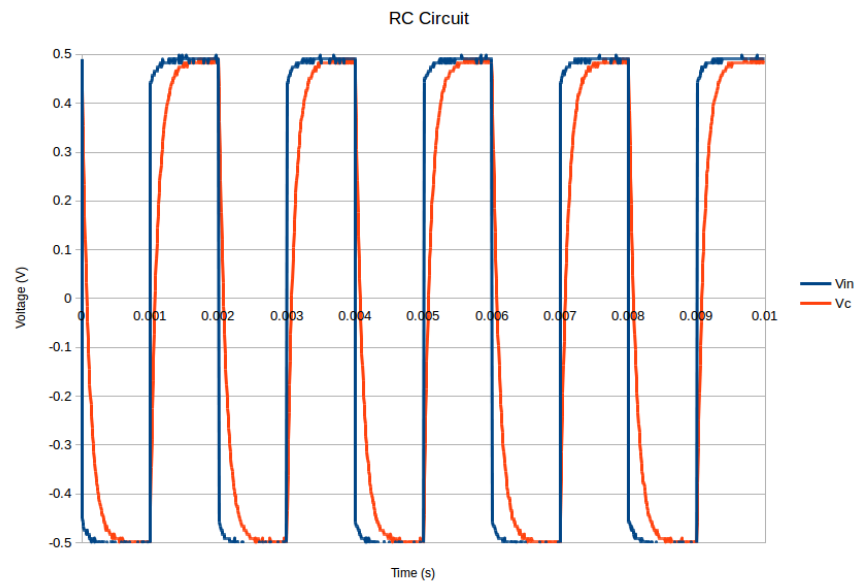


Figure 2: Plot of RC circuit measuring V_c

Nonzero DC Offset

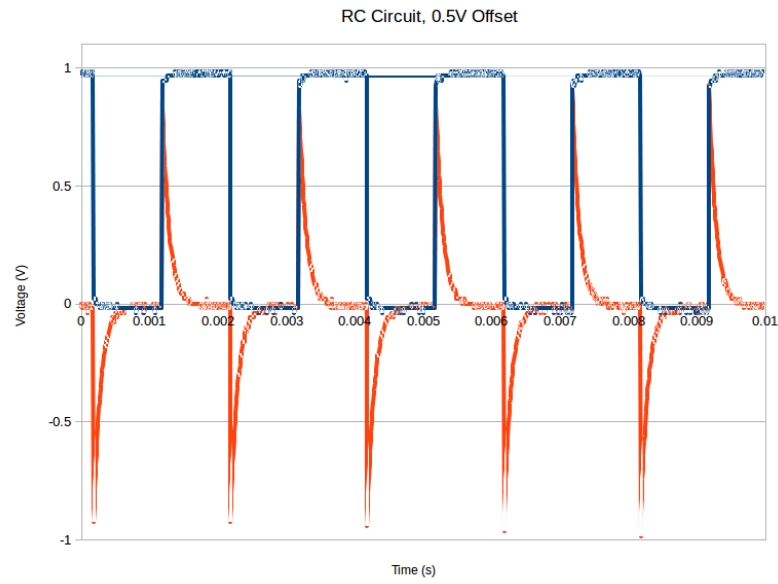


Figure 3: Plot of RC circuit, 0.5V offset measuring V_R

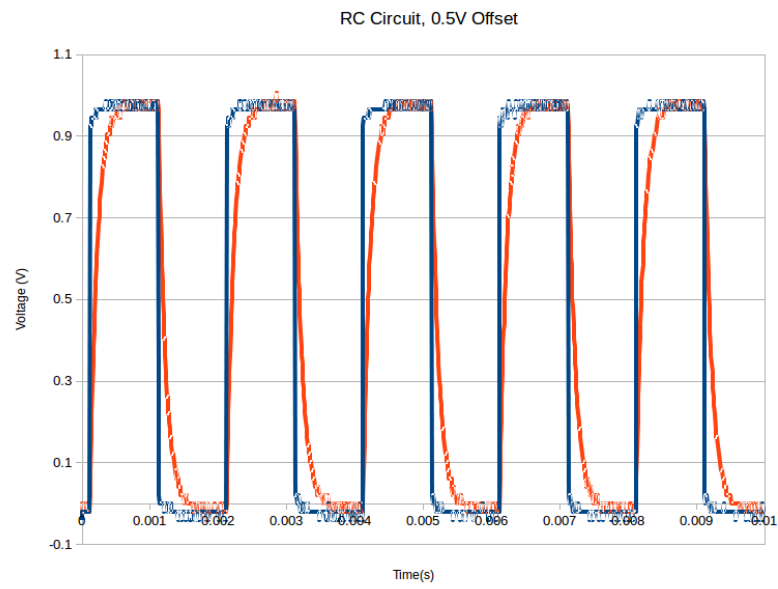


Figure 4: Plot of RC circuit, 0.5V offset measuring V_c

Frequency Response

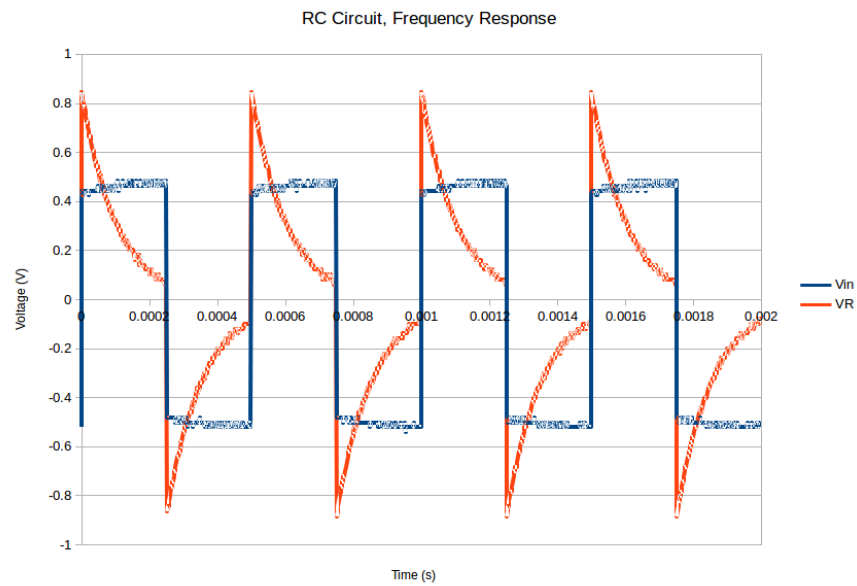


Figure 5: Plot of RC circuit, 2kHz measuring V_R

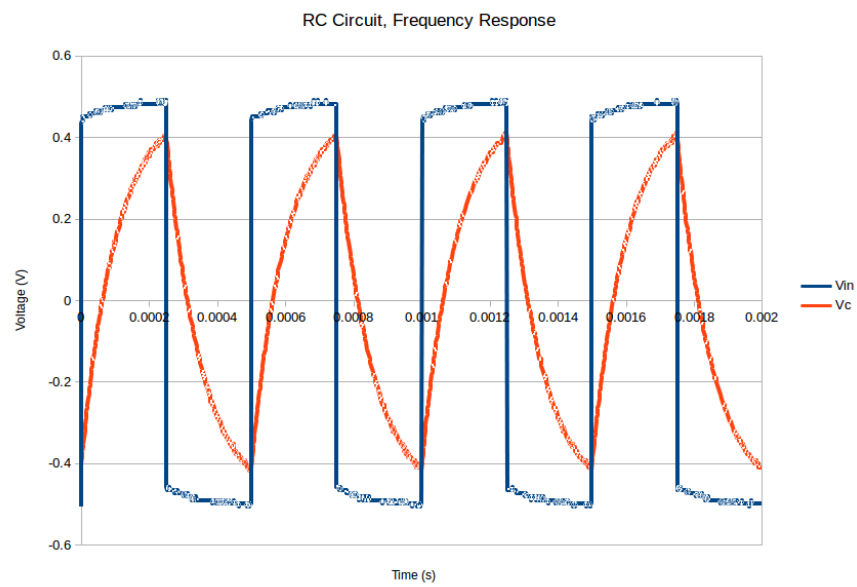


Figure 6: Plot of RC circuit, 2kHz measuring V_C

First Order OP Amp Circuit

Element	Measured Value
R_1	985.92 Ω
R_2	981.50 Ω
R_3	987.64 Ω
C	101.5nF

Table 5: Measured values for circuit elements

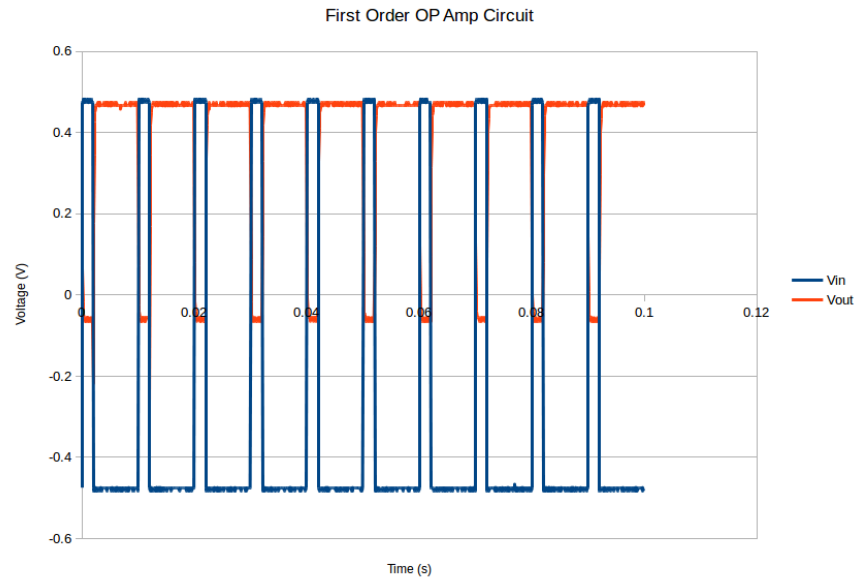


Figure 7: Plot of first order op amp circuit, 20% duty cycle, 100Hz

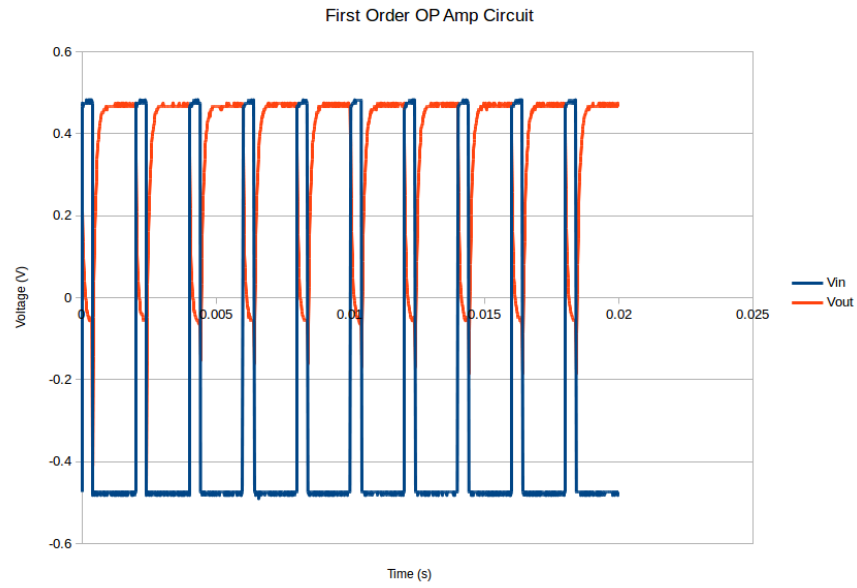


Figure 8: Plot of first order op amp circuit, 20% duty cycle, 500Hz

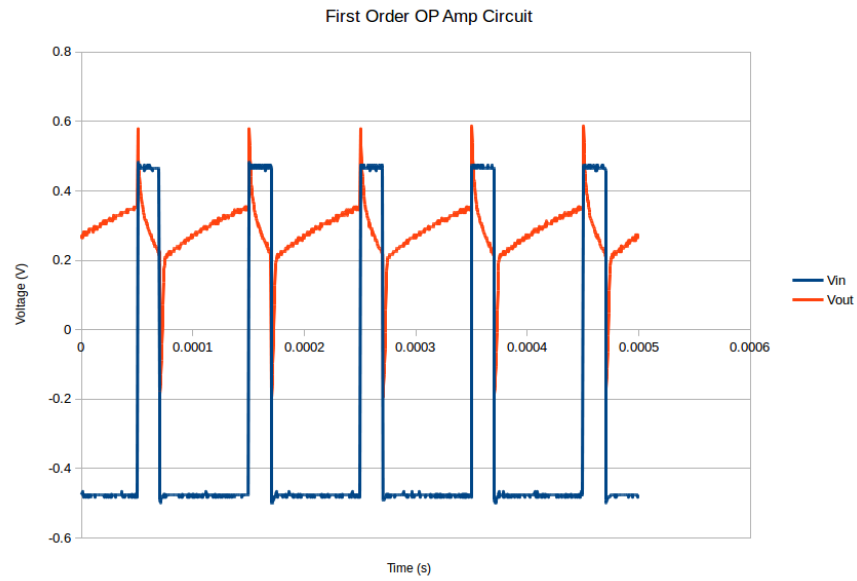


Figure 9: Plot of first order op amp circuit, 20% duty cycle, 10kHz

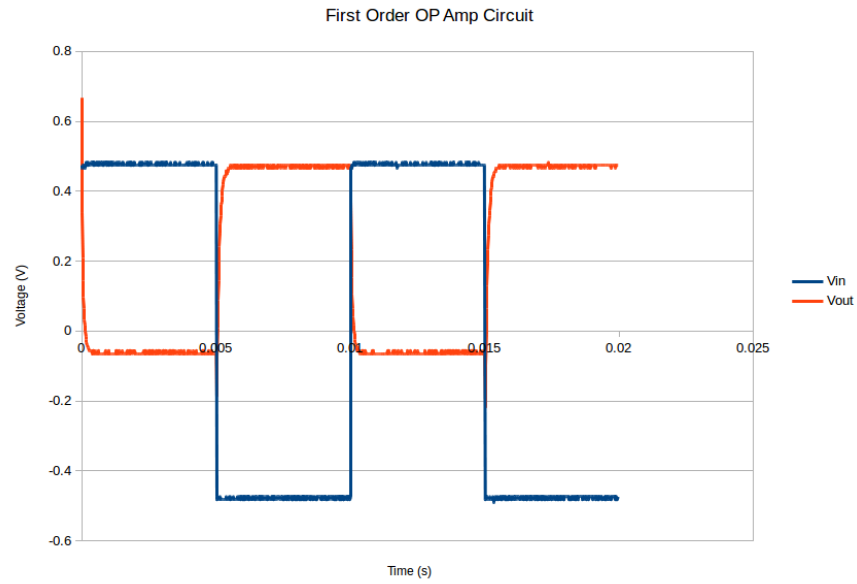


Figure 10: Plot of first order op amp circuit, 50% duty cycle, 100Hz

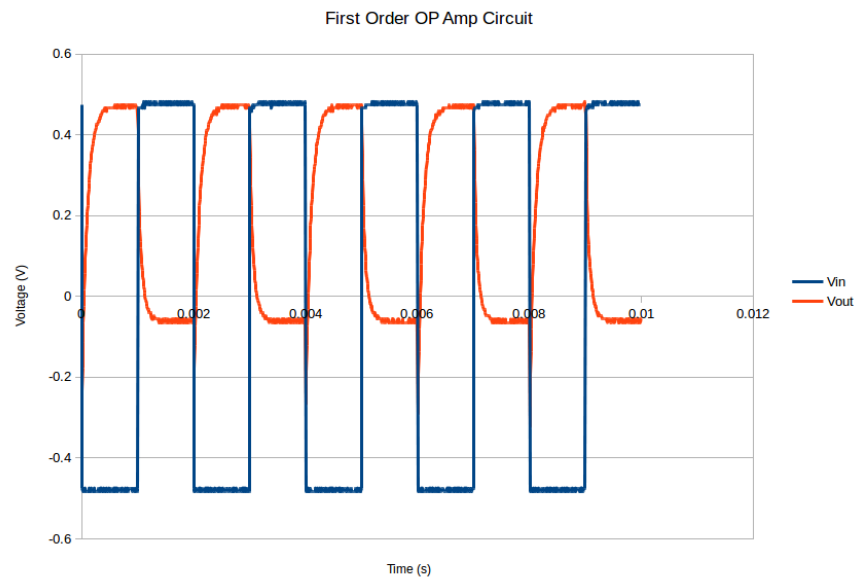


Figure 11: Plot of first order op amp circuit, 50% duty cycle, 500Hz

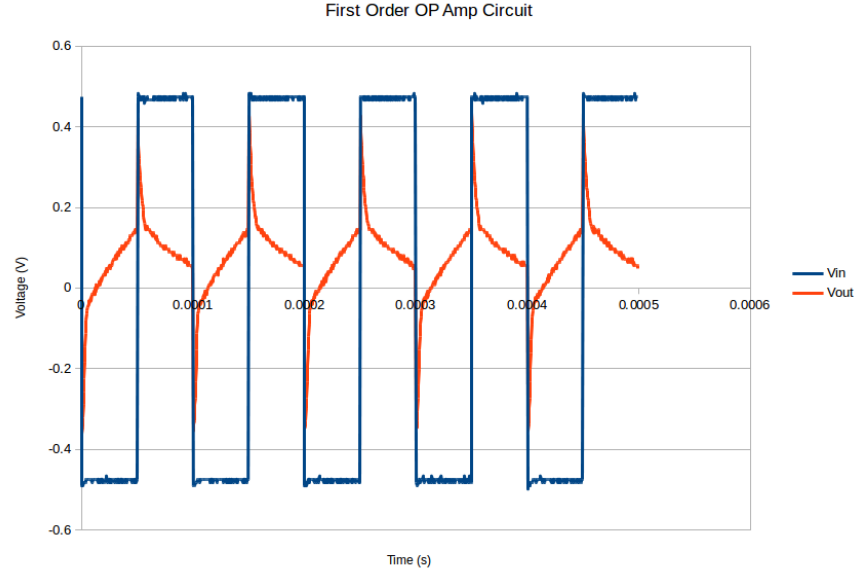


Figure 12: Plot of first order op amp circuit, 50% duty cycle, 10kHz

Series RLC Circuit — Underdamped Response, $R = 1k\Omega$

Element	Measured Value
Combined Resistance	990.57Ω
C	$575pF$
T_1	$17\mu s$
L	$10.30mH$
L_R	23.94Ω

Table 6: Measured values for circuit elements

Parameter	Calculated Value
$f_{d,1}$	$58823.5294Hz$

Table 7: Calculated $f_{d,1}$

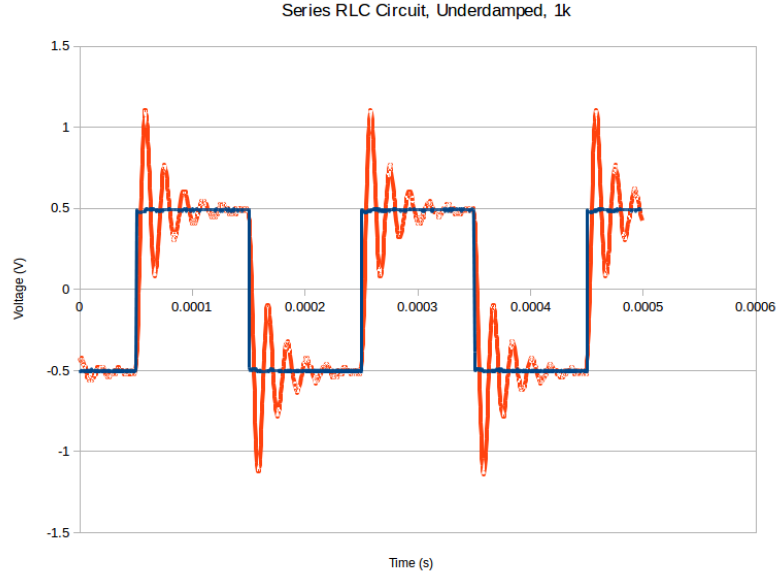


Figure 13: Plot of Series RLC Circuit — Underdamped Response, $R = 1k\Omega$

Series RLC Circuit — Underdamped Response, Minimum Response

Element	Measured Value
Combined Resistance	1.186Ω
C	$575pF$
T_1	$17\mu s$
L	$10.30mH$
L_R	23.94Ω

Table 8: Measured values for circuit elements

Parameter	Calculated Value
$f_{d,1}$	$58823.5294Hz$

Table 9: Calculated $f_{d,1}$

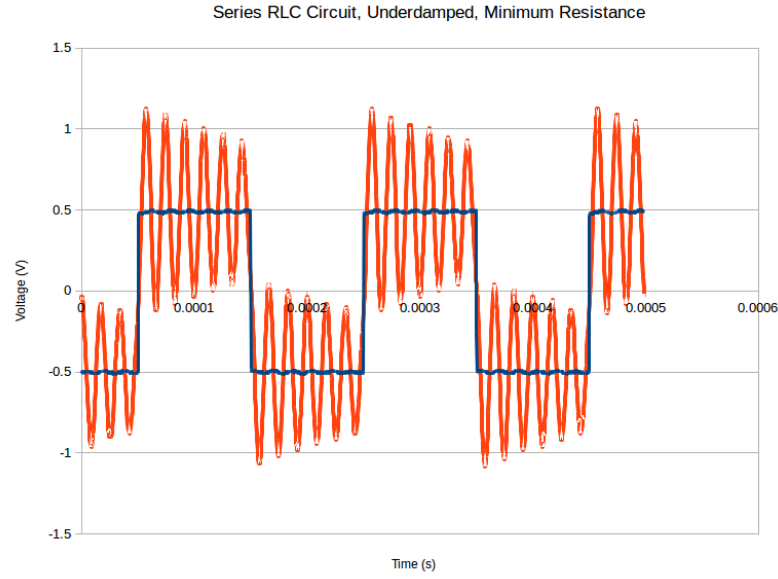


Figure 14: Plot of Series RLC Circuit — Underdamped Response, Minimum Response

Series RLC Circuit — Critically Damped Response

Element	Measured Value
Combined Resistance	$4.6208k\Omega$
C	$575pF$
L	$10.30mH$
L_R	23.94Ω

Table 10: Measured values for circuit elements

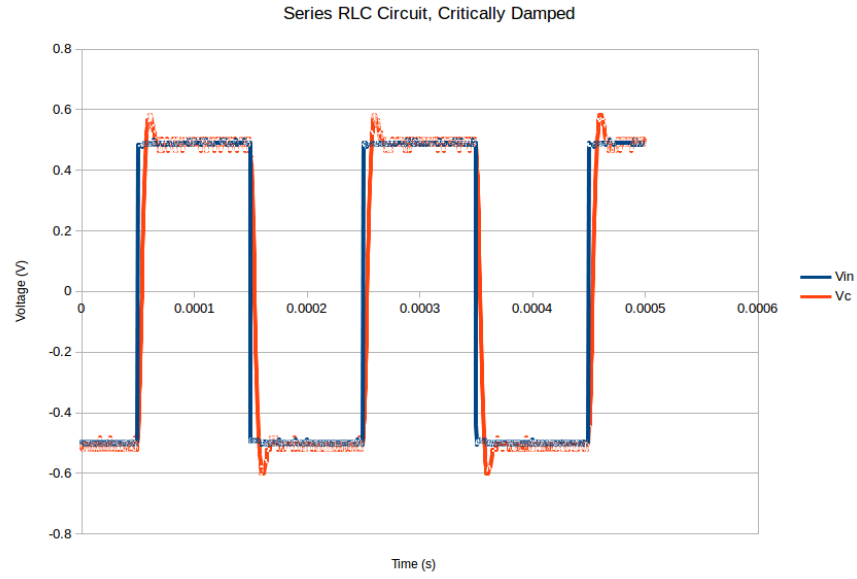


Figure 15: Plot of Series RLC Circuit — Critically Damped Response

Series RLC Circuit — Overdamped Response

Element	Measured Value
Combined Resistance	$0.12726M\Omega$
C	$575pF$
L	$10.30mH$
L_R	23.94Ω

Table 11: Measured values for circuit elements

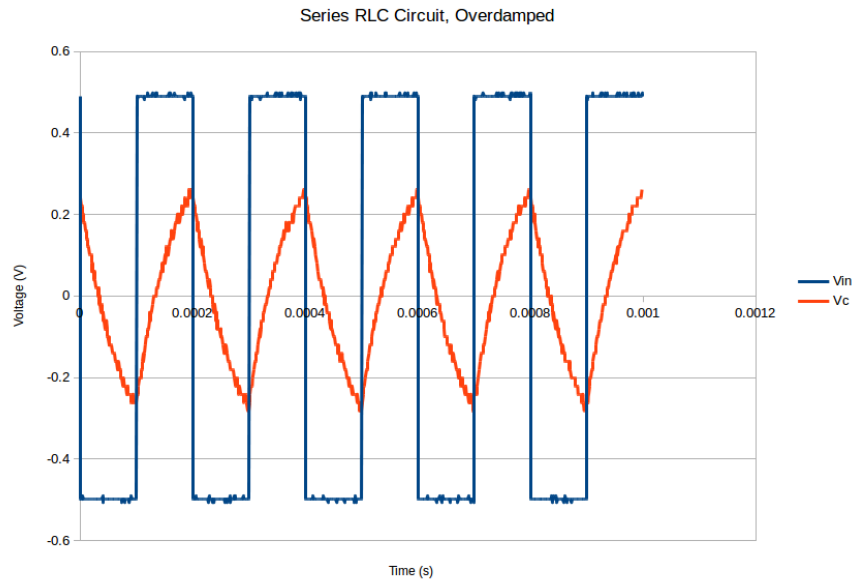


Figure 16: Plot of Series RLC Circuit — Overdamped Response

Post-Lab

Series RC Circuit

Zero DC Offset

$$V_{C,PPK,Calculated} = 0.99995V$$

$$V_{C,PPK,Measured} = 0.99698V$$

$$PercentageError = \frac{|measured - calculated|}{calculated} = \frac{|0.99698 - 0.99995|}{0.99995} = 0.297\%$$

These values are very close.

Nonzero DC Offset

$$V_{C,PPK,Measured,ZeroOffset} = 0.99698V$$

$$V_{C,PPK,Measured,NonZeroOffset} = 1.04523V$$

$$V_{C,PPK,Measured,ZeroOffset} = 1.82915V$$

$$V_{R,PPK,Measured,NonZeroOffset} = 1.90955V$$

The waveforms shapes are the same, except the values are shifted by 0.5V.

Frequency Response

$$V_{C,PPK,Calculated} = 0.91777$$

$$V_{C,PPK,Measured} = 0.82814$$

$$PercentageError = \frac{|measured - calculated|}{calculated} = \frac{|0.82814 - 0.91777|}{0.91777} = 9.766\%$$

These values are similar, but differ due to experimental errors.

First Order Op Amp Circuit

Dont know

Series RLC Circuit

$$R = 1k\Omega$$

$$f_{\text{calculated,ideal}} = 50000Hz$$

$$f_{\text{calculated,real}} = 49705.8252Hz$$

$$f_{\text{measured}} = 58823.5294Hz$$

$$PercentageError_{\text{ideal}} = \frac{|measured-calculated|}{calculated} = \frac{|58823.5294-50000|}{50000} = 17.65\%$$

$$PercentageError_{\text{real}} = \frac{|measured-calculated|}{calculated} = \frac{|58823.5294-49705.8252|}{49705.8252} = 18.34\%$$

$$T_{\text{calculated,ideal}} = 20\mu s$$

$$T_{\text{calculated,real}} = 20.1184\mu s$$

$$T_{\text{measured}} = 17\mu s$$

$$PercentageError_{\text{ideal}} = \frac{|measured-calculated|}{calculated} = \frac{|17-20|}{20} = 15\%$$

$$PercentageError_{\text{real}} = \frac{|measured-calculated|}{calculated} = \frac{|17-20.1184|}{20.1184} = 15.50\%$$

The difference between ω_d and ω_0 is dont know

Critically Damped Response

Dont know

Maximally Damped Response

The circuit does reach a new DC steady state during each half period of the square wave.