

## HW 8

\* 8.5

\* 8.16

\* 8.24

\* 8.29 (a)

\* 8.33

\* 8.49

\* 8.55

8.5

(a)

∴ Voltage across a capacitor and current through an inductor don't change instantaneously

$$V_c(0^-) = 0 = V_c(0^+)$$

$$i_L(0^-) = 0 = i_L(0^+)$$

$$\begin{aligned} \therefore \text{Voltage across } 4\Omega \text{ resistor } (V_R) &= 4i = V_c(0^+) \\ &= 0V \end{aligned}$$

$$\therefore i(0^+) = 0A$$

Also, ∴ current through the inductor

$$i_L(0^+) = 0A.$$

$$\therefore V = 6i_L(0^+) = 0V.$$

(b)

$$\frac{di_L(0^+)}{dt} = \frac{1}{R} \frac{dV_R(0^+)}{dt} = \frac{1}{4} \frac{dV_c(0^+)}{dt}$$

$$= \frac{1}{4} \frac{i_c(0^+)}{C}$$

$$= \frac{1}{4} \frac{4}{(1/4)} = 4 A/s$$

$$\frac{dV(0^+)}{dt} = 6 \frac{di_L(t)}{dt} = 6 \frac{V_L(0^+)}{L}$$


$$= 0 V/s.$$

(c) At steady state, the capacitor is an open ckt and inductor is a short ckt.

$$i(\infty) = \frac{6}{10} \times 4 = 2.4 \text{ A}$$

$$v(\infty) = \frac{4}{10} \times 4 \times 6 = 9.6 \text{ V}$$

8.16

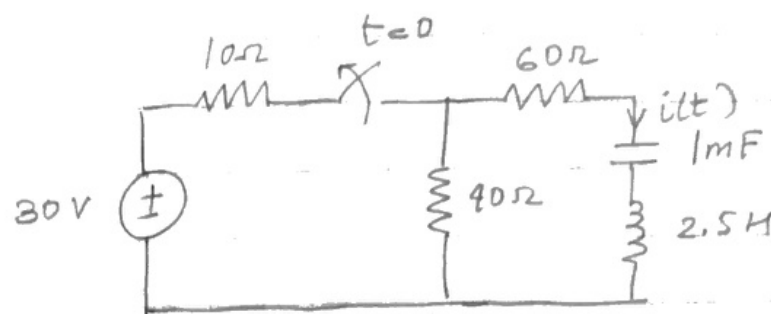

At  $t=0$ , inductor is a short ckt, while the capacitor is an open ckt.

$$\therefore i(0^-) = i(0^+) = 0A \quad - (1)$$

$$\text{and } V_c(0^-) = V_c(0^+) = \frac{40}{50} \times 30 = 24V \quad - (2)$$

$$\text{Now, } \alpha = \frac{R}{2L} = \frac{100}{2 \times (2.5)} = 20$$

$$\omega_d = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{10^{-4} \times 25}} = \frac{1}{0.05} = 20$$

$\therefore \alpha = \omega_d \Rightarrow$  critically damped.

$$\therefore i(t) = (A + Bt) e^{-20t} \quad (\text{for a critically damped system}) \quad - (3)$$

$$i(0) = A \quad (\text{from (3)})$$

$$= 0 \quad (\text{from (1)})$$

- (4)

$$\therefore \text{From (3) \& (4)} \quad i(t) = Bt e^{-20t} \quad - (5)$$

$$\Rightarrow \frac{d}{dt} i(t) = B e^{-20t} - 20Bt e^{-20t}$$

$$\Rightarrow \frac{d}{dt} i(0) = B \quad - (6)$$

Also,

$$\frac{di(0)}{dt} = \frac{di(0)}{dt} = \frac{-1}{L} [100i(0) + v_c(0)]$$


$$= \frac{-1}{2.5} [0 + 24] \quad [\text{From (2)}]$$

$$= -9.6 \text{ V} \quad - (7)$$

From (5) & (7):

$$i(t) = -9.6 t e^{-20t} \text{ A}$$

8.24

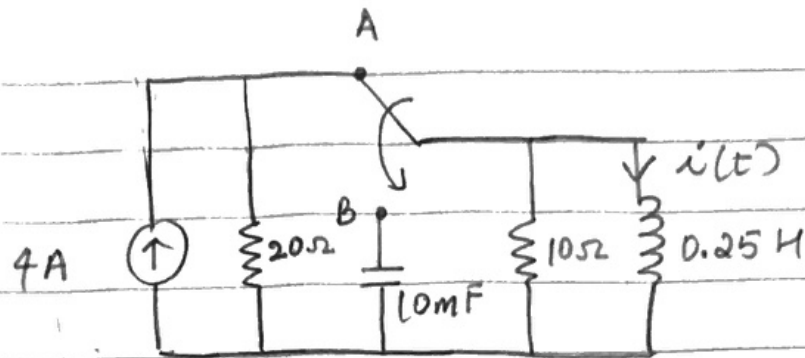

When switch is at A, the inductor is shorted,

$$\therefore i(0^-) = 4A \text{ and } v_L(0^-) = 0V - (1)$$

When switch is at B, there is a parallel RLC ckt:

$$\alpha = \frac{1}{2RC} = \frac{1}{10 \times 10^{-3} \times 10 \times 2} = 5$$

$$\omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{10^{-2} \times 0.25}} = 20$$

$\therefore \alpha < \omega_0$ , for an underdamped system:

$$s_{1,2} = -5 \pm j 19.37$$

$$\therefore i(t) = e^{-5t} (A_1 \cos 19.37t + A_2 \sin 19.37t) - (2)$$

Using initial values,

$$i(0) = A_1 \quad (\text{From (2)})$$

$$= 4 \quad (\text{From (1)})$$

$$\Rightarrow A_1 = 4. - (3)$$

Also,

$$V = L \frac{d i_L(t)}{dt}$$

$$\Rightarrow \frac{d i_L(t)}{dt} = 0 \quad (\text{From (1)}) - (4)$$

$$\text{Now, } \frac{d i}{dt} = -5e^{-5t} (A_1 \cos 19.37t + A_2 \sin 19.37t) + e^{-5t} (-A_1(19.37) \sin 19.37t + A_2(19.37) \cos 19.37t)$$

$$\therefore \frac{d i(t)}{dt} = -5(A_1) + (-19.37 A_2)$$

$$= 0 \quad (\text{From (4)})$$

$$\therefore A_2 = \frac{20}{19.37} = 1.03 - (5)$$

$\therefore$  From (2), (3) & (5) :

$$i(t) = e^{-5t} [4 \cos(19.37t) + 1.03 \sin(19.37t)]$$

8.29(a)  $\frac{d^2 v}{dt^2} + 4v = 12$

characteristic eq<sup>n</sup>:  $s^2 + 4s = 0$

$\therefore \alpha = 0$

$\omega_0 = 2$

$\therefore s_{1,2} = \pm 2j$

$\Rightarrow v_{nt}(t) = A \cos 2t + B \sin 2t$

Under steady state cond<sup>n</sup>:

$4 V_{ss}(t) = 12$

$\therefore v_{ss}(t) = 3 + A \cos 2t + B \sin 2t$

$\therefore v(t) = 3 + A + B e^{-j2t}$

Now using initial cond<sup>n</sup>:

(1)  $v(0) = 3 + A = 0$   
 $\Rightarrow A = -3$

(2)  $\frac{dv(0)}{dt} = \frac{-2A \sin(2 \times 0) + 2B \cos(2 \times 0)}{2} = 2$


$\Rightarrow B = 1$

$\therefore$  complete eq<sup>n</sup>:  $3 - 3 \cos 2t + \sin 2t$





8.33

For  $t < 0$  : equivalent ckt :

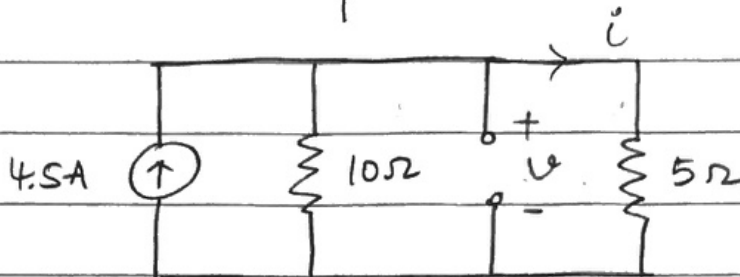

$$\therefore \left. \begin{aligned} v(0) &= (10 \parallel 5) \times 4.5 = 15V \\ i(0) &= \frac{2}{3} \times 4.5 = 3A \end{aligned} \right\} \text{--- ①}$$

For  $t > 0$  : equivalent ckt :

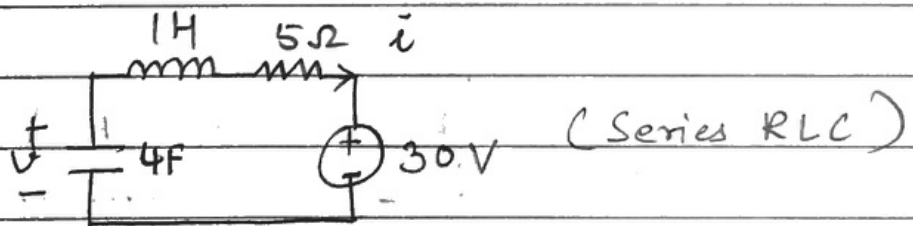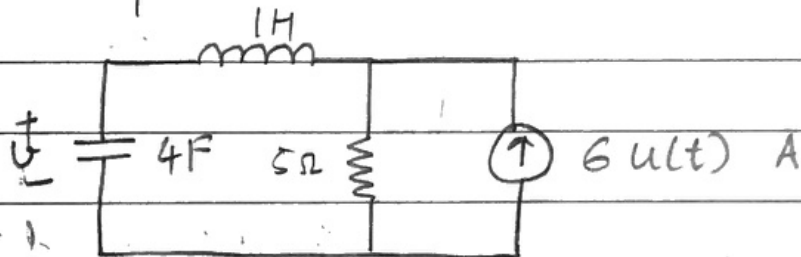

$$\alpha = \frac{R}{2L} = \frac{5}{2} = 2.5$$

$$\omega_0 = \frac{1}{\sqrt{LC}} = 0.5$$

$\therefore \alpha > \omega_0 \Rightarrow$  overdamped response.

$$\begin{aligned}
 s_{1,2} &= -2.5 \pm \sqrt{2.5^2 - 0.5^2} \\
 &= -2.5 \pm 2.44 \\
 &= -4.95, -0.05
 \end{aligned}$$

$$v(t) = V_s + [A_1 e^{-4.95t} + A_2 e^{-0.05t}]$$

At steady state :

$$v(\infty) = V_s = 30V$$

$$\therefore v(t) = 30 + [A_1 e^{-4.95t} + A_2 e^{-0.05t}] \quad \text{--- (2)}$$

Using Initial cond<sup>n</sup> :

$$(*) \quad v(0) = 30 + A_1 + A_2 = 15 \quad \text{(from (1))}$$

$$\therefore A_1 + A_2 = -15 \quad \text{--- (3)}$$

$$(*) \quad i(t) = -C \frac{dv(t)}{dt} \Rightarrow \frac{dv(0)}{dt} = \frac{3}{4} = 0.75 \quad \text{(From (1))}$$

$$\text{Also } \frac{dv(0)}{dt} = -4.95A_1 - 0.05A_2 \quad \text{(From (2))}$$

$$\therefore 4.95A_1 + 0.05A_2 = 0.75 \quad \text{--- (4)}$$

Solving (3) & (4) :

$$A_1 = 0.306 \text{ and } A_2 = -15.306 \quad \text{--- (5)}$$

$\therefore$  From (2) & (5) :

$$v(t) = 30 + [0.306 e^{-4.95t} - 15.306 e^{-0.05t}]$$

V


8.49

For  $t < 0$ , capacitor and inductor are open and short circuits respectively.

$$\therefore i(0^-) = 3A + (45/5)A = 12A \quad \text{--- (1)}$$

$$v(0^-) = 0V$$

For  $t > 0$  equivalent ckt :

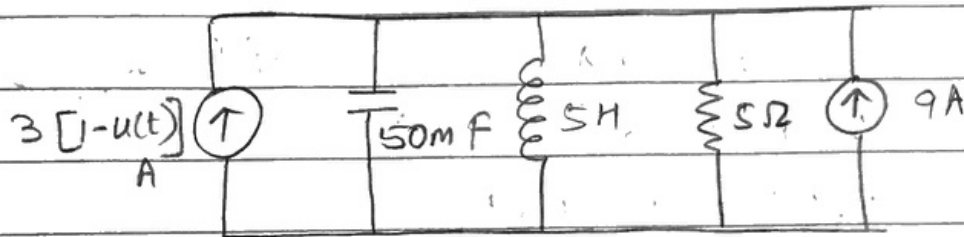

This is a parallel RLC circuit :

$$\alpha = \frac{1}{2RC} = \frac{1}{(2 \times 5 \times 50 \times 10^{-3})} = 2$$

$$\omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{5 \times 50 \times 10^{-3}}} = 2$$

$\Rightarrow \alpha = \omega_0 \Rightarrow$  critically damped.

$$\therefore s_{1,2} = -2$$

For a critically damped system :

$$i(t) = i_{ss}(t) + (A_1 + A_2 t) e^{-\alpha t} \quad \text{--- (2)}$$

For steady state response :

the inductor is a short, all the 9A flows through the inductor.

$$i_{ss} = 9A \quad \text{--- (3)}$$

∴ From (2) & (3) :

$$i(t) = 9 + (A_1 + A_2 t)e^{-2t} \quad - (4)$$

Using Initial Conditions :

$$t = 0$$


$$\begin{aligned} * i(0) &= 9 + A_1 && \text{(from (4))} \\ &= 12A && \text{(from (1))} \\ \therefore A_1 &= 3 && - (5) \end{aligned}$$

$$* v(0) = L \left. \frac{di(t)}{dt} \right|_{t=0}$$

$$\begin{aligned} \therefore \frac{v(0)}{L} &= -2(A_1) + A_2 && \text{(from (4))} \\ &= 0 && \text{(from (1))} \\ \therefore A_2 &= 6 && \text{(from (5))} \end{aligned}$$

$$\therefore \boxed{i(t) = 9 + (3 + 6t)e^{-2t}}$$

8.55

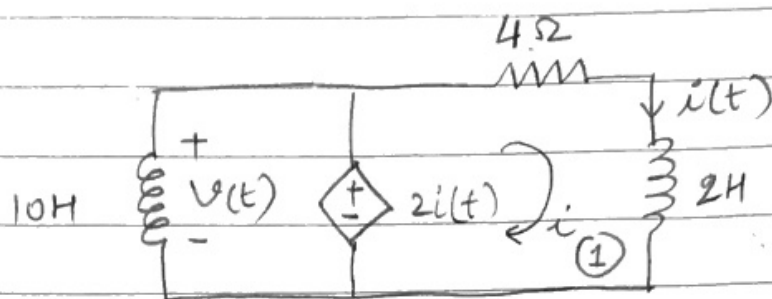

Applying KVL around loop 1:


$$-2i(t) + 4i(t) + 2 \frac{di(t)}{dt} = 0$$

$$\Rightarrow \frac{di(t)}{dt} = -i(t)$$

∴ This is a first order differential eq<sup>n</sup>:

$$\text{General sol}^n: i(t) = A + B e^{-t/2} \quad A - \textcircled{1}$$

$$\text{Now } Z = \frac{L}{R_{Th}}$$

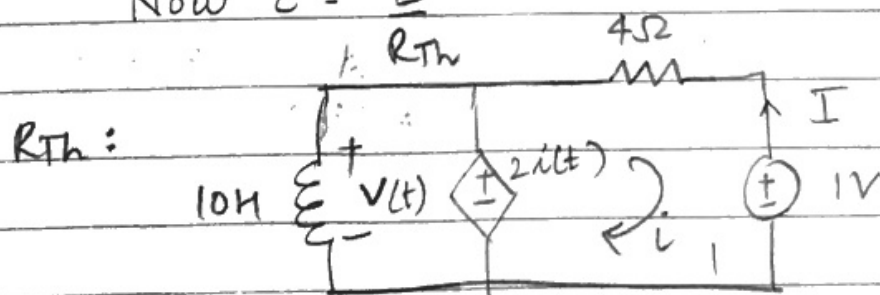


Applying KVL in loop 1:

$$-2i(t) + 4i(t) + 1 = 0$$

$$\Rightarrow i(t) = -\frac{1}{2} = -I$$

$$\therefore R_{Th} = \frac{1V}{I} = 2\Omega$$

8.55

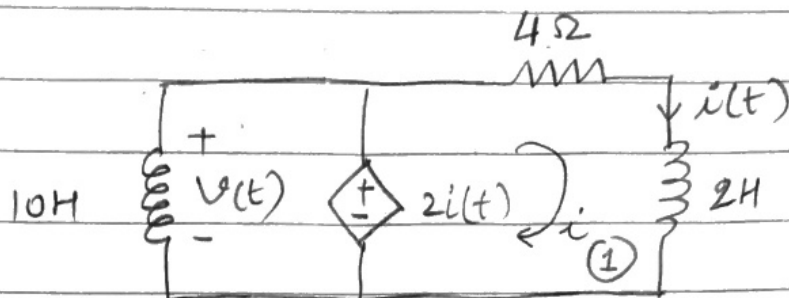

Applying KVL around loop 1:

$$-2i(t) + 4i(t) + 2 \frac{di(t)}{dt} = 0$$

$$\Rightarrow \frac{di(t)}{dt} = -i(t)$$

∴ This is a first order differential eq<sup>n</sup>:

$$\text{General sol}^n: i(t) = i(0) \cdot e^{-t} \quad \text{A} \quad \text{--- (1)}$$

$$\because i(0) = 2\text{A}$$

$$i(t) = 2e^{-t}$$

$$\begin{aligned} v(t) &= 2i(t) \\ &= 4e^{-t} \end{aligned}$$