

Name: SOLUTIONS.

EXAM 1
EECS 215
Introduction to Electronic Circuits
Wednesday, October 11, 2017, 6:00pm-8:00pm

Lecture Section (circle one):	001 Finelli	002 Lahiji
--------------------------------------	--------------------	-------------------

This test consists of 6 problems with points as indicated to total 100 points.

Read through the entire exam before beginning.

Show all work (on the pages provided in this booklet) to earn partial credit.
Briefly explain major steps, include units, and write your final answers in the areas provided.
Do not unstaple the pages.

No credit will be given if no work is shown.

Exam Policies

- No food allowed during exam.
- No books allowed (closed book exam).
- One, 8.5 x 11 inch notes page (ONE SIDED) allowed
- Only scientific calculators allowed (**graphing calculators not permitted**).
- No communication of any kind is allowed. No use of cell phones, computers, or any devices besides calculators. Violation of this will be treated as an honor code violation.
- No credit will be given for this exam without a signed honor pledge.

Write out the honor pledge and sign below.

"I have neither given nor received unauthorized aid on this examination, nor have I concealed any violations of the Honor Code"

I have neither given nor received any
unauthorized aid on this examination, nor have
I concealed any violations of the Honor Code.

Signature: XYZ

Do not write in this space

Problem 1: []/15

Problem 4: []/15

Problem 2: []/20

Problem 5: []/15


Problem 3: []/15

Problem 6: []/20

Total score []/100

Problem 1. (15 points total) Electrical current flowing through an electrical element is given by a sinusoidal signal having a period of $T = 1$ second:

$$i(t) = 10 \sin(2\pi t) \text{ mA}$$

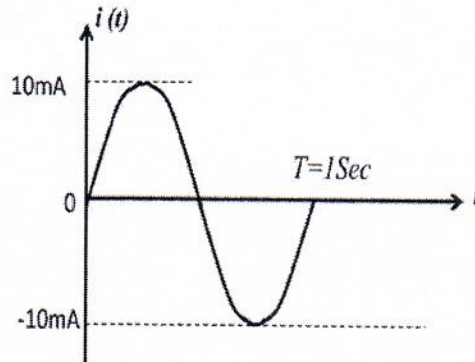

- a. Assuming there is no initial charge in the element, find the total amount of charge that has entered the element at $t = T/2 = 0.5$ sec.

$$q(0) = 0 \text{ C} \quad T = 1 \text{ sec}$$

$$q(t) = \int_0^t i(t) \cdot dt$$

$$q = \int_0^{T/2} 10 \sin(2\pi t) \cdot dt$$

$$q = -\frac{10}{2\pi} [\cos(2\pi t)]_0^{T/2}$$

$$= -\frac{10}{2\pi} [-1 - 1] = 3.18 \text{ mC}$$

Total charge = 3.18 mC (5 points)

- b. If voltage across the element is $v(t) = 5 \frac{di(t)}{dt}$ V, find the power delivered to the device at $t = T/8 = 0.125$ sec.

$$v(t) = 5 \frac{di(t)}{dt} = 5.20\pi \cos 2\pi t = 100\pi \cos 2\pi t \text{ mV}$$

$$P = v \cdot i = 100\pi \times 10^{-3} \cos 2\pi \left(\frac{T}{8}\right) \cdot 10 \times 10^{-3} \sin \left[2\pi \left(\frac{T}{8}\right)\right]$$

$$= 1000\pi \frac{\sqrt{2}}{2} \cdot \frac{\sqrt{2}}{2} \times 10^{-6} = 500\pi \mu\text{W}$$

$$= 1.57 \text{ mW}$$

Power delivered = 1.57 mW (5 points)

- c. Find total energy delivered to the element after one period of the input signal.

$$E = \int_0^T p(t) \cdot dt$$


$$= \int_0^T 1000\pi \times 10^{-6} \cos 2\pi t \cdot \sin 2\pi t \cdot dt$$

$$= \int_0^{1\text{sec}} \frac{\pi \times 10^{-3}}{2} \sin 4\pi t \cdot dt$$

$$= -\frac{\pi \times 10^{-3}}{2 \times 4\pi} [\cos 4\pi t]_0^{1\text{sec}} = 0 \text{ J}$$

Total energy = 0 J (5 points)

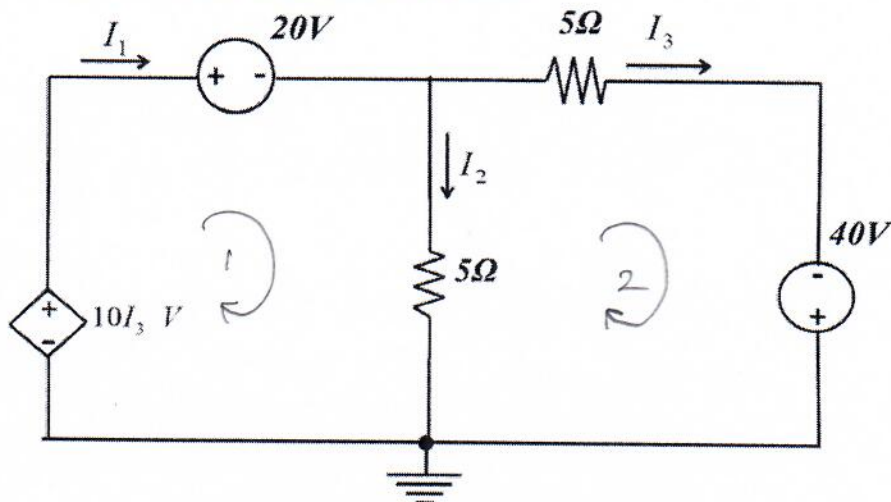Problem 2. (20 points total) For the following circuit:



a. Use KVL/KCL to find the currents I_1 , I_2 , and I_3 .

By writing KVL in loop 1:

$$-10I_3 + 20 + 5I_2 = 0 \quad - \textcircled{1}$$

By writing KVL in loop 2:

$$-40 - 5I_2 + 5I_3 = 0 \quad - \textcircled{2}$$

Adding eqⁿ $\textcircled{1} + \textcircled{2}$:

$$-5I_3 = 20$$

$$\Rightarrow I_3 = -4 \text{ A} \quad - \textcircled{3}$$


Substituting $\textcircled{3}$ in eqⁿ $\textcircled{1}$,

$$I_2 = -12 \text{ A}$$

$$I_1 = I_2 + I_3 = -16 \text{ A}$$

$$I_1 = \underline{-4 \text{ A}}, I_2 = \underline{-12 \text{ A}}, I_3 = \underline{-16 \text{ A}} \quad (10 \text{ points total})$$

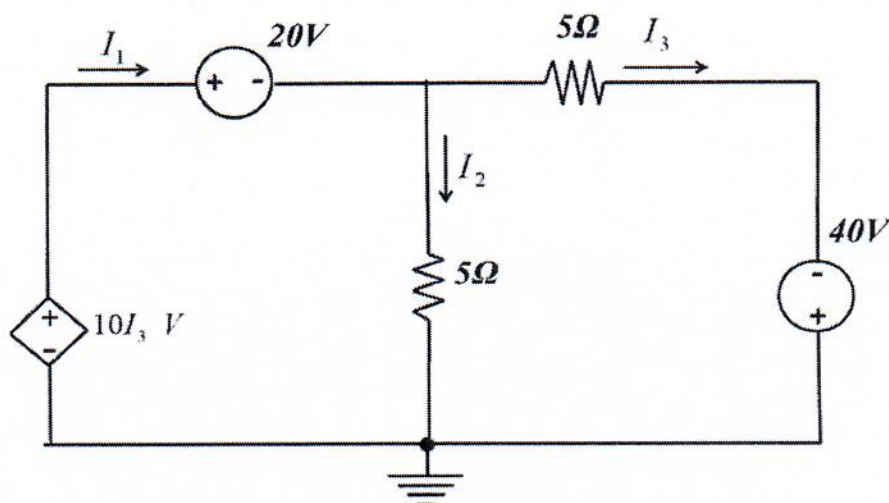- b. For the same circuit (redrawn here for convenience), determine the power absorbed by each element and show that power is conserved in the circuit.



$$P_{10I_3} = -I_1 \cdot V_{10I_3} = -(-16)(10 \cdot (-4)) = -640 \text{ W}$$

$$P_{20V} = I_1 \cdot 20 \text{ V} = -16 \cdot 20 = -320 \text{ W}$$

$$P_{5\Omega} = 5 \cdot I_2^2 = 5 \cdot (-12)^2 = 5 \times 144 = 720 \text{ W}$$

$$P_{5\Omega} = 5 \cdot I_3^2 = 5 \cdot (-4)^2 = 80 \text{ W}$$


$$P_{40V} = -(I_3 \cdot 40 \text{ V}) = 160 \text{ W}$$

$$\begin{aligned} \Sigma \text{ Power} &= P_{10I_3} + P_{20V} + P_{5\Omega} + P_{5\Omega} + P_{40V} \\ &= -640 \text{ W} - 320 \text{ W} + 720 \text{ W} + 80 \text{ W} + 160 \text{ W} \\ &= 0 \text{ W} \end{aligned}$$

Power absorbed by: dependent source = -640 W, 20 V source = -320 W,
middle resistor = 720 W, top resistor = 80 W, 40 V source = 160 W,

Is power conserved? Yes (10 points total)

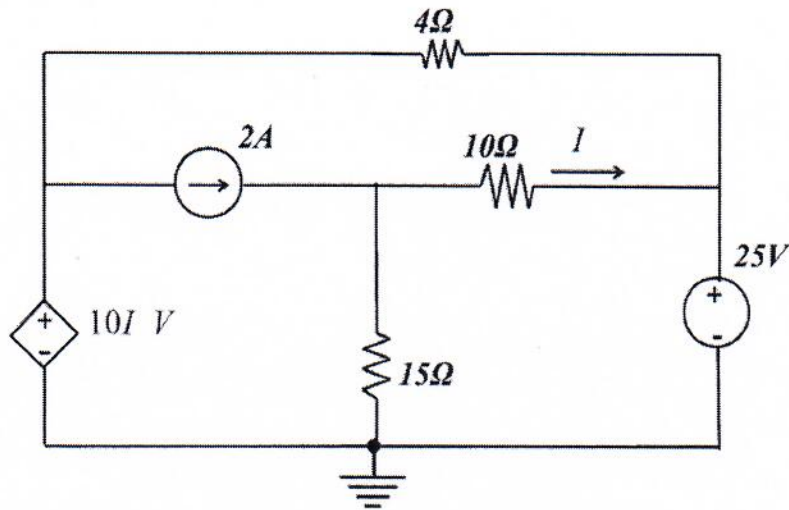
Problem 3. (15 points) In this circuit, use superposition to determine the value of current I in 10Ω resistor



$$I = I_{01} + I_{02} \rightarrow \begin{array}{l} \text{due to } 2A \\ \text{source} \end{array} \quad \begin{array}{l} \text{due to } 25V \\ \text{source} \end{array}$$


I_{01} : Open circuit $2A$ current source

$$I_{01} = \frac{-25V}{10 + 15} = -1A$$

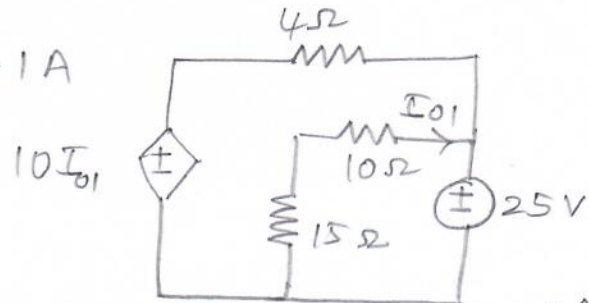

I_{02} : Short circuit $25V$ source

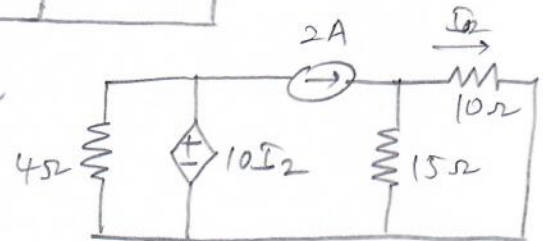
$$\begin{aligned} I_{02} &= 2A \cdot \left(\frac{15 \parallel 10}{10} \right) \\ &= 2A \cdot \left(\frac{15}{25} \right) \\ &= 1.2A \end{aligned}$$



$$\therefore I = I_{01} + I_{02} = 0.2A$$

$$I = \underline{0.2A} \text{ (15 points)}$$

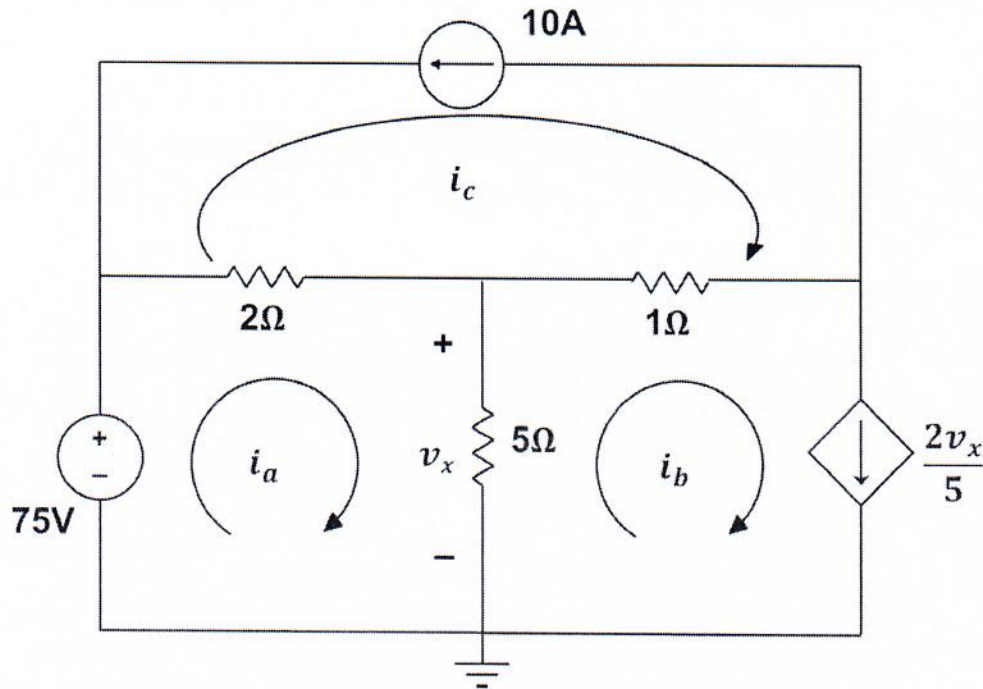Problem 4. (15 points) For this circuit, apply mesh analysis to find the currents i_a , i_b , and i_c .



KVL around mesh a:

$$-75 + 2(i_a - i_c) + 5(i_a - i_b) = 0$$

$$7i_a - 5i_b - 2i_c = 75 \quad (1)$$

KVL around mesh b not needed since $i_b = 2v_x/5$
 constraint eqn: $v_x = 5(i_a - i_b)$ } $i_b = 2(i_a - i_b)$
 $i_a = \frac{3}{2}i_b \quad (2)$

KVL around mesh c not needed since $i_c = -10A \quad (3)$

combine equations (1) + (3)

$$7i_a - 5i_b + 20 = 75 \Rightarrow 7i_a - 5i_b = 55 \quad (4)$$


combine equations (4) and (2)

$$\frac{21}{2}i_b - 5i_b = 55 \Rightarrow i_b = 10A$$

$$i_a = \frac{3}{2}i_b \Rightarrow i_a = 15A$$

$$i_a = \underline{15A}, i_b = \underline{10A}, i_c = \underline{-10A} \quad (15 \text{ points total})$$

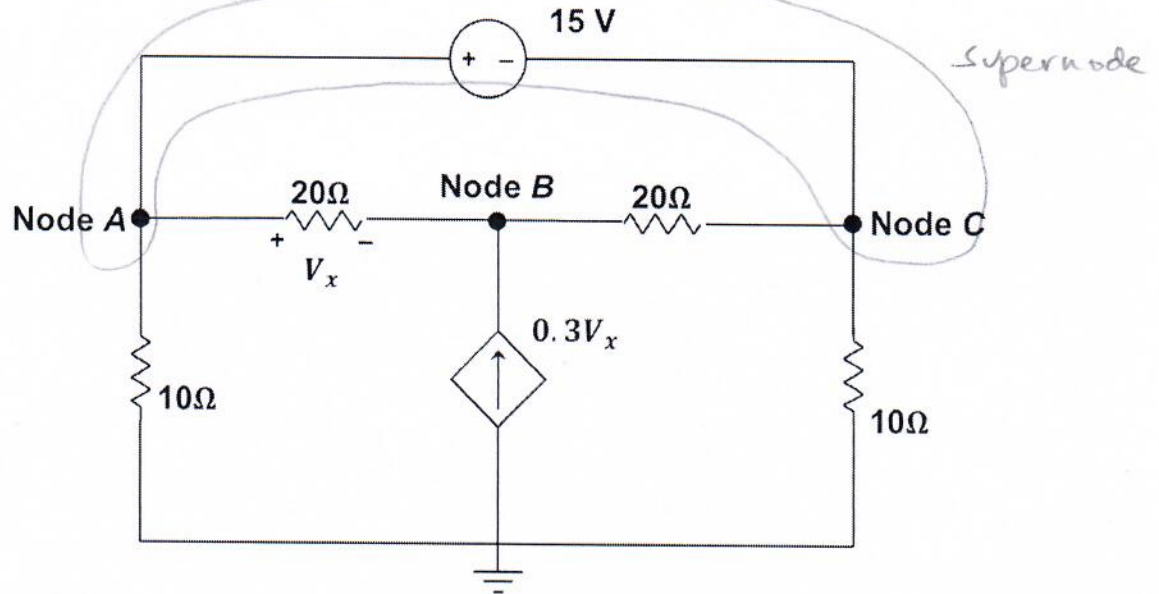Problem 5. (15 points total) Derive the three independent equations that would be required to solve for the node voltages by completing the steps outlined below.
(Note, you are not asked to solve the system of equations).



- a. Noting that a voltage source is connected between Nodes A and C, write KCL at the supernode between those two nodes and simplify the equation.

$$\left(\frac{V_A}{10} + \frac{(V_A - V_B)}{20} + \frac{(V_C - V_B)}{20} + \frac{V_C}{10} = 0 \right) 20$$


$$2V_A + (V_A - V_B) + (V_C - V_B) + 2V_C = 0$$

$$3V_A - 2V_B + 3V_C = 0$$

$$\underline{2} V_A + \underline{-2} V_B + \underline{3} V_C = \underline{0} \text{ (5 points)}$$

The blanks above should be integers

Circuit redrawn here for convenience

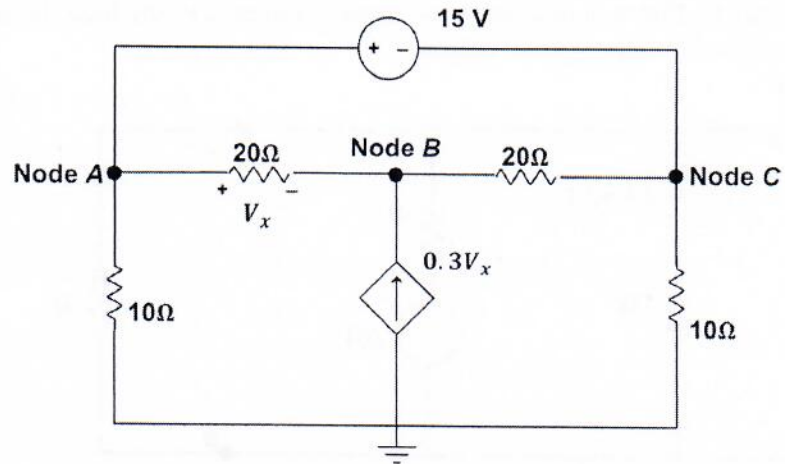

- b. Write the constraint equation for the 15V source

$$V_A - V_C = 15$$

$$\underline{1} V_A + \underline{0} V_B + \underline{-1} V_C = \underline{15} \quad (5 \text{ points})$$

The blanks above should be integers

- c. Write KCL at node B.

$$\frac{V_B - V_A}{20} - 0.3 V_x + \frac{V_B - V_C}{20} = 0$$

$$\text{and } V_x = V_A - V_B$$


$$\left(\frac{V_B - V_A}{20} - \frac{3}{10} (V_A - V_B) + \frac{V_B - V_C}{20} = 0 \right) 20$$

$$V_B - V_A - 6(V_A - V_B) + (V_B - V_C) = 0$$

$$\underline{-7} V_A + \underline{8} V_B + \underline{-1} V_C = \underline{0} \quad (5 \text{ points})$$

The blanks above should be integers

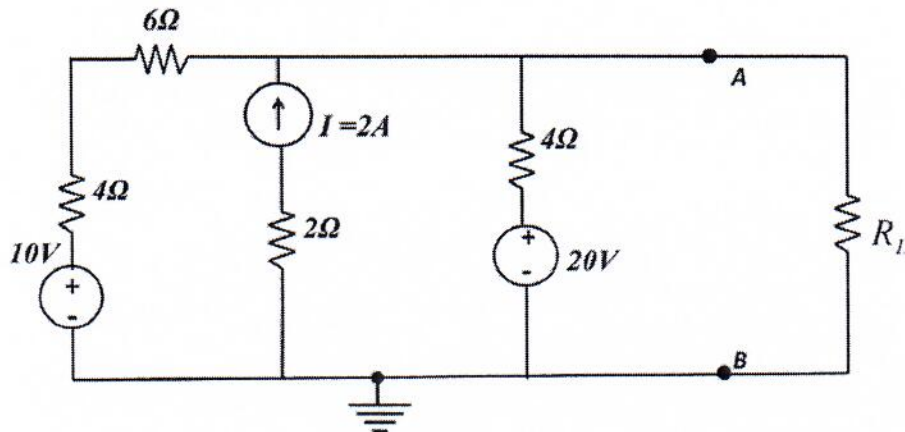Problem 6. (20 points total) For the circuit below, we desire to calculate the value of the load resistor R_L that will maximize the power delivered to the load. In doing this, complete the steps outline below.



- a. Find the Thevinin equivalent of the circuit at terminals A-B.

Using Nodal Analysis in the ckt with R_L removed or open ckt:


$$-2 + \frac{V_{ab}-10}{10\Omega} + \frac{V_{ab}-20}{4\Omega} = 0$$

$$-2 + \frac{2V_{ab}-20+5V_{ab}-100}{20\Omega} = 0$$


$$7V_{ab} = 160, \quad V_{ab} = \frac{160}{7} \text{ V}$$

To find R_{Th} , we turn off all independent sources:
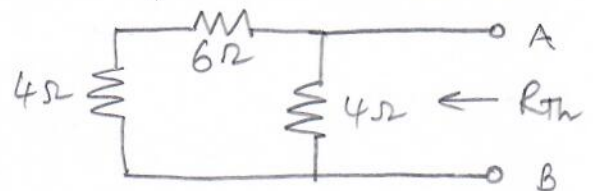
$$R_{Th} = \frac{10 \times 4}{10+4} = \frac{40}{14} = \frac{20}{7} \Omega$$



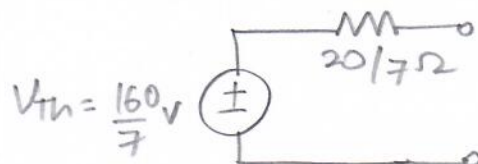Draw the Thevenin's equivalent circuit here:




(10 points)

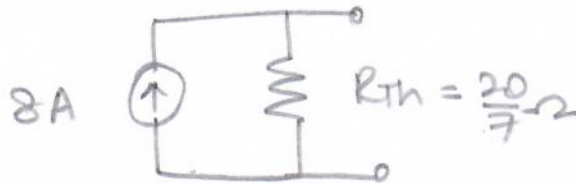- b. Find the Norton's current and resistance.

$$I_N = \frac{V_{Th}}{R_{Th}} = \frac{160 \times 7}{20 \times 7} = 8 \text{ A}$$

Draw the Norton's equivalent circuit here:



(5 points)

- c. Find R_L to extract the maximum power, and also calculate the amount of this maximum power.

For maximum power transfer to load,

$$R_L = R_{Th}$$

$$\Rightarrow R_L = \frac{20}{7} \Omega$$

$$P_{max} = \left(\frac{V_{Th}}{R_{Th} + R_L} \right)^2 R_L = \frac{V_{Th}^2}{4 R_{Th}}$$

$$= \frac{1}{4} \times \frac{160^2}{7^2 \times \frac{20}{7}}$$

$$= 45.715 \text{ W}$$

$$R_L = \underline{\frac{20}{7} \Omega}, \text{ power} = \underline{45.715 \text{ W}} \text{ (5 points total)}$$