

Your name: Partial Solution Key

**EECS 215.  
Final Exam  
April 25, 2016**

**This text consists of 8 problems with points as indicated to total 90 points.  
Please note that Laplace tables are attached at the end of the exam.**

Read through the entire exam before beginning.

**Show all work** (on the pages provided in this booklet) to earn partial credit.

**No credit will be given if no work is shown.**

Briefly explain major steps, include units, and write your final answers in the areas provided.  
Do not unstaple the pages.

**Exam policies**

- The College of Engineering Honor Code is followed. Please write and sign the honor code pledge ("I have neither given nor received unauthorized aid on this examination, nor have I concealed any violations of the Honor Code.") in the box below.
- Only scientific calculators are allowed – no exceptions.
- No communication of any kind is allowed. No use of cell phones, computers, or any devices besides *scientific* calculators.
- Three sides of 8.5x11 inch notes pages are allowed. No books allowed (closed book exam).

Write and sign the honor pledge:

Signed: \_\_\_\_\_

\_\_\_\_\_  
No credit will be given for this exam without a signed honor pledge.

Do not write in this space

Problem 1: [    ]/10

Problem 2: [    ]/10

Problem 3: [    ]/15

Problem 4: [    ]/10

Problem 5: [    ]/5


Problem 6: [    ]/15

Problem 7: [    ]/10

Problem 8: [    ]/15

**Total score [    ]/90**

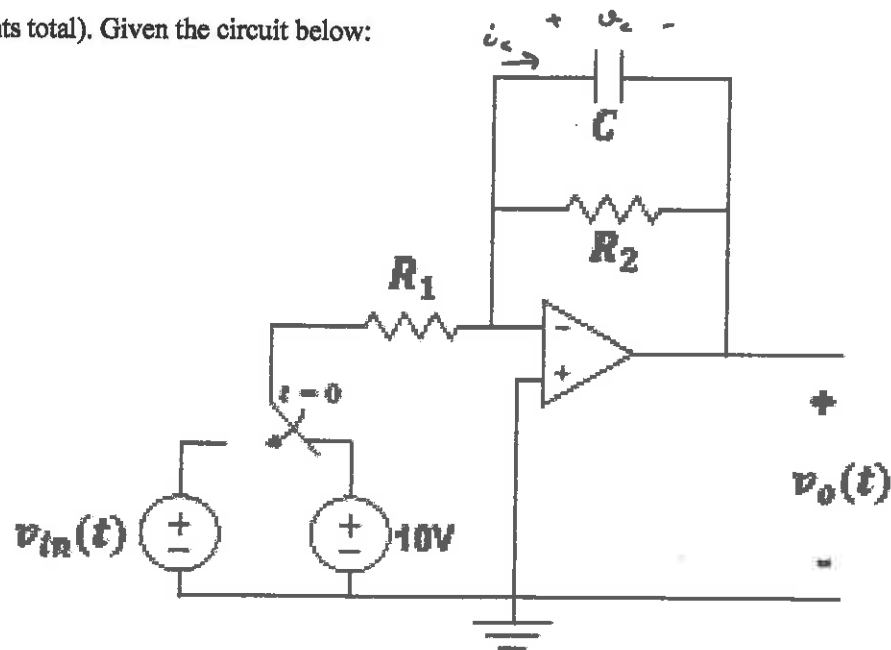1. (10 points total). Given the circuit below:



- (2 points). Assuming switch has been connected to the 10V source for a long time prior to switching at  $t = 0$ , determine the initial value for the voltage  $v_o(0^+)$ .
- (8 points). Derive (but do not solve) the differential equation describing  $v_o(t)$ ,  $t \geq 0$ .

Part a)

The capacitor looks like an open-circuit in steady-state.  
Therefore, at  $t = 0^-$ ,

$$\frac{0-10}{R_1} + \frac{v_c(0^-)}{R_2} = 0$$

$$\Rightarrow v_c(0^-) = \frac{R_2}{R_1} \times 10 = v_c(0^+)$$

Also,  $v_c = -v_o \Rightarrow v_c(0^+) = -v_o(0^+)$

$$\Rightarrow v_o(0^+) = -\frac{R_2}{R_1} \times 10 \text{ volts}$$

Write your answer here:

a.  $v_o(0^+) = -\frac{R_2}{R_1} \times 10 \text{ volts}$

b. Differential equation for  $v_o(t)$ :  $\frac{dv_o}{dt} + \frac{1}{R_2 C} v_o = -\frac{1}{R_1 C} v_{in}(t)$

Problem 1 score: [ ]/10

Part b)

KCL at the op-amp - terminal, for  $t \geq 0$

$$\frac{0 - v_{in}(t)}{R_1} + \frac{0 - v_o(t)}{R_2} + i_c = 0$$

Also,  $i_c = C \frac{dv_c}{dt} = -C \frac{dv_o}{dt}$

Therefore,

$$\frac{-v_{in}(t)}{R_1} + \frac{-v_o(t)}{R_2} - C \frac{dv_o(t)}{dt} = 0$$

$$\Rightarrow C \frac{dv_o}{dt} + \frac{v_o}{R_2} = - \frac{v_{in}(t)}{R_1}$$

$$\Rightarrow \frac{dv_o}{dt} + \frac{1}{R_2 C} v_o = - \frac{1}{R_1 C} v_{in}(t)$$

2. (10 points total). A circuit voltage is governed by the following differential equation and initial conditions:

$$\frac{d^2v}{dt^2} + 4\frac{dv}{dt} + 3v = -10e^{-5t}, \quad v(0) = 3, \quad \left.\frac{dv}{dt}\right|_{t=0} = v'(0) = 5$$

- a. (8 points). Use the Laplace transform method to solve for  $V(s)$ . Express your answer as the ratio of two polynomials.
- b. (2 points). Is this circuit critically damped, underdamped, or overdamped?

a)

$$s^2 V(s) - s v(0) - v'(0) + 4(s V(s) - v(0)) + 3 V(s) = \frac{-10}{s+5}$$

$$(s^2 + 4s + 3)V(s) - 3s - 5 - 12 = \frac{-10}{s+5}$$

$$V(s) = \frac{\frac{-10}{s+5} + \frac{(3s+17)(s+5)}{s+5}}{s^2 + 4s + 3}$$

$$V(s) = \frac{3s^2 + 32s + 75}{(s^2 + 4s + 3)(s+5)}$$

b)

$$\zeta = \frac{4}{2} = 2, \quad \omega_0 = \sqrt{3} = \sqrt{3}; \quad \zeta > \omega_0 \Rightarrow \boxed{\text{overdamped}}$$


Write your answer here:

a.  $V(s) =$  \_\_\_\_\_

- b. Which type of damping (circle one): critically damped, underdamped, overdamped

Problem 2 score: [ ]/10

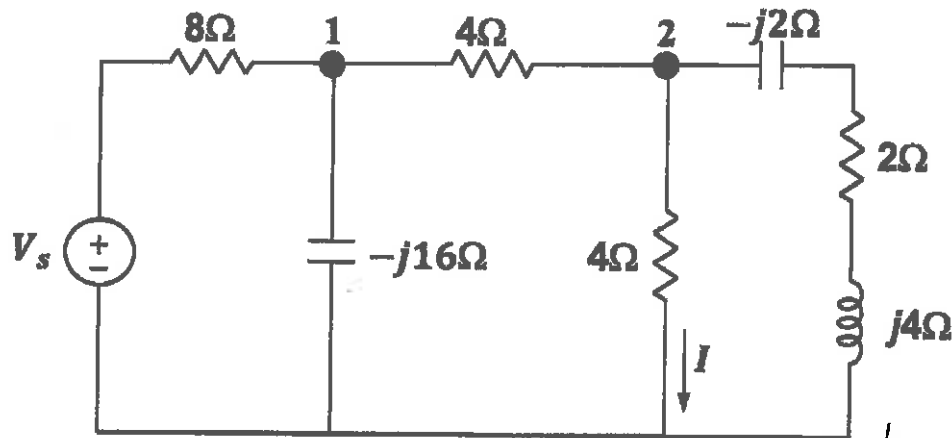3. (15 points total). Given the circuit below:



- (9 points). Establish the nodal equations for nodes 1 and 2, and express the equations in matrix form. Simplify the equations so that each element of the matrix is a complex number in rectangular form. (See part b for an example of the required form.)
- (6 points). The nodal matrix equation for the same circuit but with some different component values is given below. (The  $4\Omega$  resistor from node 2 to ground is unchanged from the above figure.) Find the voltage at node 1 ( $V_1$ ) when the  $4\Omega$  resistor has a current  $I = 3\angle 45^\circ$  A.

Part a.

$$\begin{bmatrix} 3 + 2j & -5 \\ -2 - 3j & 1 + 2j \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} (5 + 2j)V_s \\ 0 \end{bmatrix}$$

KCL node 1,

$$\frac{V_1 - V_s}{8} + \frac{V_1}{-j16} + \frac{V_1 - V_2}{4} = 0$$

$$\Rightarrow V_1 \left( \frac{1}{8} + j\frac{1}{16} + \frac{1}{4} \right) - \frac{1}{4}V_2 = \frac{1}{8}V_s$$

Multiply throughout by 16.

$$\Rightarrow V_1 (2 + j + 4) - 4V_2 = 2V_s$$

$$\Rightarrow V_1 (6 + j) - 4V_2 = 2V_s$$

Write your answer here:

a. Please clearly circle your solution, written in matrix form, above or on the next page.

b.  $V_1 = \underline{7.4421 \angle 52.125^\circ} \text{ Volts}$

Problem 3 score: [ ]/15

KCL node 2,

$$\frac{V_2 - V_1}{4} + \frac{V_2}{4} + \frac{V_2}{2+j2} = 0$$

$$\Rightarrow \frac{V_2 - V_1}{4} + \frac{V_2}{4} + \frac{V_2(2-j2)}{8} = 0$$

Multiply throughout by 4,

$$\Rightarrow V_2 - V_1 + V_2 + V_2(1-j) = 0$$

$$\Rightarrow -V_1 + V_2(3-j) = 0$$

In matrix form,

$$\begin{bmatrix} 6+j & -4 \\ -1 & 3-j \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} 2V_s \\ 0 \end{bmatrix}$$

Part b

$$V_2 = 4I = 12 \angle 45^\circ$$

$$(-2-3j)V_1 + (1+2j)V_2 = 0$$

$$\Rightarrow V_1 = \frac{1+2j}{2+3j} \times V_2 = \frac{(1+2j)(2-3j)}{4+9} \times V_2 = \frac{2+6+j(4-3)}{13} \times V_2$$

$$= \frac{8+j}{13} \times 12 \angle 45^\circ$$

$$= \frac{\sqrt{65} \times 12}{13} \angle 45^\circ + \tan^{-1}\left(\frac{1}{8}\right)$$

$$= 7.4421 \angle 52.125^\circ \text{ Volts}$$

4. (10 points total). An inductive load connected to a 220 V power supply draws a current of 7.6 A. (Both voltage and current are RMS values.) The average power delivered to the load is 1317 W.
- (4 points). Find the apparent power, the reactive power, and the power factor of the load. (Don't forget to specify whether the power factor is leading or lagging.)
  - (4 points). The system frequency is  $\omega = 377$  rad/sec. Determine the capacitance of a parallel capacitor that will result in a power factor of 1 (unity power factor) for the combined load and capacitor.
  - (2 points). What is the value of the current drawn from the power supply after the capacitor is installed?

### Part a

Apparent power,  $|S| = |V| \times |I| = 220 \times 7.6 = 1672 \text{ VA}$

Power factor,  $pf = \frac{P}{|S|} = \frac{1317}{1672} = 0.7877$

- the load is inductive so the power factor is lagging

Reactive power:  $|S|^2 = P^2 + Q^2$

$\Rightarrow Q = \sqrt{|S|^2 - P^2} = \sqrt{1672^2 - 1317^2} = 1030.1 \text{ VAR}$

### Part b

To achieve unity power factor, the capacitor must fully compensate the reactive power drawn by the load. Therefore,

$Q_{cap} = \frac{V^2}{X_c} = 1030.1 \Rightarrow X_c = \frac{220^2}{1030.1} = 47 \Omega$

$X_c = \frac{1}{\omega C} \Rightarrow C = \frac{1}{\omega X_c}$

$= \frac{1}{377 \times 47} = 56.45 \mu\text{F}$

### Part c

In this case,  $|S| = P = |V| \times |I|$

$\Rightarrow |I| = \frac{P}{|V|} = \frac{1317}{220} = 6.0 \text{ Amps}$

Write your answer here:

- Apparent power: 1672 VA  
Reactive power: 1030.1 VAR  
Power factor: 0.7877 lagging
- Capacitance: 56.45  $\mu\text{F}$
- Current: 6.0 Amps

Problem 4 score: [ ]/10

5. (5 points total). A load impedance with  $S = 500 - j200$  VA is supplied from a voltage source  $V_s = 10\angle 20^\circ$  volts (RMS).
- (2 points). Compute the current drawn by the load, expressed as an RMS phasor in polar form.
  - (2 points). Determine the apparent power and the power factor of the load.
  - (1 points). Sketch the complex power triangle, clearly labelling  $P$ ,  $Q$  and  $S$ .

Part a

$$S = VI^* \Rightarrow I = \left(\frac{S}{V}\right)^* = \frac{500 + j200}{10\angle -20^\circ} = \frac{538.5165\angle 21.90^\circ}{10\angle -20^\circ}$$

$$\Rightarrow I = 53.8516\angle 41.80^\circ \text{ Amps}$$


Part b

Apparent power =  $|S| = 538.5165$  VA (from above).

$$\text{Power Factor} = \frac{P}{|S|} = \frac{500}{538.5165} = 0.9285 \text{ leading}$$

(Power factor is leading because the current phasor leads the voltage phasor.)

Part c

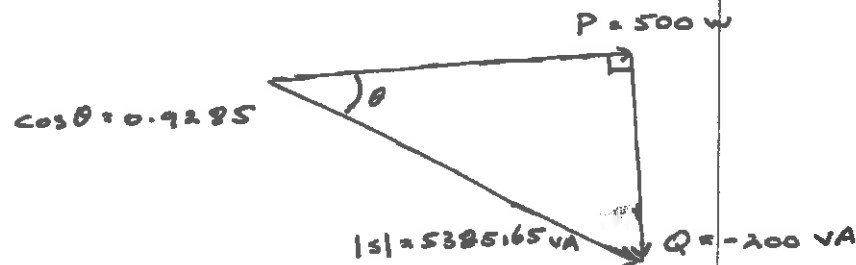

Write your answer here:

a. Current: 53.8516  $\angle$  41.80° Amps

b. Apparent power: 538.5165 VA

Power factor: 0.9285 leading

c. Please circle your clearly labeled power triangle above or on the next page.

Problem 5 score: [ ]/5



6. (15 points total). A circuit is characterized by the following transfer function:

$$H(s) = \frac{V_o(s)}{V_i(s)} = \frac{5s + 2}{(s^2 + 2s + 1)} = \frac{5s + 2}{(s+1)^2}$$

Apply partial fraction expansion to find the output  $v_o(t)$  if  $v_i(t) = 10 u(t)$  Volts.  $\Rightarrow V_i(s) = \frac{10}{s}$

$$V_o(s) = \frac{10(5s+2)}{s(s+1)^2} = \frac{A}{s} + \frac{B}{(s+1)^2} + \frac{C}{s+1}$$

$$A = 10 \left( \frac{5s+2}{(s+1)^2} \right) \Big|_{s=0} = 20$$

$$B = 10 \left( \frac{5s+2}{s} \right) \Big|_{s=-1} = \frac{-3}{-1} = 30$$

$$C = 10 \left( \frac{d}{ds} \left( \frac{5s+2}{s} \right) \Big|_{s=-1} \right) = 10 \left( \frac{s5 - (5s+2)}{s^2} \right) \Big|_{s=-1} = 10 \left( \frac{-5 - (-5+2)}{1} \right) = -20$$

$$v_o(t) = \mathcal{L}^{-1} \left\{ \frac{20}{s} + \frac{30}{(s+1)^2} + \frac{-20}{s+1} \right\}$$


$$v_o(t) = (20 + 30t e^{-t} - 20 e^{-t}) u(t)$$

Write your answer here:



$$v_o(t) = \underline{\hspace{10cm}}$$

Problem 6 score: [ ]/15

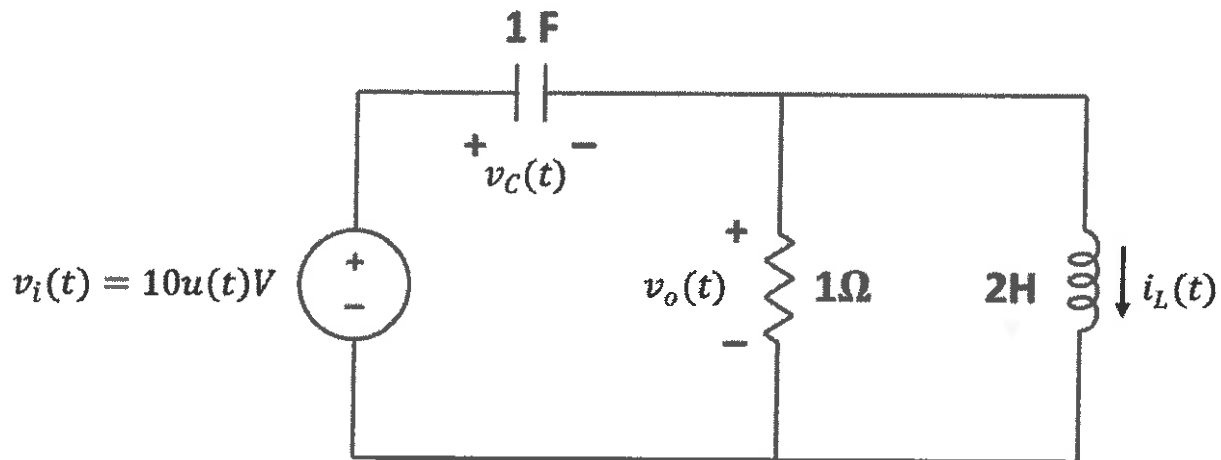7. (10 points). Given the circuit below with initial conditions  $v_C(0) = 0$  and  $i_L(0) = \frac{1}{2} A$ .



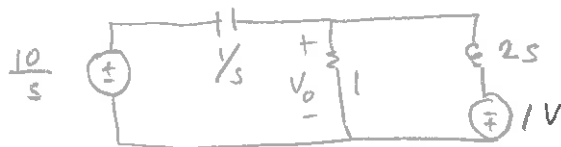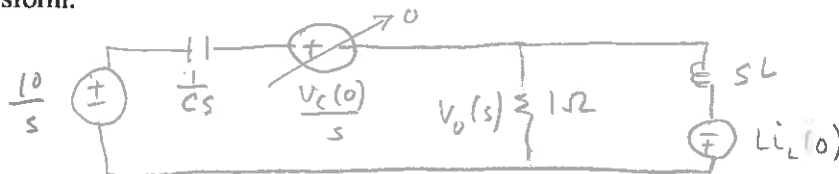- a. (3 points). Draw the s-domain circuit.  
b. (7 points). Solve for  $V_o(s)$ , the Laplace transform of  $v_o(t)$ . Do not compute the inverse Laplace transform.



KCL

$$\frac{V_o - 10/s}{1/s} + \frac{V_o}{1} + \frac{V_o + 1}{2s} = 0$$

$$2s \left( sV_o - 10 + V_o + \frac{1}{2s} V_o + \frac{1}{2s} = 0 \right)$$

$$(2s^2 + 2s + 1) V_o = 20s - 1$$

$$V_o(s) = \frac{20s - 1}{2s^2 + 2s + 1}$$

Write your answer here:

- a. Please circle the s-domain circuit above or on the next page  
b.  $V_o(s) =$  \_\_\_\_\_

Problem 7 score: [ ]/10

8. (15 points total). A circuit has a voltage transfer function as follows:

$$H(s) = \frac{V_o(s)}{V_i(s)} = \frac{500s}{s^2 + 1000s + 250,000}$$

$$H(j\omega) = \frac{500j\omega}{1000j\omega + 250,000 - \omega^2}$$

- (2 points). What is the resonant frequency  $\omega_o$  for the filter?
- (2 points). What is  $M_o$ , the magnitude of the transfer function at the resonant frequency?
- (3 points). Write  $H(s)$  in standard form for Bode plots.
- (5 points). Sketch the straight-line approximation to the magnitude response using the semilog paper on the next page.
- (2 points). Indicate the location of  $\omega_o$  on the Bode plot.
- (1 point). What type of filter does this circuit represent?

a)  $\omega_o$  when  $|H(j\omega)|$  real  $\Rightarrow$  when denominator purely imag.

$$\omega_o^2 = 250,000 \Rightarrow \boxed{\omega_o = 500 \text{ rad/sec}}$$

$$b) M_o = \left| \frac{500j(500)}{1000j(500)} \right| = \boxed{\frac{1}{2}}$$

$$c) H(s) = \frac{500s}{250,000 \left( 1 + 2j\zeta \frac{s}{500} + \left( \frac{s}{500} \right)^2 \right)} = \frac{s/500}{\left( 1 + s/500 \right)^2}$$

$\zeta = 1$

• zero at origin,  $k = 500 \Rightarrow$

mag = straight line, slope = 20 dB/dec  
crossing origin at  $\omega = 500$

• double pole at  $\omega_c = 500 \Rightarrow$

mag = flat until  $\omega = 500$ , then  
straight line slope = -40 dB/dec

20 dB/dec  
 $\omega = 500$

500  
-40 dB/dec

d, e) see attached

f) bandpass

Write your answer here:

- $\omega_o =$  \_\_\_\_\_
- $M_o =$  \_\_\_\_\_
- $H(s) =$  \_\_\_\_\_
- Sketch the magnitude plot on the next page
- Label  $\omega_o$  on the sketch.
- Filter type: \_\_\_\_\_

Problem 8 score: [ ]/15

