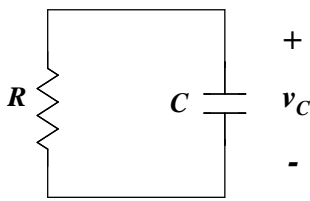
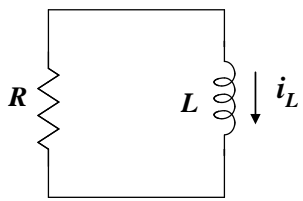




EECS 215 Equation and Procedure Sheet

First/Second Order Circuits

Jamie Phillips

First Order Circuits



Source-free RC ($v_s=0$)	Source-free RL ($v_s=0$)
	
$v_C(t) = v_C(0)e^{-t/RC} = v_C(0)e^{-t/\tau}$	$i_L(t) = i_L(0)e^{-tR/L} = i_L(0)e^{-t/\tau}$

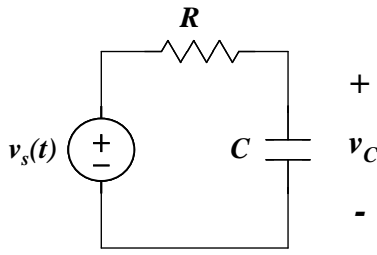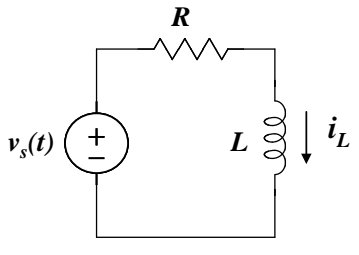Step response RC ($v_s=V_S u(t)$)	Step response RL ($v_s=V_S u(t)$)
	
$v_C(t) = V_S + (v_C(0) - V_S)e^{-t/RC}$	$i_L(t) = \frac{V_S}{R} + \left(i_L(0) - \frac{V_S}{R} \right) e^{-tR/L}$

General procedure for first order circuits:

- 1) Find Thevenin/Norton equivalent
- 2) Write differential equation for simple circuit – variable on left side of equation and forcing function on right.
- 3) Determine natural solution (forcing function = 0). Common trial function is Ke^{st} , determine s by inserting into differential equation.
- 4) Determine forced solution. Use trial function that resembles forcing function. Insert trial function into differential equation to determine unknown constants. If the differential equation does not work, use a different trial function.
- 5) Write complete solution (natural + forced). Apply initial/boundary condition to determine unknown constant (for example, the value K in the natural solution)

Second Order Circuits

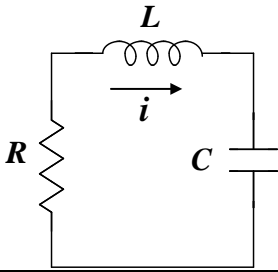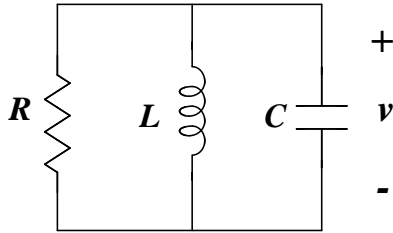Source-free Series RLC ($v_s=0$) (or natural solution for series RLC)	Source-free Parallel RLC ($v_s=0$) (or natural solution for parallel RLC)
	
Differential Equation: $\frac{d^2 i}{dt^2} + \frac{R}{L} \frac{di}{dt} + \frac{i}{LC} = 0$	Differential Equation: $\frac{d^2 v}{dt^2} + \frac{1}{RC} \frac{dv}{dt} + \frac{v}{LC} = 0$
Characteristic Equation: $s^2 + s \frac{R}{L} + \frac{1}{LC} = 0$	Characteristic Equation: $s^2 + s \frac{1}{RC} + \frac{1}{LC} = 0$
Roots: $s_{1,2} = -\frac{R}{2L} \pm \sqrt{\left(\frac{R}{2L}\right)^2 - \frac{1}{LC}}$ $s_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2}$ $\alpha = \frac{R}{2L} \quad \omega_0 = \frac{1}{\sqrt{LC}}$	Roots: $s_{1,2} = -\frac{1}{2RC} \pm \sqrt{\left(\frac{1}{2RC}\right)^2 - \frac{1}{LC}}$ $s_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2}$ $\alpha = \frac{1}{2RC} \quad \omega_0 = \frac{1}{\sqrt{LC}}$
Solutions: Overdamped, $\alpha > \omega_0$ $i(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t}$ Critically damped, $\alpha = \omega_0$ $i(t) = (A_1 t + A_2) e^{-\alpha t}$ Underdamped, $\alpha < \omega_0$ $i(t) = (B_1 \cos \omega_d t + B_2 \sin \omega_d t) e^{-\alpha t}$ $\omega_d = \sqrt{\omega_0^2 - \alpha^2}$	Solutions: Overdamped, $\alpha > \omega_0$ $v(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t}$ Critically damped, $\alpha = \omega_0$ $v(t) = (A_1 t + A_2) e^{-\alpha t}$ Underdamped, $\alpha < \omega_0$ $v(t) = (B_1 \cos \omega_d t + B_2 \sin \omega_d t) e^{-\alpha t}$ $\omega_d = \sqrt{\omega_0^2 - \alpha^2}$

General procedure for second order circuits:

- 1) Determine differential equation using nodal analysis or other circuit technique. Arrange differential equation with variables on left, forcing function on right. The differential equation will look like the following

$$\frac{d^2v}{dt^2} + 2\alpha \frac{dv}{dt} + \omega_0^2 v = f(t)$$

where $f(t)$ is the forcing function. Note that if you are solving for current, the differential equation will be in terms of i instead of v .

- 2) Begin determination of the natural solution (forcing function = 0) by determining coefficients in the characteristic equation. In class, we had used the trial function is Ke^{st} and determined s by inserting into differential equation, resulting in the following characteristic equation.

$$s^2 + 2\alpha s + \omega_0^2 = 0$$
$$s_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2}$$

Determine the value of α and ω_0 given the differential equation in 1).

- 3) Determine if circuit is overdamped, critically damped, or underdamped based on values of α and ω_0 . Determine the natural solution based on this result.

Overdamped, $\alpha > \omega_0$

$$v(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t}$$

Critically damped, $\alpha = \omega_0$

$$v(t) = (A_1 t + A_2) e^{-\alpha t}$$

Underdamped, $\alpha < \omega_0$

$$v(t) = (B_1 \cos \omega_d t + B_2 \sin \omega_d t) e^{-\alpha t}, \quad \omega_d = \sqrt{\omega_0^2 - \alpha^2}$$

Do not solve for unknown coefficients (A_1 , A_2 , B_1 , B_2 , etc) until you have the complete solution!

- 4) Determine forced solution. Use trial function that resembles forcing function. Insert trial function into differential equation to determine unknown constants. If the differential equation does not work, use a different trial function.
- 5) Write the complete solution (natural + forced). Apply initial/boundary conditions to determine unknown constants (A_1 , A_2 , B_1 , B_2 , etc). Note that you will need two initial/boundary values. These will typically be $v(0^+)$ and $dv(0^+)/dt$, or $v(0^+)$ and $v(\infty)$ for the case of a forcing function applied at $t=0$.