

HW # 2 Solutions

Assignment problems:

2.13

2.17

2.25

2.32


2.41

2.44

2.59. (a)

2.59

2.13

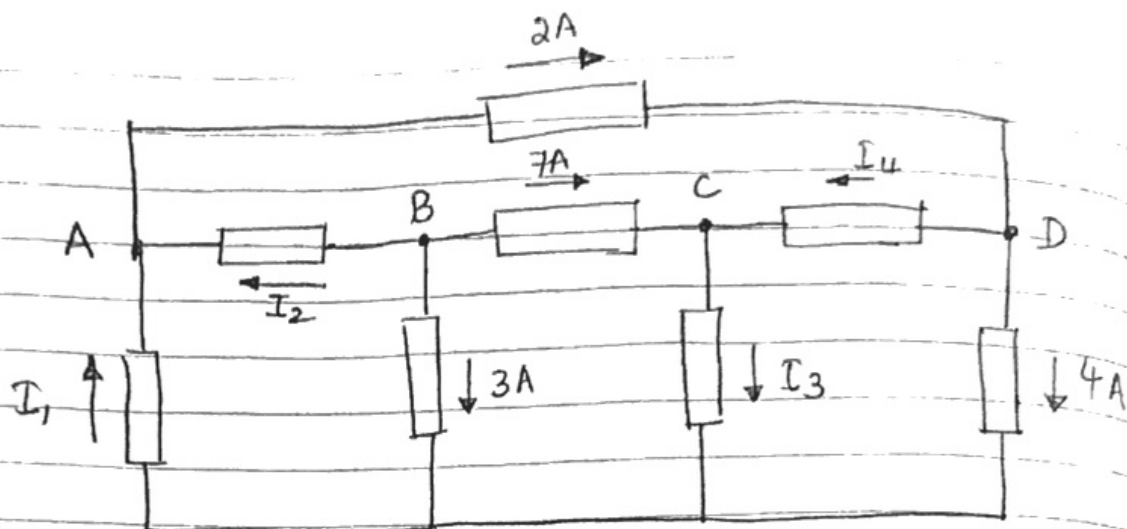

At node B, $\sum I_o = 0$... (KCL)

$$\Rightarrow 3 + 7 + I_2 = 0$$

$$\Rightarrow I_2 = -10A$$

At node A, $\sum I = 0$... (KCL)

$$2 = I_2 + I_1$$

$$= -10 + I_1$$

$$\Rightarrow I_1 = 12A$$

At node D, $\sum I = 0$... (KCL)

$$2 = 4 + I_4$$

$$\Rightarrow I_4 = -2A$$


At node C, $\sum I_o = 0$

$$\Rightarrow I_3 = I_4 + 7$$

$$= -2 + 7$$

$$= 5A$$

2.17

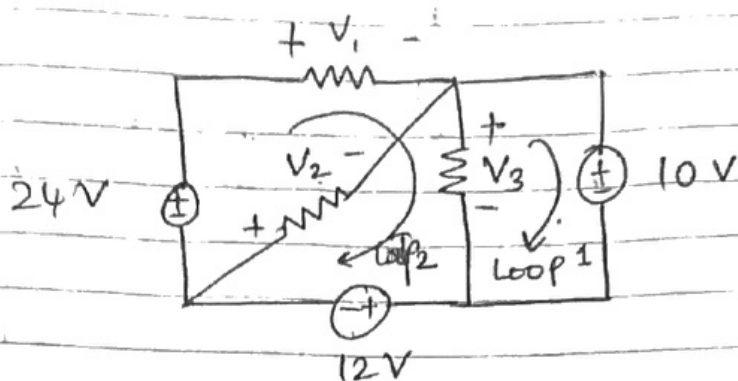

Applying KVL in loop 1:

$\frac{1}{2}$

$$V_3 = 10V.$$

Applying KVL in loop 2:

(1)


$$24 - 12 = V_1 + V_3$$

$$12 = V_1 + 10$$

$\frac{1}{2}$

$$\Rightarrow \underline{\underline{V_1 = 2V.}}$$

2.25

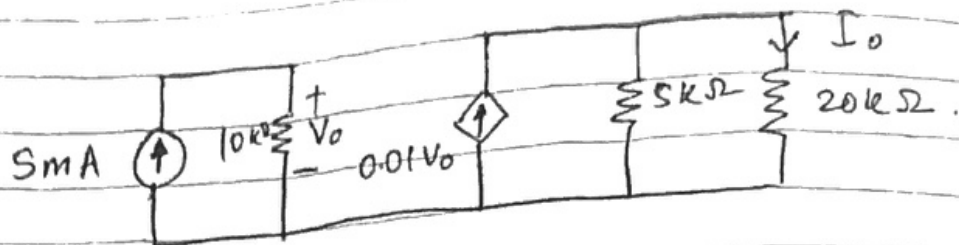

(1/2)

$$V_0 = 5 \times 10^{-3} \times 10 \times 10^3 = \underline{\underline{50 \text{ V}}}$$

By current divider

(1)

$$I_0 = \frac{5}{(20+5)} \times 0.01 \times 50$$

$$= 0.1 \text{ A}$$


∴ Power across 20k resistor =


(1)

$$(0.1)^2 \times 20 \times 10^3$$

$$= \underline{\underline{0.2 \text{ KW}}}$$

2.32

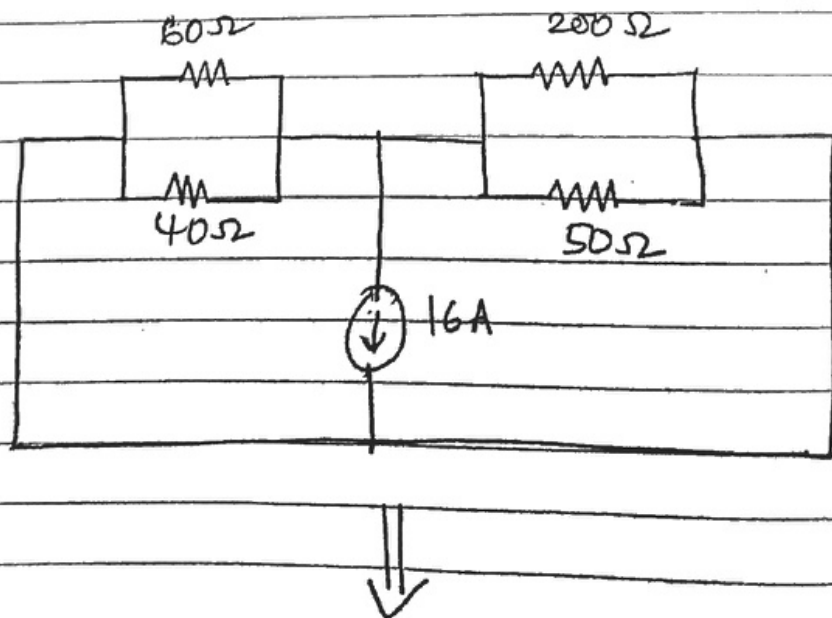

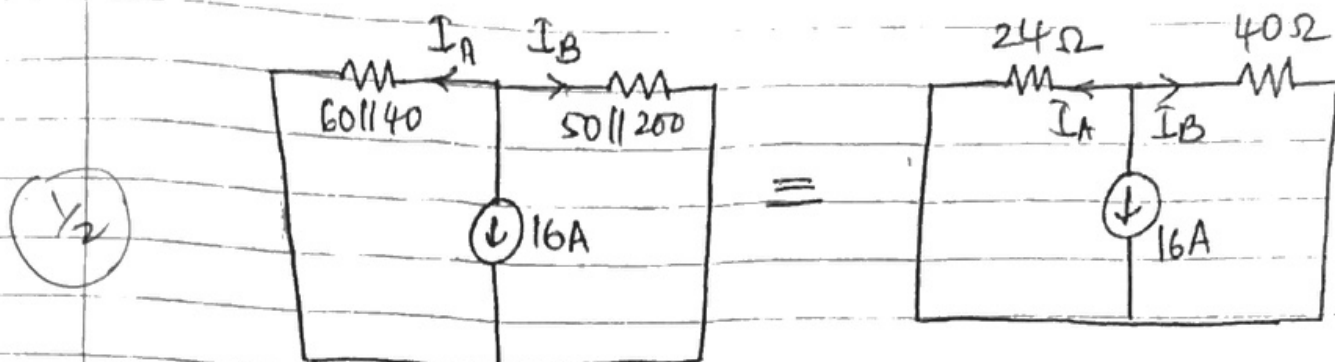


Current Division


$$\therefore I_A = -\frac{40}{64} \times 16 = -10 \text{ A}$$

$$\therefore I_B = -6 \text{ A.}$$




Now, for the I_A branch:

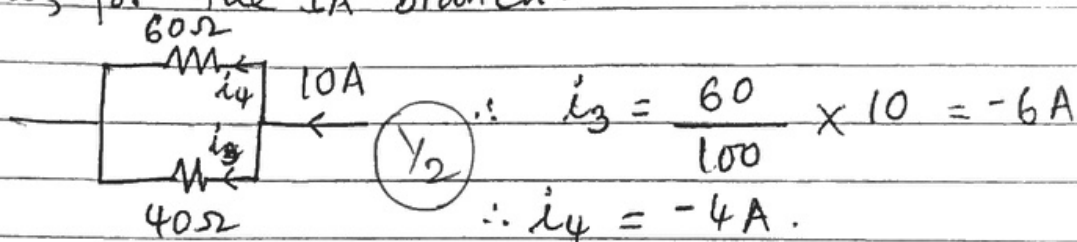

And for the I_B branch:

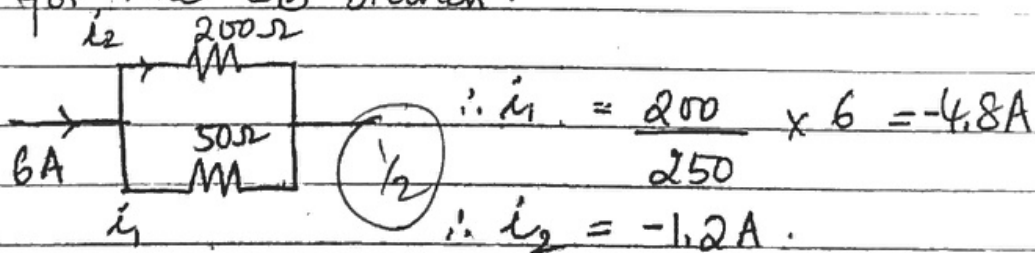

2.41

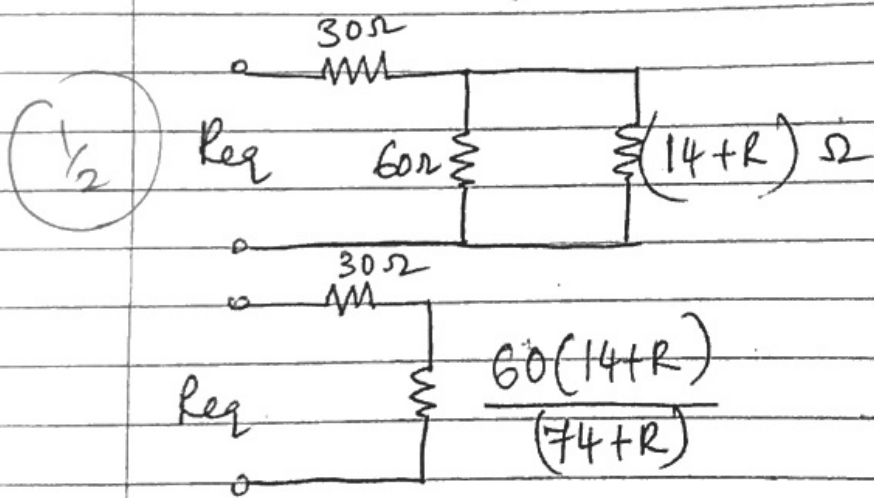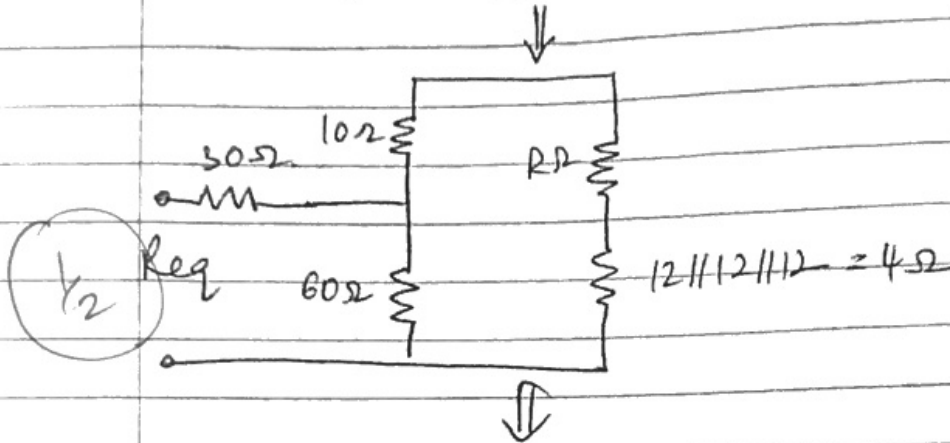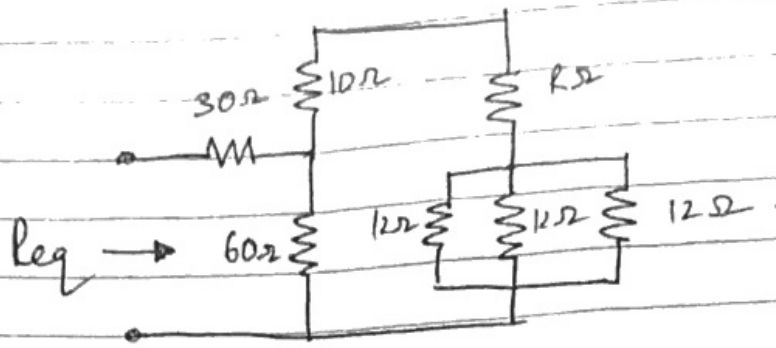


$\therefore R_{eq} = 50 = \frac{30(74+R) + 840 + 60R}{74+R}$

$$3700 + 50R = 2220 + 30R + 840 + 60R$$


$640 = 40R$

$$\Rightarrow \underline{\underline{R = 16 \Omega}}$$


2.44

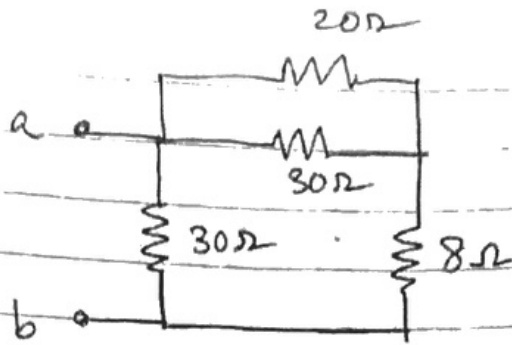

\Downarrow
 $20 \parallel 30 = 12\Omega$

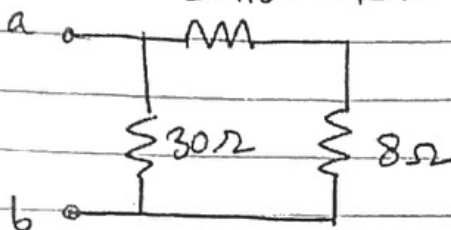


\Downarrow

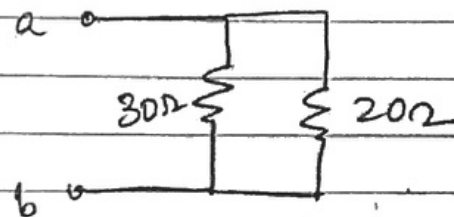

\Downarrow
 $R_{eq} \Rightarrow 12\Omega \quad \therefore R_{ab} = 12\Omega$

2.5/a

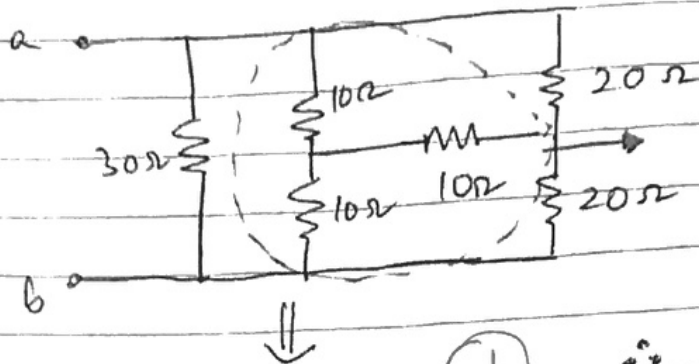


changing from
Wye to Delta
network

∴ For Delta network,


$$R_a = R_b = R_c = \frac{100 + 100 + 100}{10}$$

$$= 30 \Omega$$


(1)

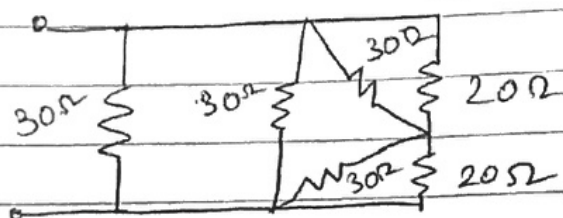

(1/2)

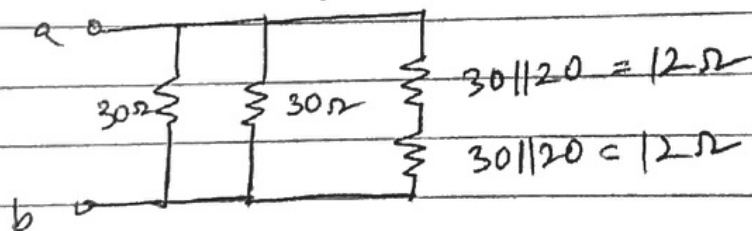

(1/2)

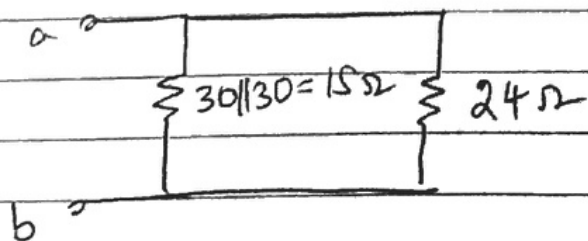


∴ $R_{ab} = 15 \parallel 24 = \frac{120}{13} \Omega$

(1/2)

$$= 9.231 \Omega$$

2.59

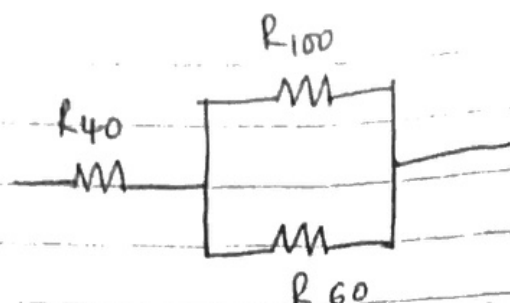

\therefore Voltage rating of each bulb is 110 V,
if we replace each bulb by resistors,

$$R_{40} = (110)^2 / 40 = 302.5 \Omega$$

$$R_{100} = (110)^2 / 100 = 121 \Omega$$

$$R_{60} = (110)^2 / 60 = 201.67 \Omega$$

\therefore If this ckt is connected to a 220 V supply,

$$I_{\text{tot}} = \frac{220}{302.5 + (121 \parallel 201.67)}$$

$$= 0.582 \text{ A}$$

$$\therefore \text{Voltage across } R_{40} = 302.5 \times 0.582$$

$$= \underline{176.05 \text{ V}}$$

|| Much higher than rated voltage (110V)

\therefore This bulb will burn out!

$$\text{Voltage across } R_{100} \text{ \& } R_{60} = 43.95 \text{ V}$$


To prevent the bulbs from burning out,

$$V_{40} \leq 110 \text{ V}; V_{60} \leq 110 \text{ V}; V_{100} \leq 110 \text{ V}$$

Now,
 $V = IR.$

∴ For a given current level,
 if $R \uparrow$, $V \uparrow$

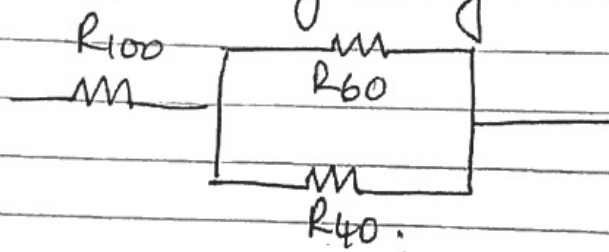So, if we want to use the same series and parallel combination, then the two bulbs with the highest resistances should be in \parallel^2 with each other, while the bulb with the lowest resistance should be in series with the \parallel^2 combination, thus yielding!



Checking:

$$R_{tot} = (302.5 \parallel 201.67) + 121 = 242.001 \Omega$$

$$V_{100} = \frac{121}{242.001} \times 220 \approx 110 \text{ V}!$$

$$V_{60 \parallel 40} = 110 \text{ V}!$$

∴ This combination will work.