

HW 5

SOLUTIONS

* 5.5

* 5.18


* 5.21

* 5.39

* 5.47

* 5.66

5.5

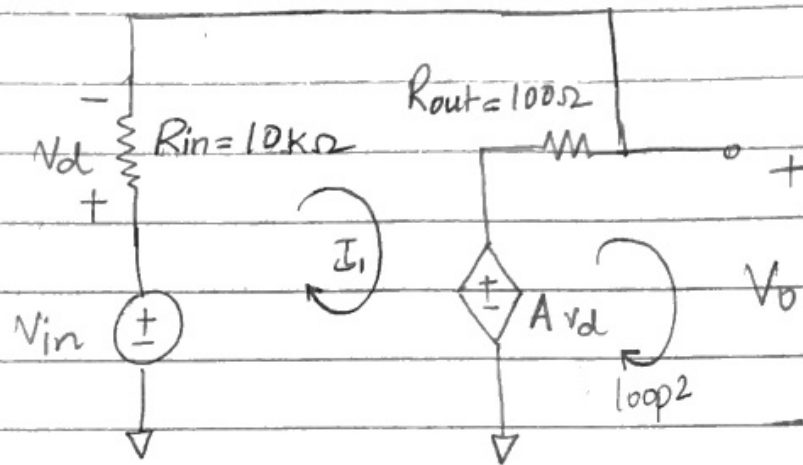

Applying KVL around loop 1:

$$\textcircled{1} \quad -V_{in} + R_{in} \cdot I + R_{out} I + A v_d = 0 \quad - \textcircled{1}$$

By Inspection:

$$v_d = I R_{in}$$

$$- \textcircled{2}$$

From $\textcircled{1}$ and $\textcircled{2}$:

$$\textcircled{X_2} \quad I = \frac{V_{in}}{(R_{in} + A R_{in} + R_{out})} \quad - \textcircled{3}$$

Applying KVL around loop 2:

$$\textcircled{1} \quad -A v_d - I R_{out} + V_o = 0$$

$$\Rightarrow V_o = \frac{A V_{in} R_{in}}{(R_{in} + A R_{in} + R_{out})}$$

$$- \frac{R_{out} V_{in}}{(R_{in} + A R_{in} + R_{out})} = 0$$

(From $\textcircled{3}$)

$\frac{1}{2}$

$$\frac{V_o}{V_{in}} =$$

$$\frac{A R_{in} + R_{out}}{(R_{in} + A R_{in} + R_{out})}$$


(Dividing throughout by V_{in})

Now substituting $R_{in} = 10k\Omega$, $R_{out} = 100\Omega$
and $A = 10^5$

$\frac{1}{2}$

$$\therefore \frac{V_o}{V_{in}} = 0.99$$

5.18

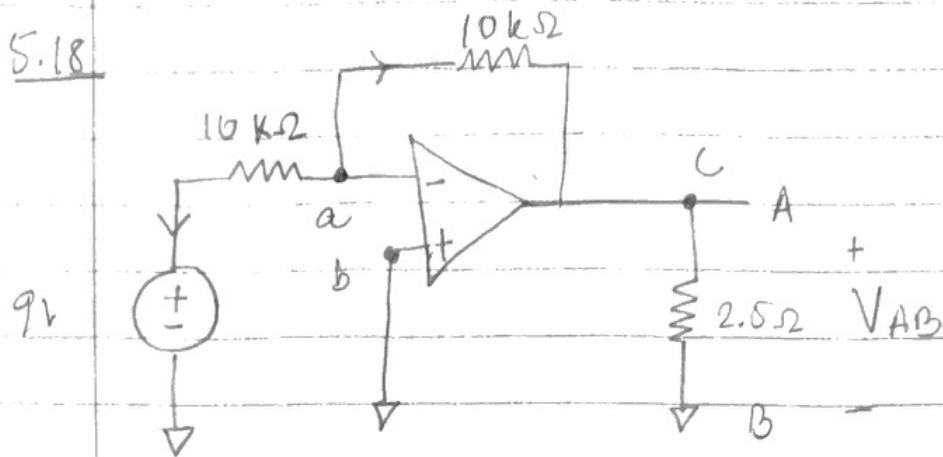

To find the thevenin equivalent, we find the open ckt voltage, V_{AB} and short ckt current, I_{sc} . $\therefore R_{th} = \frac{V_{AB}}{I_{sc}}$

Applying KCL at node a:

$$\textcircled{1} \quad \frac{V_a - 9}{10k} + \frac{V_a - V_c}{10k} = 0 \quad (\text{Assuming ideal op-amp})$$

— (1)

Now, for an ideal op-amp:

$$V_a = V_b = 0V \quad \text{— (2)}$$

$\textcircled{1/2}$

From (1) + (2) :

$\textcircled{1/2}$

$$V_c = -9V$$

$$\Rightarrow V_c = V_{AB} = -9V$$


Approach I for R_{th}

Now, if there's a short ckt between A & B,


① $I_{sc} = \infty$ $\therefore R_{th} = \frac{V_{AB}}{I_{sc}} = 0\Omega$

Approach II for R_{th}

Equivalent ckt for op-amp:

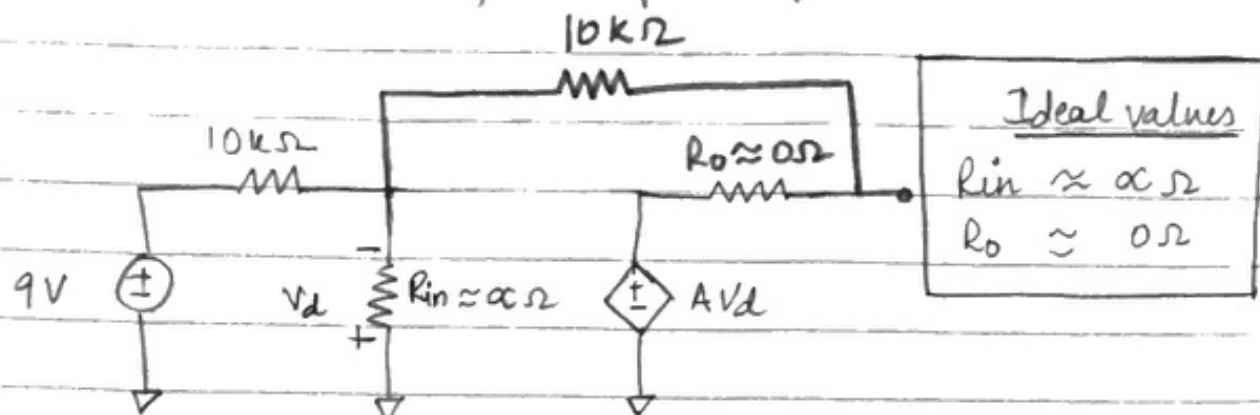

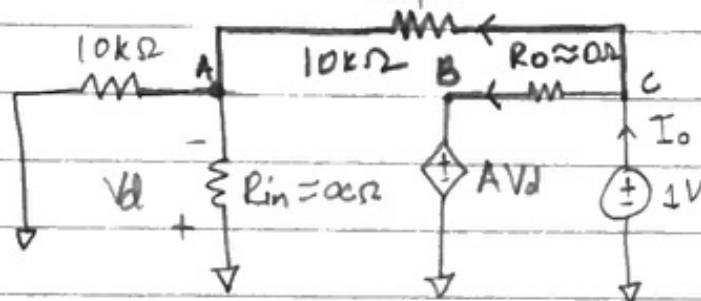
⇓ Short the 9V source but not the dependent source.



Applying KCL at node C: $I_o = \frac{1 - AV_d}{R_o} + \frac{1 + V_d}{10k\Omega}$
 $\therefore R_o \approx 0, \frac{1 - AV_d}{R_o} \approx \infty \therefore I_o \approx \infty$


$\therefore R_{th} = 1V / I_o \approx 0\Omega$

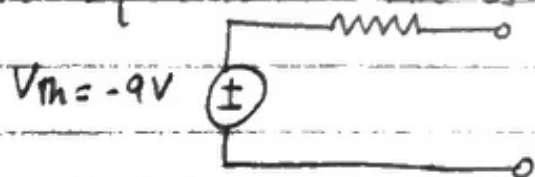\therefore Thevenin Equivalent: $R_{th} = 0\Omega$



①/2

5.21

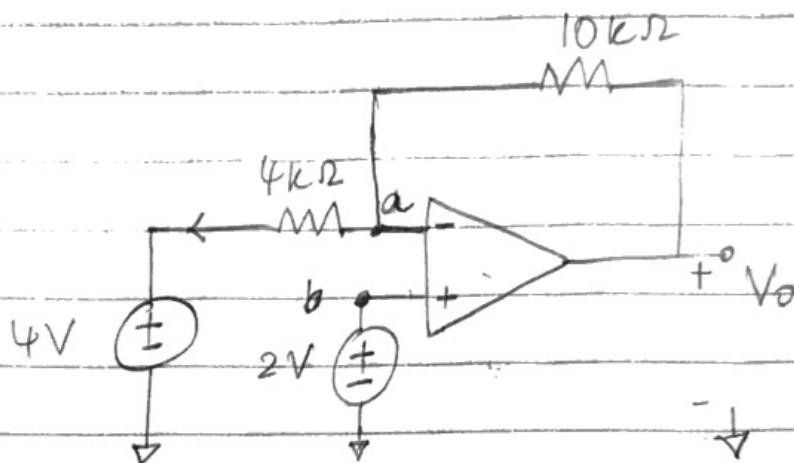

Applying KCL at node a:

$$\textcircled{1} \quad \frac{V_a - 4}{4k} + \frac{V_a - V_o}{10k} = 0 \quad \text{--- (1)}$$

(Assuming Ideal op-Amp)

Now, for an ideal op-Amp:


$$\textcircled{1} \quad V_a = V_b = 2V \quad \text{--- (2)}$$

From (1) & (2):

$$\frac{-2}{4} + \frac{2 - V_o}{10} = 0$$
$$10 \times (-0.5 + 0.2) = V_o$$

$$\textcircled{1} \quad \Rightarrow \quad \boxed{V_o = -3V}$$

5.39

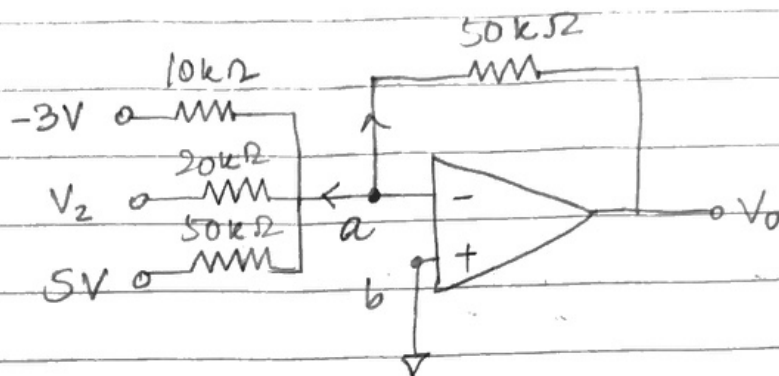

Applying KCL at node a :

$$(1) \quad \frac{V_a + 3V}{10k} + \frac{V_a - V_2}{20k} + \frac{V_a - 5V}{50k} + \frac{V_a - V_o}{50k} = 0$$

(Assuming Ideal Op-Amp) - (1)

Now for an ideal Op-Amp :

$$(1) \quad V_a = V_b = 0V. \quad - (2)$$

From (1) & (2) :


$$\frac{3}{10} - \frac{V_2}{20} - \frac{5}{50} + \frac{16.5}{50} = 0$$

$$\Rightarrow \frac{30 - 10 + 33}{5} = V_2$$

(1)

$$V_2 = 10.6V$$

5.47

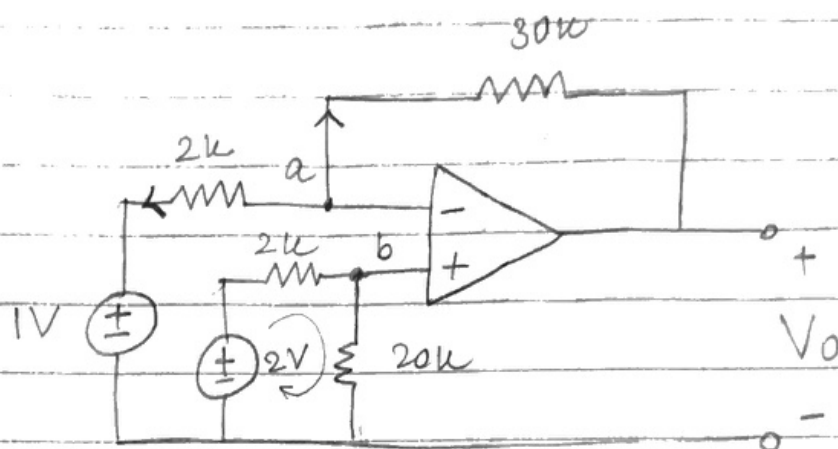

At node b, $V_b =$ voltage across $20k$ resistor.

Applying voltage divider rule:

$$(1) \quad V_b = \frac{20}{22} \times 2V = \frac{20}{11} V.$$

Now, for an ideal op-amp:

$$(2) \quad V_a = V_b = \frac{20}{11} V. \quad \text{--- (1)}$$


Applying KCL at a:

$$(1) \quad \frac{V_a - 1}{2k} + \frac{V_a - V_o}{30k} = 0$$

$$V_o = 30k \left(\frac{0.818}{2k} + \frac{1.818}{30k} \right).$$

$$(2) \quad \therefore \boxed{V_o = 14.09 V}$$

5.66

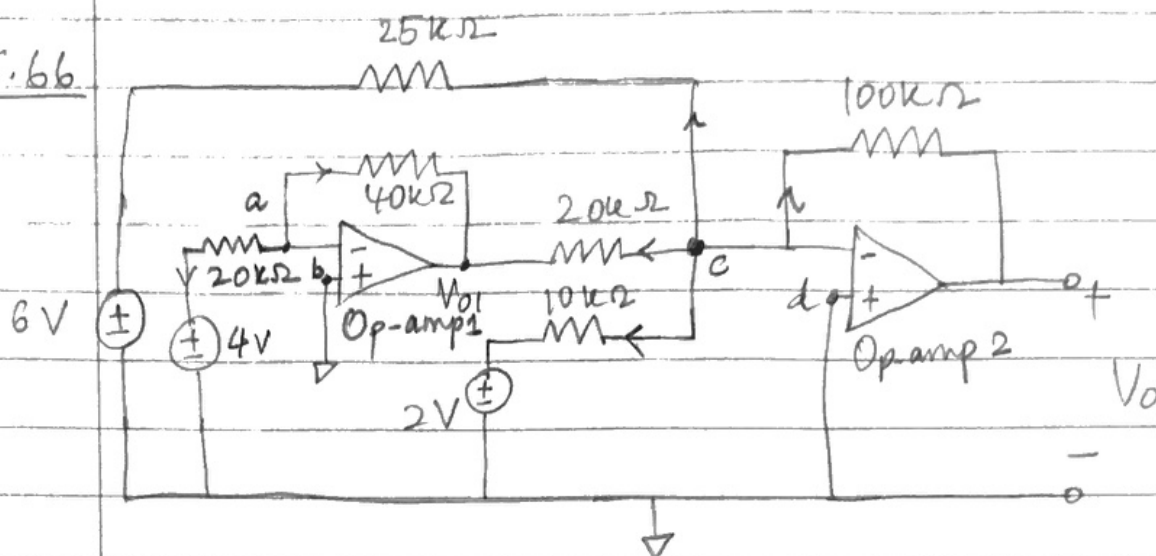

For an ideal op-Amp 1:

(1) $V_a = V_b = 0$ — (1)

Applying KCL at a:

(1/2)
$$\frac{V_a - 4V}{20k} + \frac{V_a - V_{o1}}{40k} = 0$$

$$\frac{2}{40k} \times \left(-\frac{4}{20k} \right) = V_{o1} \text{ (From (1))}$$

(1/2)
$$V_{o1} = -8V$$
 — (2)

For an ideal op-Amp 2:

(1/2)
$$V_c = V_d = 0V$$
 — (3)

Thus, applying KCL at node c:

(1)
$$\frac{V_c - 2V}{10k} + \frac{V_c - V_{o1}}{20k} + \frac{V_c - 6V}{25k} + \frac{V_c - V_o}{100k} = 0$$

$$\therefore V_o = -2 \left(\frac{100}{10} \right) + 8 \left(\frac{100}{20} \right) + 6 \left(\frac{100}{25} \right)$$

$\frac{1}{2}$

\therefore

$$V_0 = -4V$$