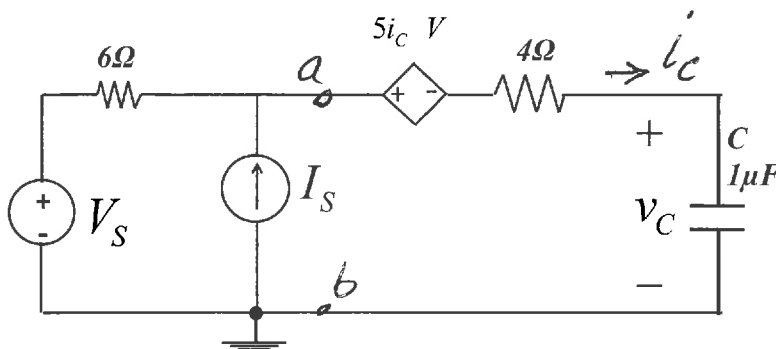



Name :

ID #

Problem # 1(20 Points)

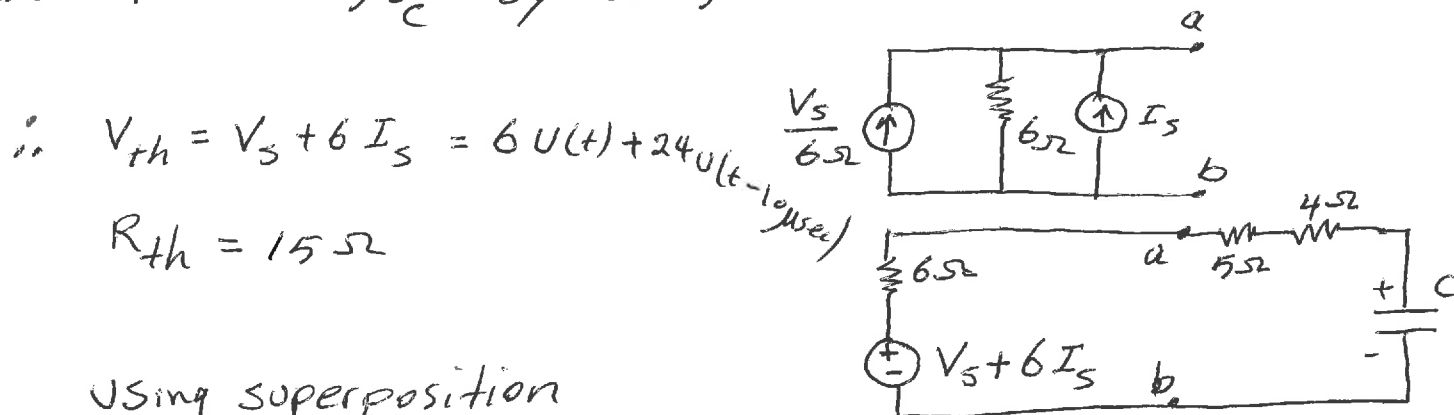a) Find $v_C(t)$ in the following circuit if $V_S(t) = 6u(t)$ and $I_S(t) = 4u(t - 10\mu\text{sec})$.


Let's first do some source transformation, and also replace $5i_C$ by a 5Ω resistance.



$$\therefore V_{th} = V_S + 6I_S = 6U(t) + 24U(t - 10\mu\text{sec})$$

$$R_{th} = 15\Omega$$

Using superposition

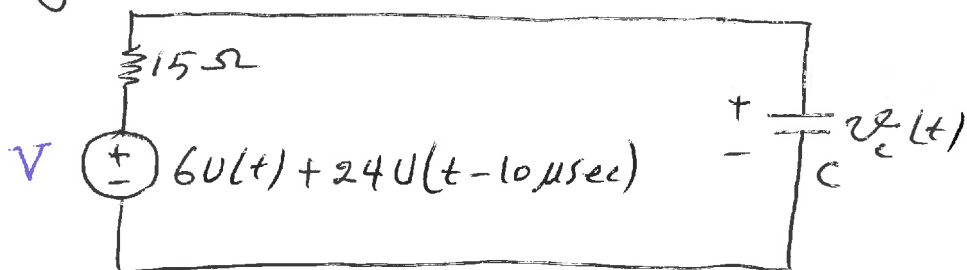

$$v_C(t) = 6(1 - e^{-t/\tau})U(t) + 24(1 - e^{-(t-10\mu\text{sec})/\tau})U(t-10\mu\text{sec})$$

$$\tau = RC = 15\Omega \times 1 \times 10^{-6} = 15\mu\text{sec}$$

b) Find the final value of the voltage on the capacitor

$$V_C(t \rightarrow \infty) = 6 + 24 = 30\text{ V}$$

Another approach

You can also use this method to find $v_c(t)$

$$v_{c_1}(t) = 6(1 - e^{-t/\tau}) u(t) ,$$

then at $t = 10 \mu\text{sec}$, V jumps to 30 V , with capacitor having initial value

$$v_{c_1}(t) = 6(1 - e^{-10 \mu\text{sec}/15 \mu\text{sec}}) = 2.9 \text{ V}$$

$$v_c(t) = V_F + (V_i - V_F) e^{-t/\tau} \quad \text{for } t > 10 \mu\text{sec}$$
$$= 30 + (2.9 - 30) e^{-(t-10 \mu\text{s})/\tau}$$

$$v_c(t) = 30 + (2.9 - 30) e^{-(t-10 \mu\text{s})/15 \mu\text{sec}}$$

$$v_c(t) = 30 - 27.1 e^{-(t-10 \mu\text{s})/15 \mu\text{sec}}$$