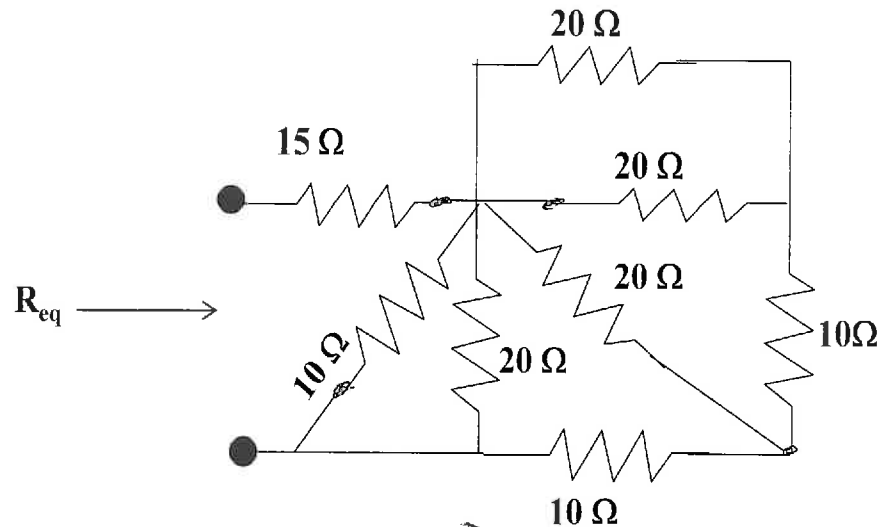


Name :

ID #

Problem # 1(5 Points)

Find R_{eq} by combining the resistors.

$$R_{eq1} = \left\{ \left[(20 \parallel 20) + 10 \right] \parallel 20 + 10 \right\}$$

$$= (10 + 10) \parallel 20 + 10 = 20 \Omega$$


$$R_{eq} = \left[(R_{eq1} \parallel 20) \parallel 10 \right] + 15$$

$$= (20 \parallel 20) \parallel 10 + 15$$

$$= 5 \Omega + 15 \Omega = 20 \Omega$$

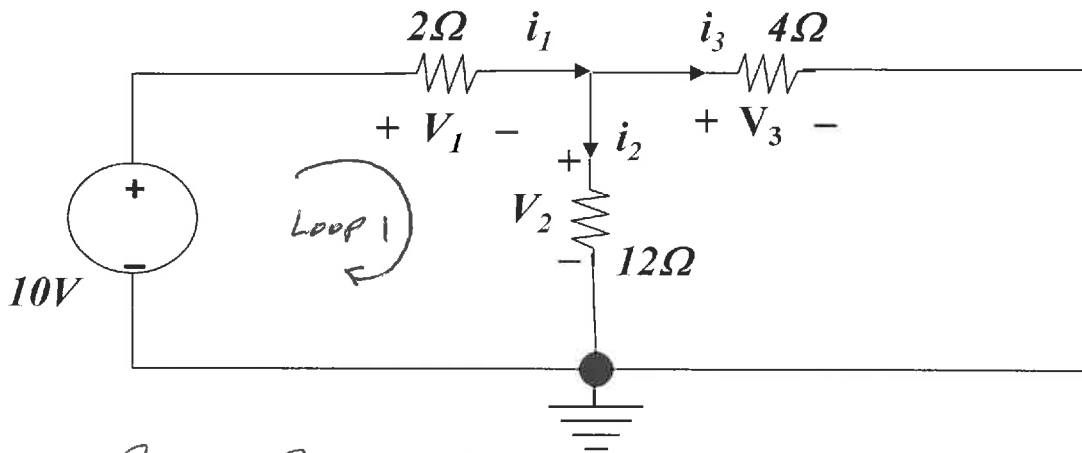Problem # 2

Find all the currents and voltages in this circuit using KVL / KCL and any resistance combinations.



$$R = 4\ \Omega \parallel 12\ \Omega = \frac{48}{16} = 3\ \Omega$$

$$I_1 = \frac{10\text{ V}}{2\ \Omega + 3\ \Omega} = 2\text{ A} \quad \text{Ohms law in } 2\ \Omega \text{ resistor}$$

$$V_1 = 2\ \Omega \times 2\text{ A} = 4\text{ V} \quad \swarrow$$

$$V_1 + V_2 - 10 = 0 \quad \text{in Loop 1}$$

$$V_2 = 10 - 4 = 6\text{ V}, \quad V_3 = V_2 = 6\text{ V}$$

$$I_2 = \frac{6\text{ V}}{12\ \Omega} = 0.5\text{ A}$$

$$I_3 = I_1 - I_2 = 2 - 0.5 = 1.5\text{ A} \quad \text{KCL}$$