

Name: \_\_\_\_\_ **ANSWER KEY** \_\_\_\_\_

**EXAM 2**  
**EECS 215**  
**Introduction to Electronic Circuits**  
**Wednesday, November 16, 2017, 6:00pm-8:00pm**

<b>Lecture Section (circle one):</b>	<b>001 Finelli</b>	<b>002 Lahiji</b>
--------------------------------------	--------------------	-------------------

**This test consists of 6 problems with points as indicated to total 90 points.**

Read through the entire exam before beginning.

**Show all work** (on the pages provided in this booklet) to earn partial credit.

Briefly explain major steps, include units, and write your final answers in the areas provided.

Do not unstaple the pages.

**No credit will be given if no work is shown.**

**Exam Policies**

- No food allowed during exam.
- No books allowed (closed book exam).
- One, 8.5 x 11 inch notes page (TWO SIDED) allowed
- Only scientific calculators allowed (**graphing calculators not permitted**).
- No communication of any kind is allowed. No use of cell phones, computers, or any devices besides calculators. Violation of this will be treated as an honor code violation.
- No credit will be given for this exam without a signed honor pledge.

**Write out the honor pledge and sign below.**

“I have neither given nor received unauthorized aid on this examination, nor have I concealed any violations of the Honor Code”

---

---

---

Signature: \_\_\_\_\_

Do not write in this space

Problem 1: [     ]/15

Problem 4: [     ]/10

Problem 2: [     ]/15

Problem 5: [     ]/15


Problem 3: [     ]/15

Problem 6: [     ]/20

**Total score [     ]/90**

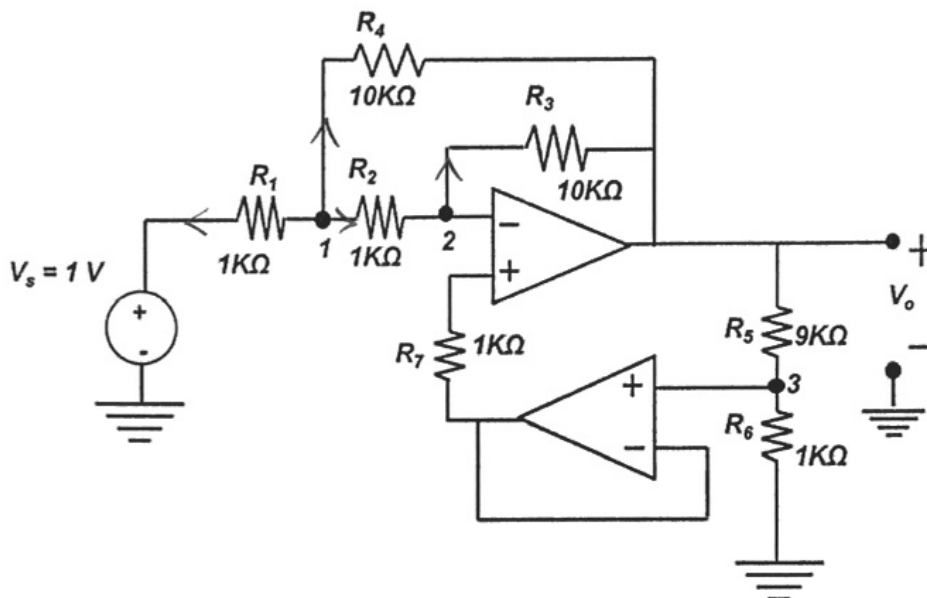Problem 1. (15 points total) Assuming the OpAmp in the circuit is ideal, find the value of the output voltage  $V_o$ . We recommend the following series of steps:

- Apply KCL at node 1
- Apply KCL at node 2
- Apply the voltage divider relationship at node 3
- Determine the relationship between the voltage at nodes 2 and 3
- Combine the equations and solve for  $V_o$



$$V_o = \underline{-5.58V} \quad (15 \text{ points})$$


(a) KCL at node 1:

$$\frac{V_1 - 1}{1k} + \frac{V_1 - V_o}{10k} + \frac{V_1 - V_2}{1k} = 0$$

or  $21V_1 - 10V_2 - V_o = 10 \quad \text{--- (1)}$

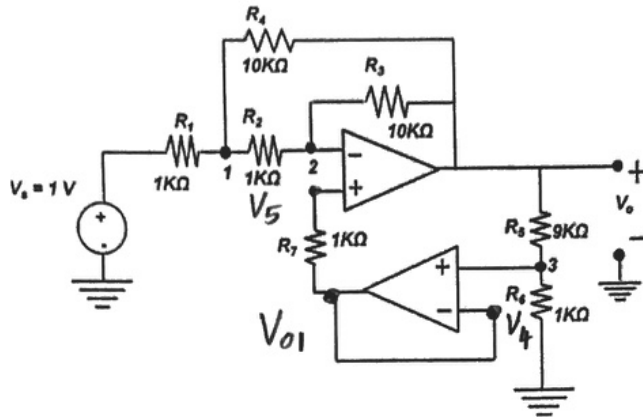(b) KCL at node 2:

$$-\left(\frac{V_1 - V_2}{1k}\right) + \frac{V_2 - V_o}{10k} = 0 \quad \text{or} \quad 10V_1 - 11V_2 + V_o = 0 \quad \text{--- (2)}$$



(Circuit redrawn for your convenience)

(c) Voltage Divider at 3:

$$V_3 = \frac{V_0}{10}$$

$$\therefore V_{01} = V_4 = V_3 = \frac{V_0}{10} \quad \text{--- (3)}$$

(d)  $\therefore$  Current through 1k resistor between  $V_5$  &  $V_{01} = 0A$ ,

$$\therefore V_5 = V_{01} = \frac{V_0}{10} \quad (\text{From (3)})$$

$$\therefore V_2 = V_5 = \frac{V_0}{10} = V_3 \quad \text{--- (4)}$$

$$\therefore V_5 = V_3$$

(e) Combining (1), (2) + (4)

Linear eq<sup>n</sup>:

$$\left. \begin{array}{l} \textcircled{1} \quad 21V_1 - 2V_0 = 10 \\ \textcircled{2} \quad 100V_1 - V_0 = 0 \end{array} \right\}$$

$$V_0 = -5.58V$$

Problem 2. (15 points total) A 5 mF capacitor is initially uncharged, and the current flowing through the capacitor is defined as:

$$i_c(t) = \begin{cases} 0, & t \leq 0 \text{ sec} \\ 20t \text{ A}, & 0 \leq t \leq 0.025 \text{ sec} \\ 0.5 \text{ A}, & t \geq 0.025 \text{ sec} \end{cases}$$

Determine the voltage  $v_c(t)$  for  $t \geq 0$  and write your answer here:

$$v_c(t) = \begin{cases} \frac{2 \times 10^3 t^2}{2} \text{ V} & (7 \text{ points}), \quad 0 \leq t \leq 0.025 \text{ sec} \\ 100t - 1.25 \text{ V} & (8 \text{ points}), \quad t \geq 0.025 \text{ sec} \end{cases}$$

$$V_c(t) = \frac{1}{C} \int_{t_0}^t i_c(t) dt + V_c(t_0)$$


For:  $0 \leq t \leq 0.025 \text{ s}$

$$\begin{aligned} V_c(t) &= \frac{1}{5 \times 10^{-3}} \int_0^t 20t \cdot dt + \overset{0 \text{ V}}{\cancel{V_c(0)}} \\ &= 2 \times 10^3 t^2 \text{ V} \end{aligned}$$

For  $t \geq 0.025 \text{ s}$

$$\begin{aligned} V_c(t) &= \frac{1}{5 \times 10^{-3}} \int_{0.025}^t 0.5 dt + V_c(0.025) \\ &= 100 (t - 0.025) + (2000)(0.025)^2 \\ &= 100t - 1.25 \text{ V} \end{aligned}$$

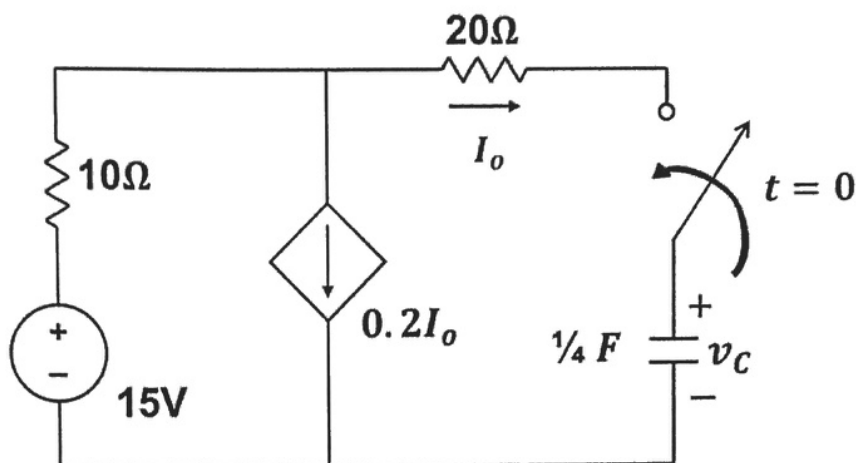Problem 3. (15 points) The switch in the circuit below has been **open** for a very long time, and it **closes** at  $t = 0$ . Find an expression for  $v_C(t)$ ,  $t \geq 0$



$$v_C(t) = 15 - 15e^{-t/8} \text{ V} \quad (15 \text{ points})$$

(\*)

At  $t = 0$

$$v_C(0^-) = 0 \text{ V} = v_C(0^+)$$

(\*)


$t \rightarrow \infty$ , capacitor acts as an open ckt:


$$I_o = 0 \text{ A}$$

$\therefore$  Currents in all branches = 0 A

Applying KVL in outermost loop:

$$15 \text{ V} = V_C(\infty)$$

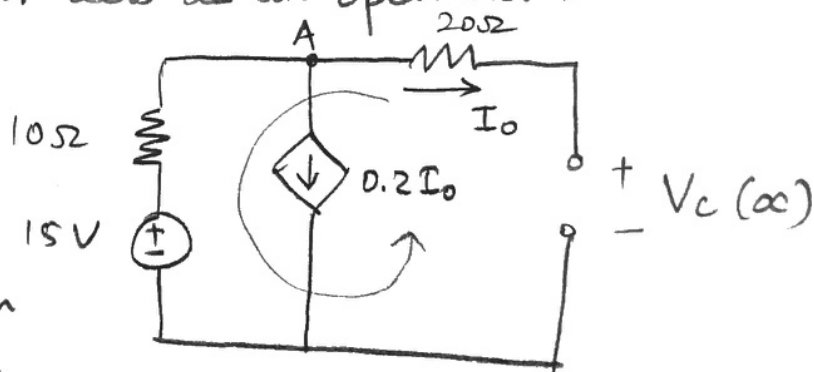

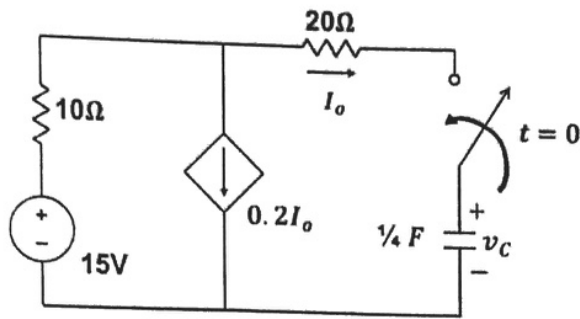


(Circuit redrawn for your convenience)

\* Finding  $z = R_{Th}C$

$$I_o = \frac{V_A - 1V}{20} \quad \text{--- (1)}$$

KCL at node A:

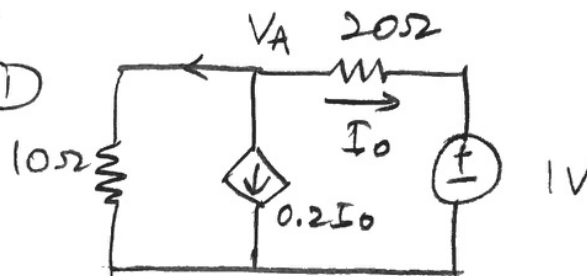

$$\frac{V_A}{10} + 0.2 \left( \frac{V_A - 1V}{20} \right) + \frac{V_A - 1V}{20} = 0$$

(Using (1))

$$\therefore V_A = 0.375$$

$$I_o = -0.0312 A$$

$$\therefore R_{Th} = \frac{1V}{-I_o}$$


$$= 32 \Omega$$

$$\therefore z = 8s$$

\*  $v_c(t) = v_c(\infty) + [v_c(0) - v_c(\infty)] e^{-t/z}$

$$= 15 - 15 e^{-t/8} \text{ V}$$

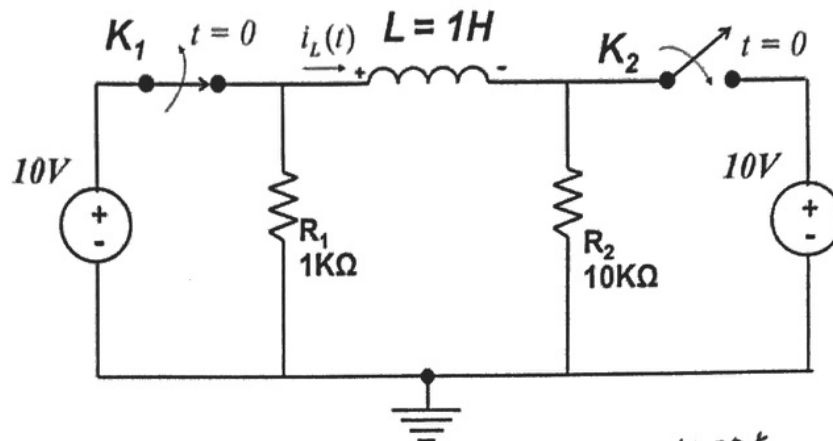Problem 4. (10 points). Switches  $K_1$  and  $K_2$  after being in position shown in the circuit for a long time, are moved to the new position at  $t = 0$ . With the given parameters in this circuit, find  $i_L(t)$ ,  $t > 0$



$$i_L(t) = -10 + 11e^{-1000t} \quad (10 \text{ points})$$

(\*)

$$t = 0^-$$

$$i_L(0^-) = \frac{10V}{10k} = 1mA$$

$$\therefore i_L(0^+) = 1mA$$

(\*)

$$t \rightarrow \infty, i_L(\infty) = -\frac{10V}{1k} = -10mA$$


(\*)

$$\tau = \frac{L}{R_{Th}}$$

$$\therefore R_{Th} = 1k\Omega$$

( $\because$  10k resistor is shorted)

$$\therefore \tau = 1/1k = 1ms$$

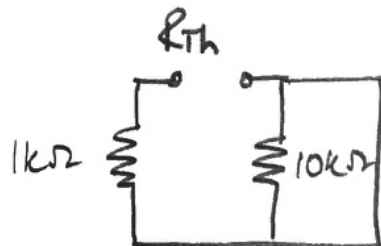

(\*)

$$i_L(t) = i_L(\infty) + [i_L(0^+) - i_L(\infty)]e^{-t/\tau}$$

$$= -10 + 11e^{-1000t} \quad mA$$

Problem 5. (15 points total) For the circuit below, the switch has been in position A for a long time, then it moves to position B at  $t = 0$ . Determine the initial and final values as listed below (don't forget to include units):

$$i_L(0^+) = \underline{-0.5 \text{ A}} \quad (2 \text{ points})$$


$$v_C(0^+) = \underline{-10 \text{ V}} \quad (2 \text{ points})$$

$$i_L'(0^+) = \underline{0} \quad (3.5 \text{ points})$$

$$v_C'(0^+) = \underline{10 \text{ V/s}} \quad (3.5 \text{ points})$$

$$i_L(\infty) = \underline{0.1667 \text{ A}} \quad (2 \text{ points})$$
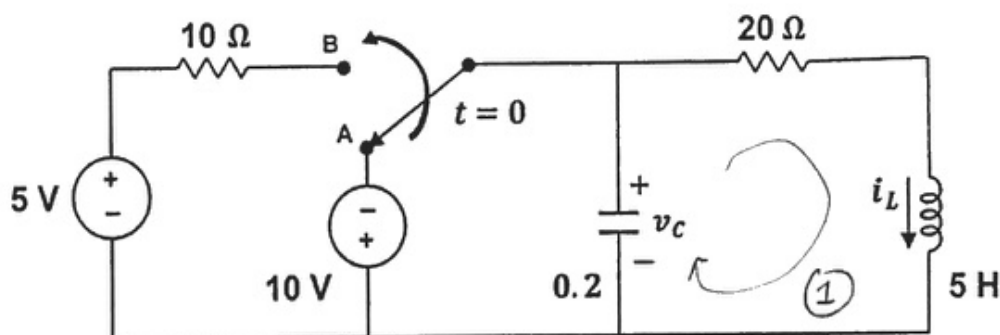
$$v_C(\infty) = \underline{3.33 \text{ V}} \quad (2 \text{ points})$$



$$(a) \quad i_L(0^-) = \frac{-10}{20} = -0.5 \text{ A} = i_L(0^+)$$

$$(b) \quad v_C(0^-) = -10 \text{ V} = v_C(0^+)$$

$$(c) \quad i_L'(0^+) = \frac{v_C(0^+)}{L}$$


Applying KVL around (1):

$$-v_C(0^+) + 20 i_L(0^+) + v_L(0^+) = 0$$

$$\therefore v_L(0^+) = 0 \text{ V}$$

$$\therefore i_L'(0^+) = 0 \text{ A/s}$$



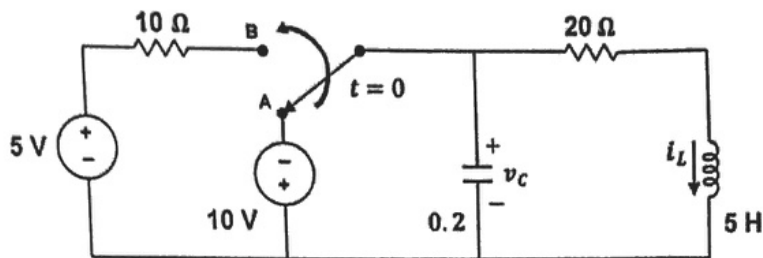

(Circuit redrawn here)

(d)  $V_B = V_C(0^+)$

KCL at B:


$$\frac{V_C(0^+) - 5}{10} + i_C(0^+) = 0$$

$$+ i_L(0^+) = 0$$

$$\therefore \frac{15}{10} + 0.5 = i_C(0^+)$$

$$\therefore i_C(0^+) = 2A$$


$$\therefore V'_C(0^+) = 10V/s$$

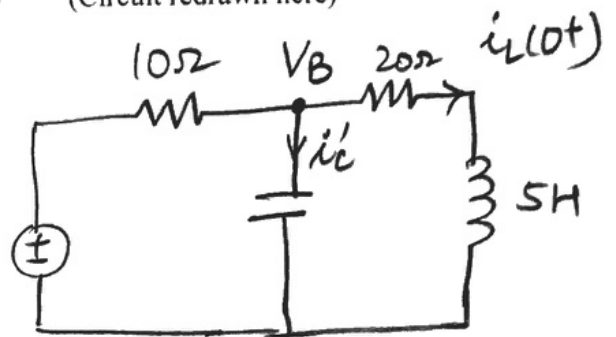

(e)  $i_L(\infty) = \frac{5}{10+20} = 0.1667A$

(f)  $V_C(\infty) = \frac{20}{30} \times 5V = 3.33V.$

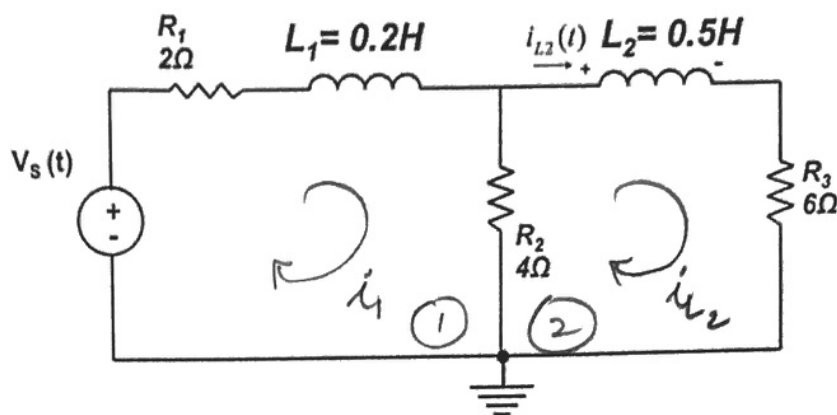Problem 6. (20 points total). In the circuit below,  $V_s(t) = 10 u(t)$  V.



- (a) (10 points) Using **mesh analysis**, derive a second order differential equation that describes the current  $i_{L2}(t)$  for  $t > 0$ . Write your answer by filling in the blanks below:

$$\frac{d^2 i_{L2}(t)}{dt^2} + \underline{50} \frac{di_{L2}(t)}{dt} + \underline{440} i_{L2}(t) = \underline{400} \quad (10 \text{ points})$$

- (b) (10 points) Suppose the answer for part (a) is as follows (note, this is *NOT* the correct answer):

$$\frac{d^2 i_{L2}(t)}{dt^2} + 10 \frac{di_{L2}(t)}{dt} + 20 i_{L2}(t) = 15 A$$

Solve the equation to find  $i_{L2}(t)$ ,  $t \geq 0$

$$i_{L2}(t) = \underline{\hspace{2cm}} \quad (10 \text{ points})$$

(a) For  $t > 0$  KVL in loop 1:

$$-10 + 2i_1 + 0.2 \frac{di_1}{dt} + 4(i_1 - i_2) = 0$$

$$6i_1 + 0.2 \frac{di_1}{dt} - 4i_2 - 10 = 0 \quad \text{--- (1)}$$

KVL in loop 2:


$$-4(i_1 - i_2) + 0.5 \frac{di_2}{dt} + 6i_2 = 0$$

$$\therefore i_1 = \frac{1}{4} [10 i_2 + 0.5 \frac{d}{dt} i_2(t)] - \textcircled{2}$$

Substitute  $\textcircled{2}$  in  $\textcircled{1}$  :

$$0.025 \frac{d^2 i_2(t)}{dt^2} + 1.25 \frac{d}{dt} i_2(t) + 11 i_2(t) - 10 = 0$$
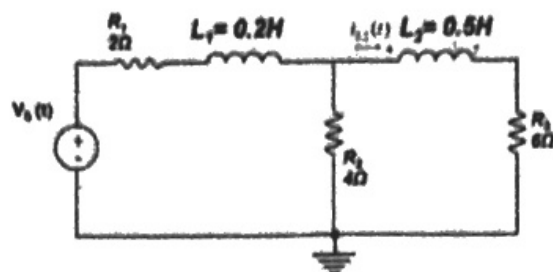
$$\therefore \frac{d^2 i_2(t)}{dt^2} + 50 \frac{d}{dt} i_2(t) + 440 i_2(t) = 400$$



(Circuit redrawn for your convenience)

Q6(b). Need  $i_2(0^+)$  and  $\left. \frac{d}{dt} i_2(t) \right|_{t=0} = \frac{v_{L2}(t)}{L}$


$t = 0^-$

$$\therefore i_2(0^+) = i_2(0^-) = 0A$$

$\therefore$  No current flows

through the circuit at  $t = 0^+$ ,
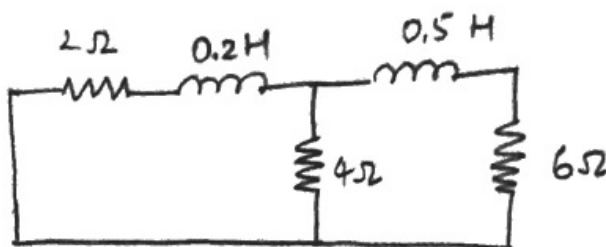
$$v_{L2}(0^+) = 0V \Rightarrow \frac{d}{dt} i_2(t) = 0 A/s$$



$$\text{eq}^n : \frac{d^2}{dt^2} i_2(t) + 10 \frac{d}{dt} i_2(t) + 20 i_2(t) = 15$$

$$\text{roots : } -2.76, -7.76$$

$$\text{natural response : } A_1 e^{-2.76t} + A_2 e^{-7.76t} = i_2(t)$$

$$\text{steady state response } i_2(t) = \frac{15}{20} = 0.75$$

Complete Sol<sup>n</sup> :

$$i_2(t) = A_1 e^{-2.76t} + A_2 e^{-7.76t} + 0.75$$

Using Initial Cond<sup>n</sup> :

$$i_{L2}(0) = A_1 + A_2 + 0.75 = 0$$

$$i'_{L2}(0) = -2.76 A_1 - 7.76 A_2 = 0$$

$$\therefore A_1 = -1.164 \quad A_2 = 0.414$$

$$\therefore i_{L2}(t) = -1.164 e^{-2.76t} + 0.414 e^{-7.76t} + 0.75 \text{ A}$$