

Name: _____

EXAM 2: EECS 215
Introduction to Electronic Circuits
Wednesday, March 22, 2017. 6:00pm-8:00pm

Lecture Section (circle 1):	001 Finelli	002 Phillips
------------------------------------	--------------------	---------------------

This test consists of five problems with points as indicated to total 60 points.

Read through the entire exam before beginning.

Show all work (on the pages provided in this booklet) to earn partial credit.

Briefly explain major steps, include units, and write your final answers in the areas provided.

Do not unstaple the pages.

No credit will be given if no work is shown.

Exam Policies

- No food allowed during exam.
- No books allowed (closed book exam).
- One, 8.5 x 11 inch notes page (TWO SIDED) allowed
Note the page of equations at the back of this exam
- Only scientific calculators allowed (**graphing calculators not permitted**).
- No communication of any kind is allowed. No use of cell phones, computers, or any devices besides calculators. Violation of this will be treated as an honor code violation.
- No credit will be given for this exam without a signed honor pledge.

Write out the honor pledge and sign below.

“I have neither given nor received unauthorized aid on this examination, nor have I concealed any violations of the Honor Code”

Signature: _____

Do not write in this space

Problem 1: []/12

Problem 4: []/12


Problem 2: []/12

Problem 5: []/12

Problem 3: []/12

Total score []/60

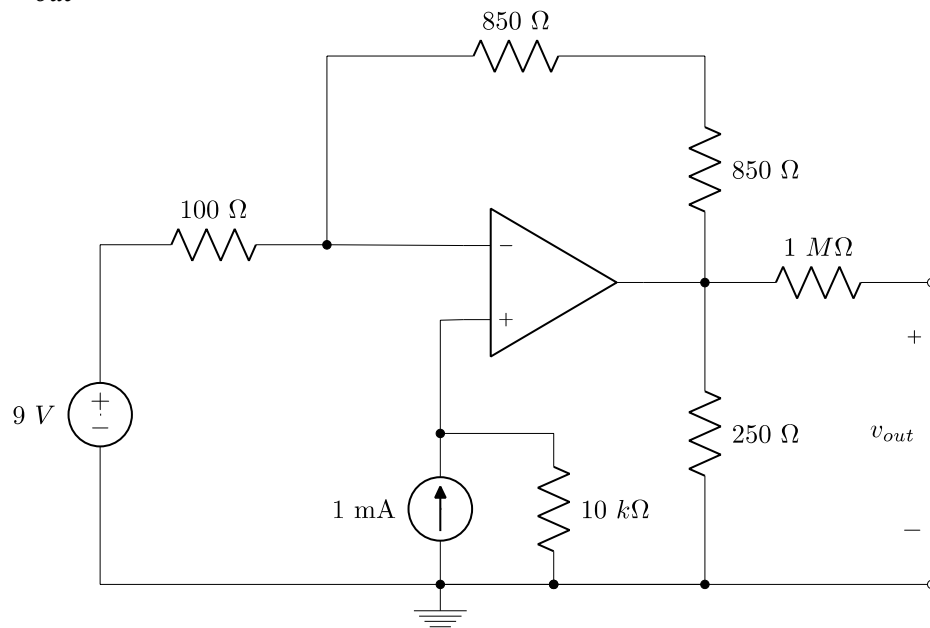1. Calculate v_{out} in the circuit below




Write your answer here:

$v_{out} =$ _____

Problem 1 score: []/12

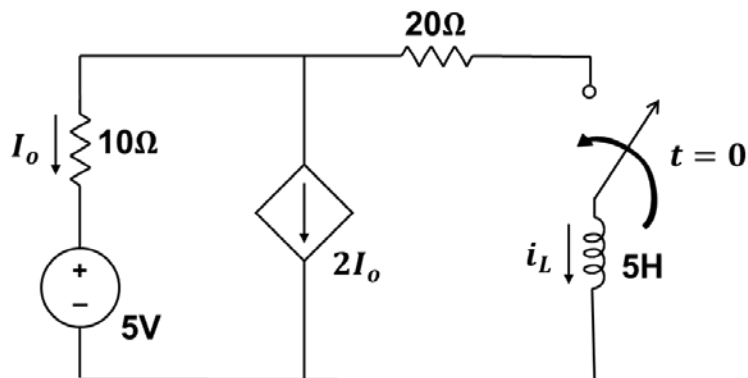2. The switch in the circuit below has been open for a very long time, and it closes at $t = 0$ seconds. Solve completely for $i_L(t)$, $t \geq 0$.




Write your answer here:

$i_L(t) =$ _____

Problem 2 score: []/12

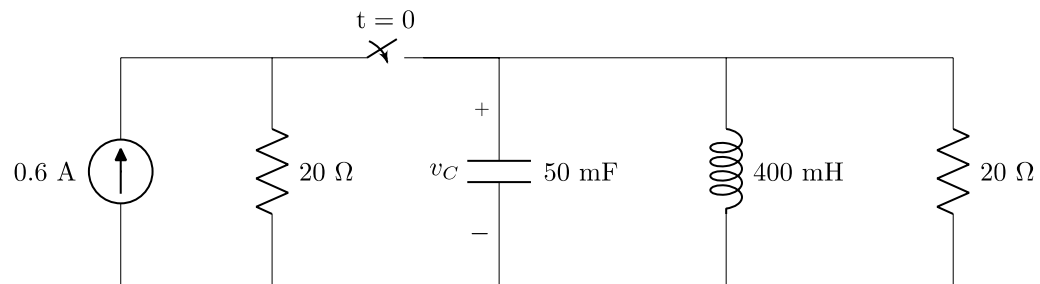3. The circuit below had the switch open for a very long time before it is closed at time $t = 0$. Find the voltage across the capacitor $v_C(t)$ for $t \geq 0$.




Write your answer here:

$v_C(t) =$ _____

Problem 3 score: []/12

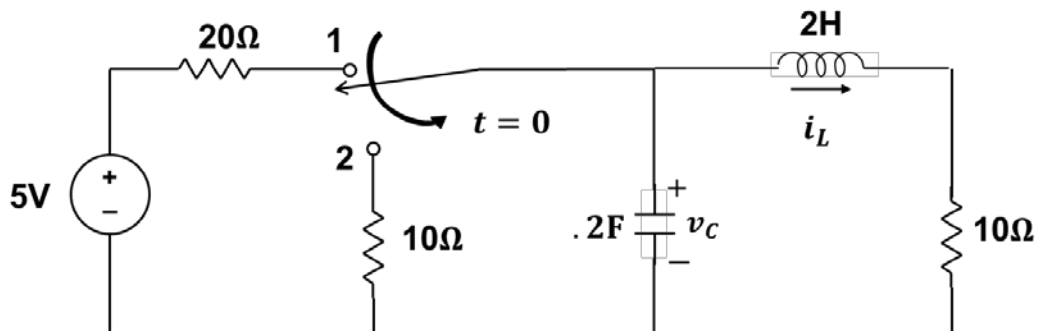4. The switch in the circuit below has been in position (1) for a very long time. At $t = 0$ seconds, it moves to position (2). Determine:
- $i_L(0^+)$ and $v_C(0^+)$
 - $i_L'(0^+)$ and $v_C'(0^+)$



Write your answer here:

$$i_L(0^+) = \underline{\hspace{2cm}}$$

$$v_C(0^+) = \underline{\hspace{2cm}}$$


$$i_L'(0^+) = \underline{\hspace{2cm}}$$

$$v_C'(0^+) = \underline{\hspace{2cm}}$$

Problem 4 score: []/12

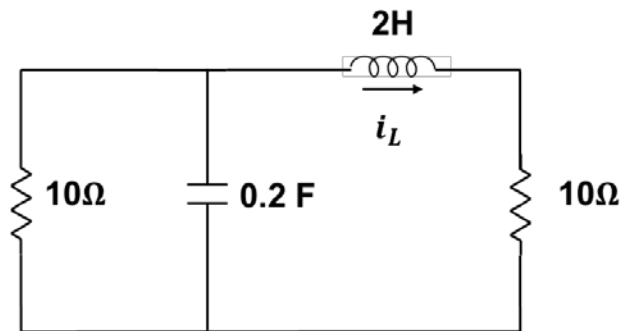5. For the circuit below, determine the second order differential equation for $i_L(t)$. Do not solve the equation. Rather, compute the constants K_1 and K_2 for the equation:

$$\frac{d^2 i_L(t)}{dt^2} + K_1 \frac{di_L(t)}{dt} + K_2 i_L(t) = 0$$



Write your answer here:

$K_1 =$ _____

$K_2 =$ _____

Problem 5 score: []/12

Capacitors and Inductors

$$i = C \frac{dv}{dt} \quad v = L \frac{di}{dt}$$

First Order Circuits

Step Response:

$$v(t) = v(\infty) + [v(0) - v(\infty)]e^{-\frac{t}{\tau}}$$

$$i(t) = i(\infty) + [i(0) - i(\infty)]e^{-\frac{t}{\tau}}$$

$$\tau = RC \text{ (RC circuit)}$$

$$\tau = L/R \text{ (RL circuit)}$$

Second Order Circuits

$$\frac{d^2x(t)}{dt^2} + 2\alpha \frac{dx(t)}{dt} + \omega_0^2 x(t) = f(t)$$

$$s_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2}$$

$$\text{Series RLC: } \alpha = R/(2L) \quad \omega_0 = 1/\sqrt{LC}$$

$$\text{Parallel RLC: } \alpha = 1/(2RC) \quad \omega_0 = 1/\sqrt{LC}$$

Over Damped ($\alpha > \omega_0$):

$$x(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t} + x(\infty)$$

Critically Damped ($\alpha = \omega_0$):

$$x(t) = (A_1 t + A_2) e^{-\alpha t} + x(\infty)$$

Under Damped ($\alpha < \omega_0$):

$$x(t) = e^{-\alpha t} (B_1 \cos \omega_d t + B_2 \sin \omega_d t) + x(\infty)$$

$$\omega_d = \sqrt{\omega_0^2 - \alpha^2}$$