

Laboratory Six — Filters

Rishabh Shah
4655 4192

Partner: Matthew Remillard

December 8, 2017

Pre-Lab

First Order Filters

Low Pass Filter

$$f_c = \frac{1}{2\pi RC} = 33.86Hz$$

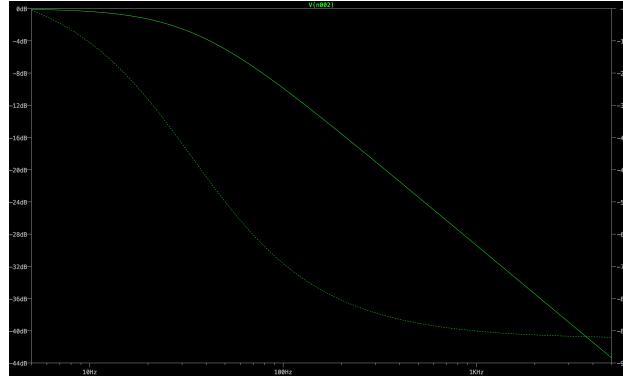


Figure 1: First order low pass filter, with cutoff frequency of $\sim 33Hz$

High Pass Filter

$$f_c = \frac{1}{2\pi RC} = 33.86Hz$$

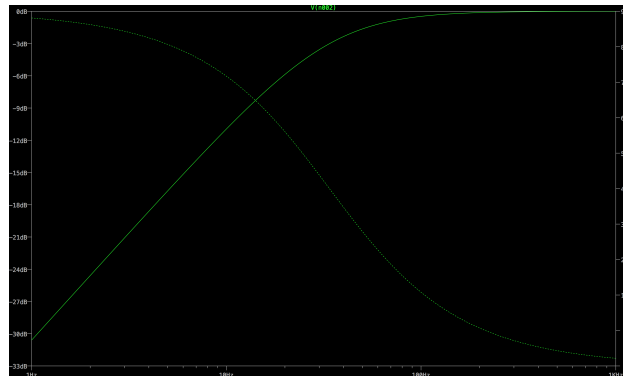


Figure 2: First order high pass filter, with cutoff frequency of $\sim 33Hz$

Second Order Filters

Low Pass Filter

$$f_{MaxGainTheoretical} = 734Hz$$

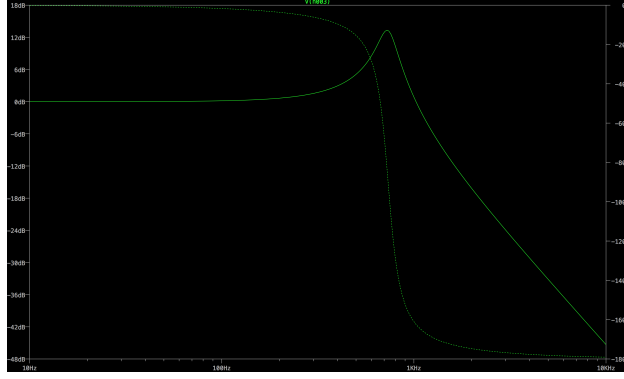


Figure 3: Second order low pass filter, with maximum gain frequency of $\sim 740Hz$

High Pass Filter

$$f_{MaxGainTheoretical} = 734Hz$$

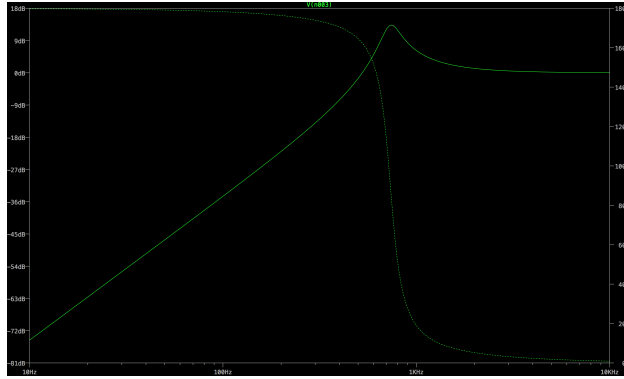


Figure 4: Second order high pass filter, with maximum gain frequency of $\sim 740Hz$

Band Pass Filter

$$f_{MaxGainTheoretical} = 734Hz$$

$$f_{Bandwidth} = 1600Hz$$

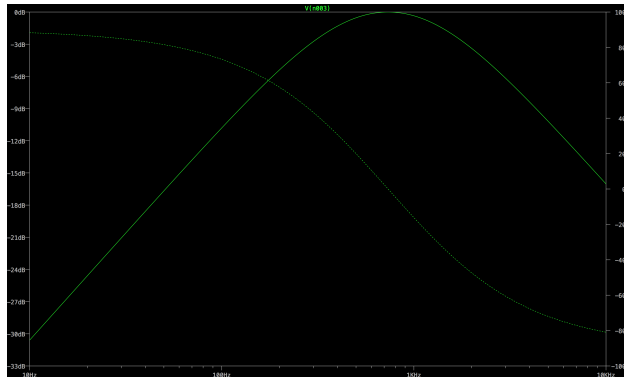


Figure 5: Second order band pass filter, with maximum gain frequency of $\sim 735Hz$

Band Reject Filter

$$f_{MaxGainTheoretical} = 734Hz$$

$$f_{Bandwidth} = 1591Hz$$

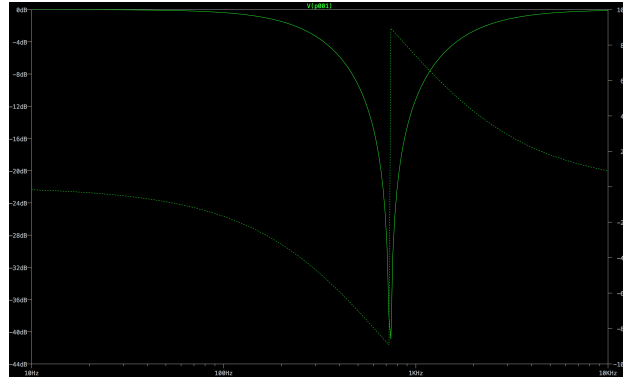


Figure 6: Second order band reject filter, with maximum gain frequency of $\sim 735Hz$, and bandwidth of $\sim 1589Hz$

Active Filters

Low Pass Filter

$$f_c = 32Hz$$

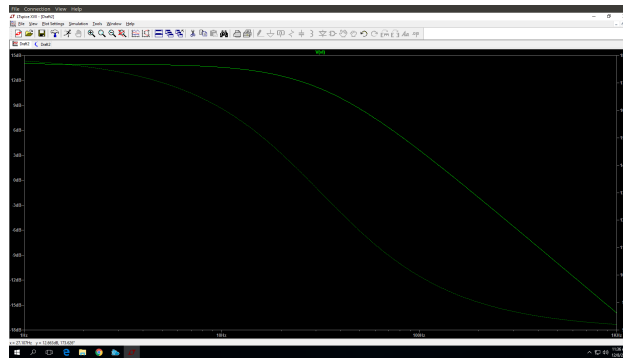


Figure 7: Active low pass filter

Lab Data

First Order Low Pass Filter

$$f_c = 33.59Hz$$

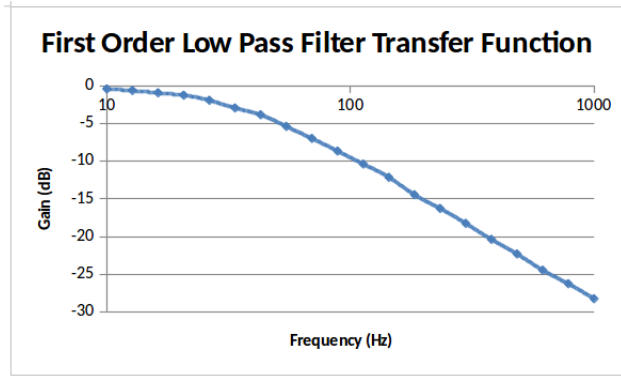


Figure 8: First order low pass filter Bode Plot

First Order High Pass Filter

$$f_c = 33.59Hz$$

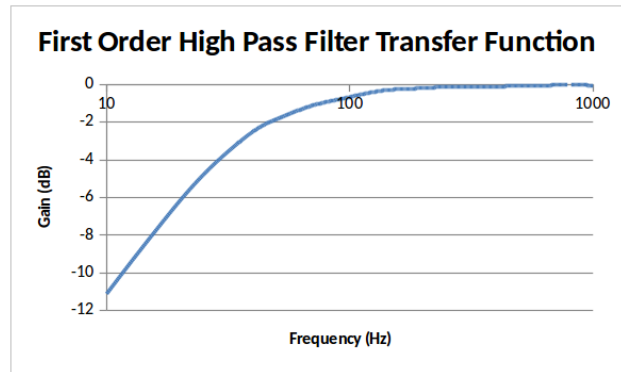


Figure 9: First order high pass filter Bode Plot

Second Order Low Pass Filter

$$f_{MaxGainMeasured} = 545.6Hz$$

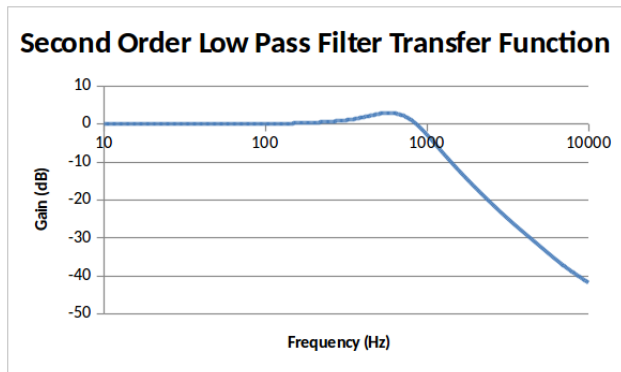


Figure 10: Second order low pass filter Bode Plot

Second Order High Pass Filter

$$f_{MaxGainMeasured} = 784.2Hz$$

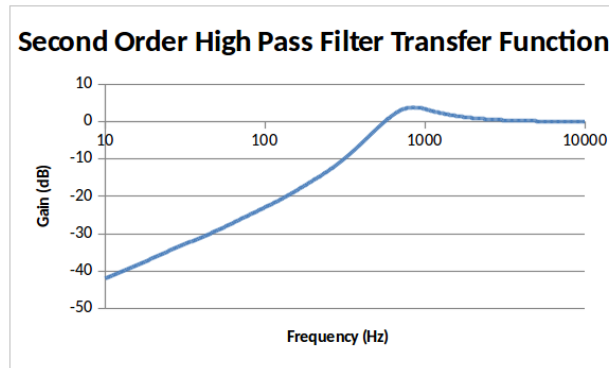


Figure 11: Second order high pass filter Bode Plot

Second Order Bandpass Filter

$$f_{MaxGainMeasured} = 701.7Hz$$

$$f_{Bandwidth} = 1012.6Hz$$

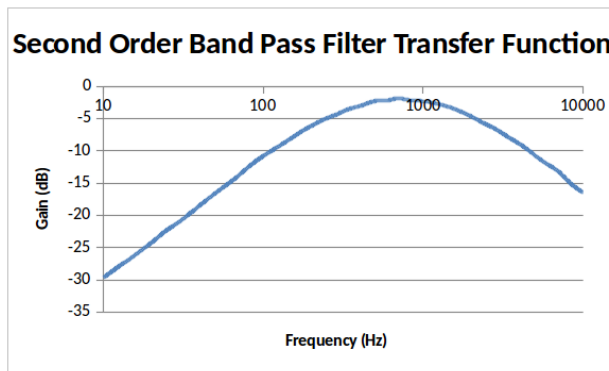


Figure 12: Second order bandpass filter Bode Plot

Second Order Band Reject Filter

$$f_{MinGainMeasured} = 701.7Hz$$

$$f_{Bandwidth} = 1788.5Hz$$

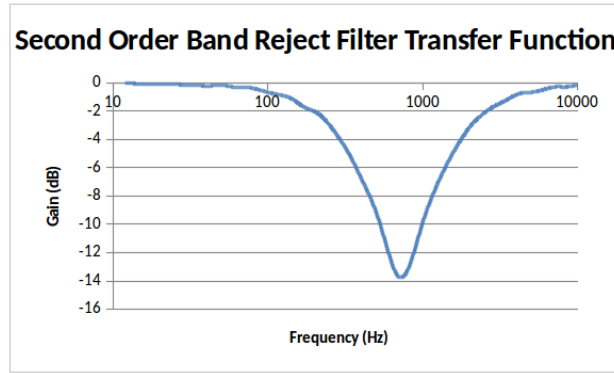


Figure 13: Second order band reject filter Bode Plot

Second Order Band Reject Filter with Different Resistor

$$f_{MinGainMeasured} = 701.7Hz$$

$$f_{Bandwidth} = 9965.4Hz$$

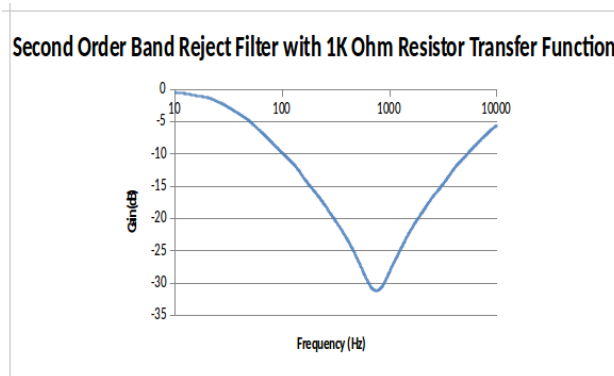


Figure 14: Second order band reject filter with 1k Ω Bode Plot

Active Filters

$$f_c = 33.59Hz$$

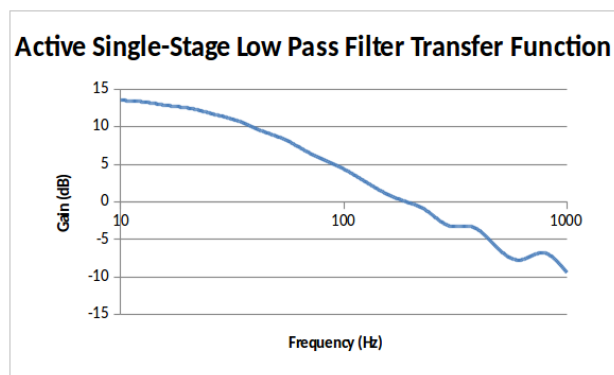


Figure 15: Single stage active filter Bode Plot

Active Filters with More Stages

$$f_c = 143.8Hz$$

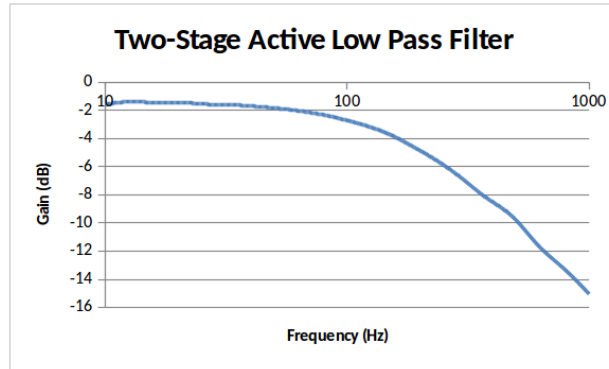


Figure 16: Two stage active filter Bode Plot

Post-Lab

First Order Low Pass Filter

$$\text{PercentageError} = \frac{|\text{measured} - \text{calculated}|}{\text{calculated}} = \frac{|33.59 - 33.86|}{33.86} = 0.80\%$$

The difference between our calculated and measured cutoff frequency is extremely small.

First Order High Pass Filter

$$\text{PercentageError} = \frac{|\text{measured} - \text{calculated}|}{\text{calculated}} = \frac{|33.59 - 33.86|}{33.86} = 0.80\%$$

The difference between our calculated and measured cutoff frequency is extremely small.

Second Order Low Pass Filter

$$\text{PercentageError} = \frac{|\text{measured} - \text{calculated}|}{\text{calculated}} = \frac{|545.6 - 734|}{734} = 25.67\%$$

The difference between our calculated and measured cutoff frequency is fairly high. This is most likely due to inaccurate use of the cursors in both LTSpice and the lab software.

The gain of the second order low pass filter decreases at a faster rate than the first order low pass filter, however, the second order low pass filter has a larger overshoot than the first order low pass filter. The first order low pass filter is better for uses where a low overshoot is needed, while the second order low pass filter is better for uses where a large rate of decrease is needed, and an overshoot is allowable.

Second Order High Pass Filter

$$\text{PercentageError} = \frac{|\text{measured} - \text{calculated}|}{\text{calculated}} = \frac{|784.2 - 734|}{734} = 6.84\%$$

The difference between our calculated and measured cutoff frequency is fairly low.

Both the theoretical and experimental Bode plots show similar slopes within the specified stop-band.

The gain of the second order high pass filter decreases at a faster rate than the first order high pass filter, however, the second order high pass filter has a larger overshoot than the first order high pass filter. The first order high pass filter is better for uses where a low overshoot is needed, while the second order high pass filter is better for uses where a large rate of decrease is needed, and an overshoot is allowable.

Increasing the resistance will result in a higher bandwidth, while decreasing the resistance will result in a lower bandwidth. It will have no effect on the frequency of maximum gain.

Second Order Bandpass Filter

$$PercentageError = \frac{|measured - calculated|}{calculated} = \frac{|701.7 - 734|}{734} = 4.40\%$$

$$PercentageError = \frac{|measured - calculated|}{calculated} = \frac{|1012.6 - 1600|}{1600} = 0.37\%$$

The difference between our calculated and measured maximum gain frequency is fairly low. Additionally, the difference between our calculated and measured bandwidth is fairly low.

Second Order Band Reject Filter

$$PercentageError = \frac{|measured - calculated|}{calculated} = \frac{|701.7 - 734|}{734} = 4.40\%$$

$$PercentageError = \frac{|measured - calculated|}{calculated} = \frac{|1788.5 - 1591|}{1591} = 12.41\%$$

The difference between our calculated and measured minimum gain frequency is fairly low. Additionally, the difference between our calculated and measured bandwidth is fairly low.

Second Order Band Reject Filter with Different Resistor

$$f_{MinGain} = 734Hz$$

$$Bandwidth = 15900Hz$$

$$PercentageError = \frac{|measured - calculated|}{calculated} = \frac{|701.7 - 734|}{734} = 4.40\%$$

$$PercentageError = \frac{|measured - calculated|}{calculated} = \frac{|9965.4 - 15900|}{15900} = 37.32\%$$

The difference between our calculated and measured minimum gain frequency is fairly low. Additionally, the difference between our calculated and measured bandwidth is fairly high. This is most likely due to inaccurate use of the cursors in both LTSpice and the lab software.

Active Filters

$$f_c = 33.86Hz$$

$$PercentageError = \frac{|measured - calculated|}{calculated} = \frac{|33.59 - 33.86|}{33.86} = 0.80\%$$

The difference between our calculated and measured cutoff frequency is extremely small.

The active filter has a similar rate of decrease in gain as the first order low pass filter, but has a lower rate of decrease in gain as the second order low pass filter. Additionally, it has a positive gain, while both the first and second order low pass filters begin at a gain very close to zero. The active circuit allows for positive gain, but dictates a second power supply. Additionally, it does not have any overshoot.

Active Filters with More Stages

The two stage active filter has a similar rate of decrease in gain as the first order low pass filter, but has a lower rate of decrease in gain as the second order low pass filter. The gain begins at a negative number, and the cutoff of the filter is lower than the single stage active filter. The two stage filter has the same disadvantages as a single stage filter. However, it would excel in areas which require low frequencies and low overshoot.