

Problem 1 (20 points)

Assuming the op-amps are ideal, determine v_{out}/v_{in} .

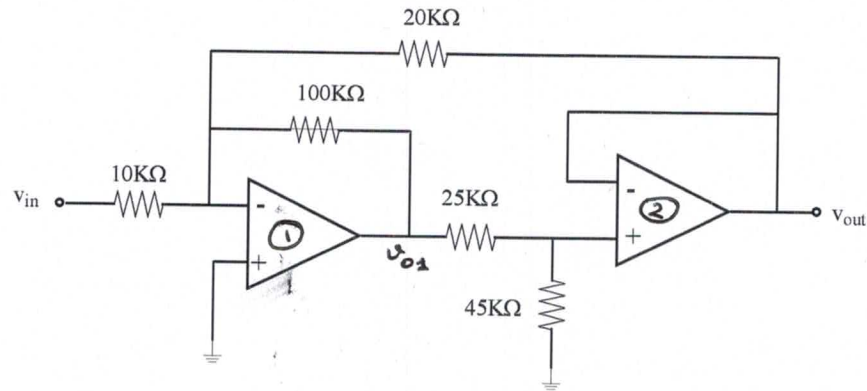


Figure 1: Circuit for Problem 1.

Write your answer here:

$$v_{out}/v_{in} = \underline{-\frac{90}{59} = -1.5254}$$

$$v_{out} = v_{n2} = v_{p2} = \frac{45k}{45k+25k} \times v_{o1}$$

$$\Rightarrow v_{o1} = \frac{14}{9} v_{out}$$

$$v_{p1} = v_{n1} = 0$$

KCL at ① negative terminal :

$$\frac{v_{in}}{10k} + \frac{v_{o1}}{100k} + \frac{v_{out}}{20k} = 0$$

$$\Rightarrow \frac{v_{in}}{10k} + \frac{14}{9} \frac{v_{out}}{100k} + \frac{v_{out}}{20k} = 0$$

$$\Rightarrow v_{out} = - \frac{1}{\frac{14}{9} \times \frac{1}{100k} + \frac{1}{20k}} \times \frac{1}{10k} \times v_{in}$$

$$= - \frac{1}{\frac{14}{90} + \frac{1}{2}} \times v_{in}$$

$$= - \frac{90}{59} v_{in} = -1.5254 v_{in}$$

Problem 2 (10 points)

1. Determine C_{eq} in terms of C_1 , C_2 and C_3 . Express your answer as the ratio of standard polynomials of C_1 , C_2 and C_3 , i.e. $C_{eq} = \frac{\text{num}(C_1, C_2, C_3)}{\text{den}(C_1, C_2, C_3)}$.
2. Determine L_{eq} in terms of L_1 , L_2 and L_3 . Express your answer as the ratio of standard polynomials of L_1 , L_2 and L_3 , i.e. $L_{eq} = \frac{\text{num}(L_1, L_2, L_3)}{\text{den}(L_1, L_2, L_3)}$.

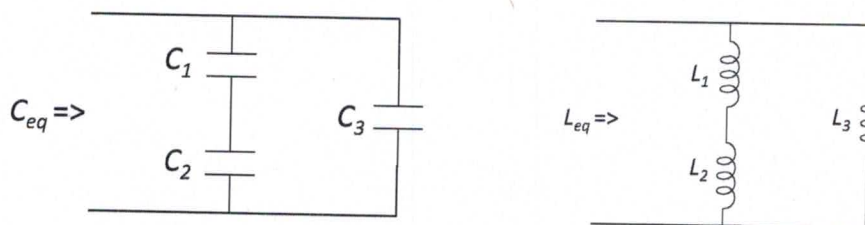


Figure 2: Circuits for Problem 2.

Write your answers here:

$$C_{eq} = \frac{C_1 C_2 + C_1 C_3 + C_2 C_3}{C_1 + C_2}$$

$$L_{eq} = \frac{L_1 L_2 + L_2 L_3}{L_1 + L_2 + L_3}$$

$$C_{eq} = \frac{1}{\frac{1}{C_1} + \frac{1}{C_2}} + C_3$$

$$= \frac{C_1 C_2}{C_1 + C_2} + C_3$$

$$= \frac{C_1 C_2 + C_1 C_3 + C_2 C_3}{C_1 + C_2}$$

$$L_{eq} = (L_1 + L_2) \parallel L_3$$

$$= \frac{(L_1 + L_2) L_3}{L_1 + L_2 + L_3}$$

$$= \frac{L_1 L_3 + L_2 L_3}{L_1 + L_2 + L_3}$$

Problem 3 (20 points)

For the given circuit, determine $v_c(t)$ for $t \geq 0$. (Note that the left-hand $3A$ source has been on from $t = -\infty$ whereas the right-hand source turns on at $t = 0$.)


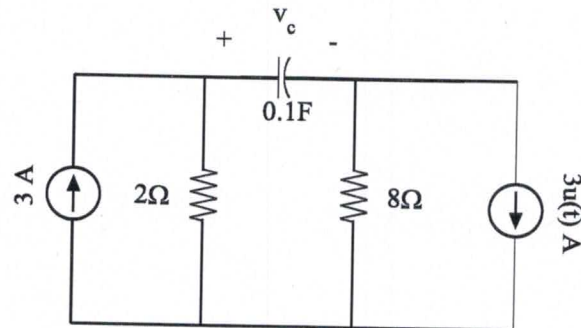


Figure 3: Circuit for Problem 3.


Write your answer here:

$$v_c(t) = \underline{30 - 24e^{-t} \text{ volts}} \quad (\text{for } t \geq 0)$$

Source transformation gives:

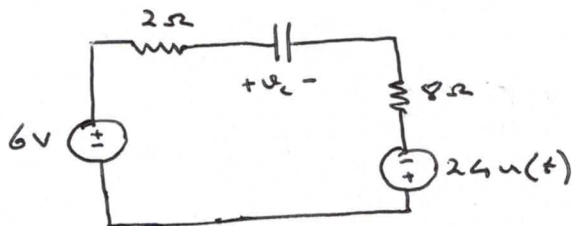

Thevenin equivalent \Rightarrow

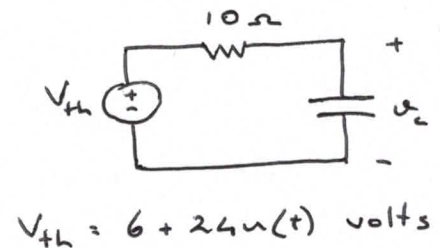

$$v_c(0^-) = 6 \text{ volts}$$

$$v_{cl} = 30 \text{ volts}, \quad v_{cu} = Ae^{-t/\tau}$$

$$\tau = RC = 10 \times 0.1 = 1 \text{ sec}$$

$$\Rightarrow v_c(t) = 30 + Ae^{-t}$$

$$v_c(0) = 30 + A = 6 \Rightarrow A = -24$$

$$\Rightarrow v_c(t) = 30 - 24e^{-t} \text{ volts} \quad t \geq 0$$

Problem 4 (25 points)

Assume the switch has been open from $t = -\infty$ and closes at $t = 0$. Determine $v_c(t)$ for $t \geq 0$.

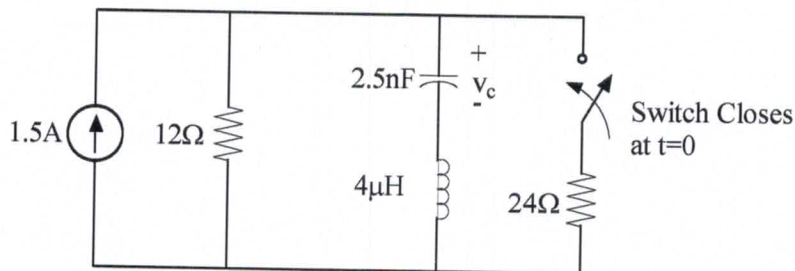



Figure 4: Circuit for Problem 4.

Write your answer here:

$$v_c(t) = \frac{12 + \left[6 \cos \omega_d t + \frac{3}{\sqrt{11}} \sin \omega_d t \right] e^{-\alpha t}}{\quad} \quad (\text{for } t \geq 0)$$

where $\omega_d = 3 \times \sqrt{11} \times 10^6 \text{ rad/sec}$, $\alpha = 10^6 \text{ s}^{-1}$, $\frac{3}{\sqrt{11}} \approx 0.603$
 $\approx 9.95 \times 10^6$

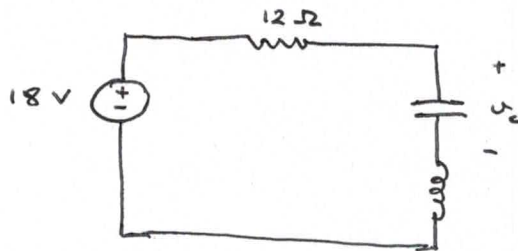For $t < 0$, source transformation gives:




Initial conditions:


$$v_c(0) = 18 \text{ V}$$

$$i_L(0) = i_c(0) = 0 \text{ A}$$

For $t \geq 0$

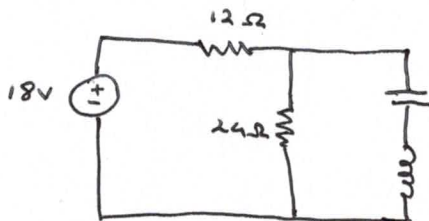

Source transformations
 \Rightarrow

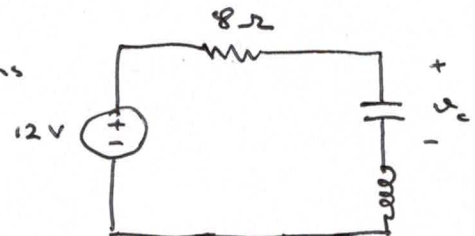

Series RLC circuit

Problem 4 (continued)

$$\alpha = \frac{R}{2L} = \frac{8}{2 \times 4\mu} = 1 \times 10^6$$

$$\omega_0 = \left(\frac{1}{LC}\right)^{\frac{1}{2}} = \left(\frac{1}{4 \times 10^{-6} \times 2.5 \times 10^{-9}}\right)^{\frac{1}{2}} = 1 \times 10^7$$

$\alpha < \omega_0 \Rightarrow$ underdamped

$$\omega_d = (\omega_0^2 - \alpha^2)^{\frac{1}{2}} = (99 \times 10^{12})^{\frac{1}{2}} = 9.95 \times 10^6 \quad (= 3 \times \sqrt{11} \times 10^6)$$

From the series RLC circuit,

$$v_{cR} = 12 \text{ V}$$

$$v_{cn}(t) = [B_1 \cos \omega_d t + B_2 \sin \omega_d t] e^{-\alpha t}$$

$$v_c(t) = v_{cR} + v_{cn}(t)$$

$$v_c(0) = 18 = 12 + B_1 \Rightarrow B_1 = 6$$

$$i_c(0) = C \left. \frac{dv_c}{dt} \right|_{t=0} = C [-\alpha B_1 + \omega_d B_2] = 0$$

$$\Rightarrow B_2 = \frac{\alpha}{\omega_d} B_1 = \frac{10^6}{3 \times \sqrt{11} \times 10^6} \times 6 = \frac{2}{\sqrt{11}} = 0.603$$

$$\Rightarrow v_c(t) = 12 + \left[6 \cos \omega_d t + \frac{2}{\sqrt{11}} \sin \omega_d t \right] e^{-\alpha t}$$

Problem 5 (25 points)

Assume the switch has been closed from $t = -\infty$ and opens at $t = 0$.

1. Determine the differential equation describing $v_1(t)$ for $t \geq 0$. Do not solve. Express the differential equation in standard form (with the coefficient of the highest derivative equal to 1.)
2. Determine the initial values $v_1(0^+)$ and $\frac{dv_1}{dt}|_{t=0^+}$.
3. Determine the steady-state value $v_1(t)$ as $t \rightarrow \infty$.

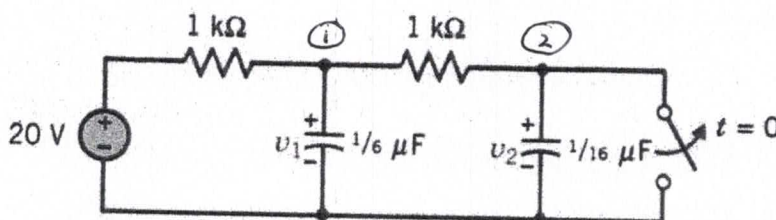


Figure 5: Circuit for Problem 5.

Write your answers here:

D.e. for $v_1(t)$: $\frac{d^2 v_1}{dt^2} + 2.8 \times 10^{-4} \frac{dv_1}{dt} + 9.6 \times 10^7 v_1 = 1.92 \times 10^7, t \geq 0$

$v_1(0^+) = 10$ volts

$\frac{dv_1}{dt}|_{t=0^+} = 0$ volts/sec

$v_1(t)|_{t \rightarrow \infty} = 20$ volts

For $t > 0$,

$$\text{KCL at node 1 gives: } \frac{v_1 - 20}{1000} + \frac{1}{6} \times 10^{-6} \frac{dv_1}{dt} + \frac{v_1 - v_2}{1000} = 0$$

$$\Rightarrow 2v_1 + \frac{1}{6} \times 10^{-3} \frac{dv_1}{dt} - 20 = v_2 \quad (1)$$

$$\text{At node 2: } \frac{v_1 - v_2}{1000} = \frac{1}{16} \times 10^{-6} \frac{dv_2}{dt}$$

$$\Rightarrow v_1 - v_2 - \frac{1}{16} \times 10^{-3} \frac{dv_2}{dt} = 0 \quad (2)$$

Problem 5 (continued)

Substitute (1) into (2):

$$v_1 - \left(2v_1 + \frac{1}{6} \times 10^{-3} \frac{dv_1}{dt} - 20 \right) - \frac{1}{16} \times 10^{-3} \left(2 \frac{dv_1}{dt} + \frac{1}{6} \times 10^{-3} \frac{d^2v_1}{dt^2} \right) = 0$$

$$\Rightarrow -\frac{1}{16} \times 10^{-3} \times \frac{1}{6} \times 10^{-3} \frac{d^2v_1}{dt^2} + \left(-\frac{1}{6} \times 10^{-3} - \frac{1}{8} \times 10^{-3} \right) \frac{dv_1}{dt} - v_1 + 20 = 0$$

$$\Rightarrow 1.0417 \times 10^{-8} \frac{d^2v_1}{dt^2} + 0.2917 \times 10^{-3} \frac{dv_1}{dt} + v_1 = 20$$

$$\Rightarrow \frac{d^2v_1}{dt^2} + 2.8 \times 10^4 \frac{dv_1}{dt} + 9.6 \times 10^7 v_1 = 1.92 \times 10^9$$

Directly from the circuit, as $t \rightarrow \infty$, $v_1 = 20$ Volts,

For $t < 0$, when the switch is closed, $v_2(0^-) = 0$

$$v_1(0^-) = \frac{1k}{1k+1k} \times 20 = 10 \text{ Volts}$$

$$= v_1(0^+)$$

At time $t = 0^+$, immediately after the switch opens, (1) is valid, so

$$2v_1(0^+) + \frac{1}{6} \times 10^{-3} \frac{dv_1}{dt} \Big|_{t=0^+} - 20 = v_2(0^+) = v_2(0^-) = 0$$

$$\Rightarrow \frac{dv_1}{dt} \Big|_{t=0^+} = 20 - 2 \times 10 = 0$$