


HW #4

SOLUTIONS

Problems :

- * 4.7
- * 4.16
- * 4.27
- * 4.48
- * 4.57
- * 4.72
- * 4.88

4.7

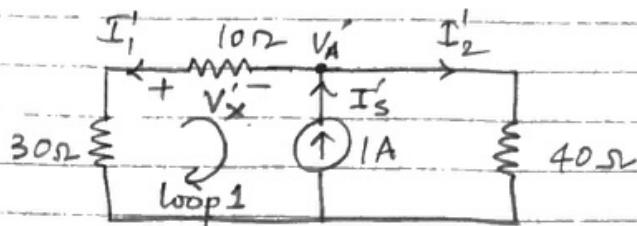

* Initial assumption: $V_x' = 1V$

Current through 10 ohm resistor:

$$I_1' = -\frac{1V}{10\Omega} = -0.1A$$

Applying KVL in loop 1:

$$\begin{aligned} \textcircled{Y_2} \quad & -30I_1' - 10I_1' + V_A' = 0 \\ & \therefore V_A = 40I_1' = 40(-0.1) \\ & \qquad \qquad \qquad = -4V \end{aligned}$$

Applying KCL at node A (V_A):

$$\begin{aligned} \textcircled{Y_2} \quad & I_1' + \frac{V_A}{40} = I_s' \\ & \Rightarrow I_s' = -0.2A \end{aligned}$$


But, actual value of $I_s = 1A$
 $= -5 \times I_s'$

\therefore Multiplication factor = -5

$$\therefore I_1 = 5 \times I_1' \\ = -0.5A$$


$$\therefore V_x = -5 \times V_x' = -5 \times (-I_1 \times 10) \\ = \underline{\underline{5V}}$$

4.16

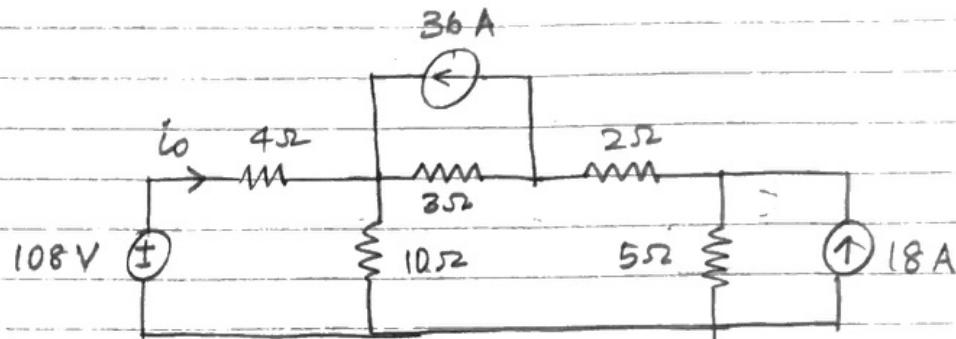

$$i_0 = i_{01} + i_{02} + i_{03} \quad (1)$$

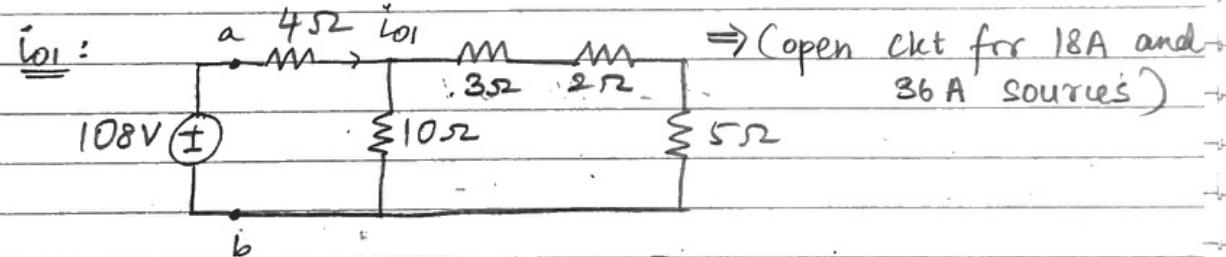↓ ↓ ↓
 (from 108V source) (from 36A source) (from 18A source)




$$R_{ab} = 4 + [10 \parallel (3+2+5)]$$

$$= 4 + 5 = 9\Omega$$

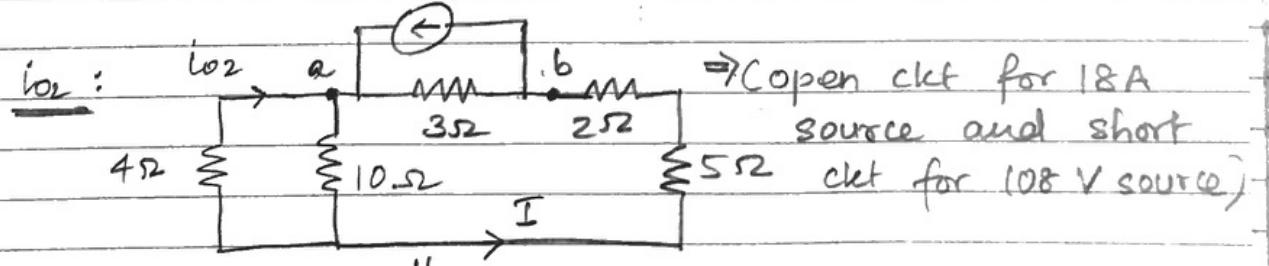
(1)

$$\therefore i_{01} = \frac{108}{9} = 12A \quad (2)$$



$$R_{ab} = ((4 \parallel 10) + 2+5)\Omega$$


$$= \frac{69}{7} \Omega$$

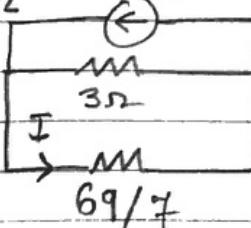

$$\Rightarrow I = \left(\frac{8}{\frac{69}{7} + 3} \right) \times 36 = 8.4 A$$

①
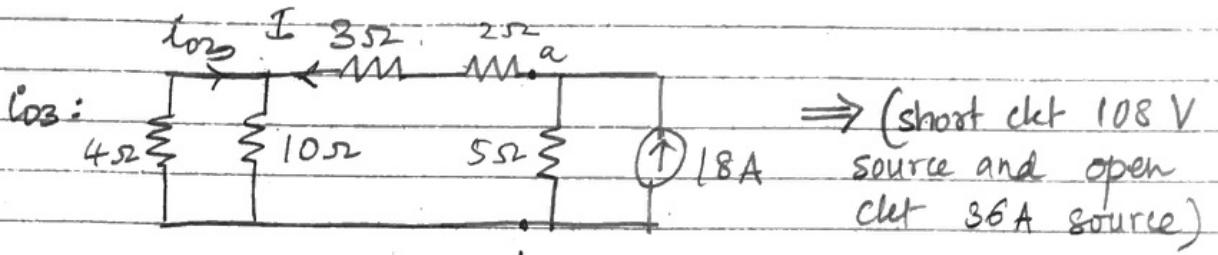
$$i_{02} = \frac{-10}{14} (I) = -6A \quad - \textcircled{3}$$



\Rightarrow (short ckt 108 V
source and open
ckt 36A source)

$$R_{ab} = (4||10) + 5 = \frac{55}{7} \Omega$$

$$I = \frac{5}{5+\frac{55}{7}} \times 18 = 7A$$

①


$$i_{03} = -\frac{10}{14} \times 7 = -5A \quad - \textcircled{4}$$

From ①, ②, ③ and ④


②

$$i_0 = 12 - 6 - 5 = \underline{\underline{1A}}$$


4.27

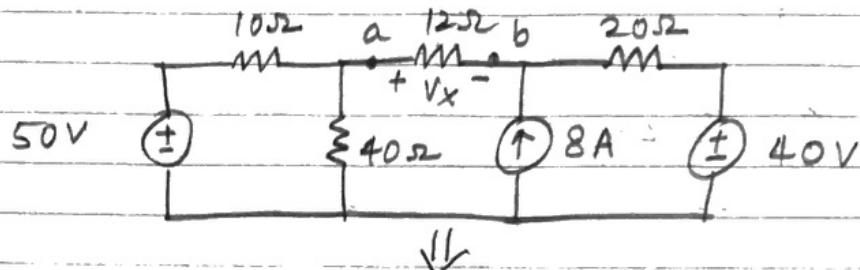

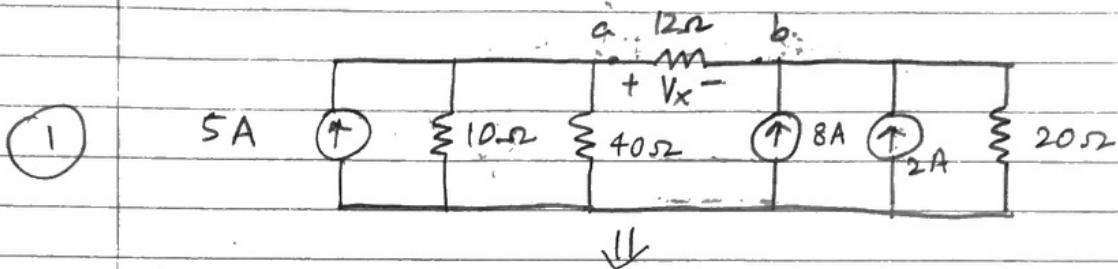Applying source transformation to 50V & 40V sources:



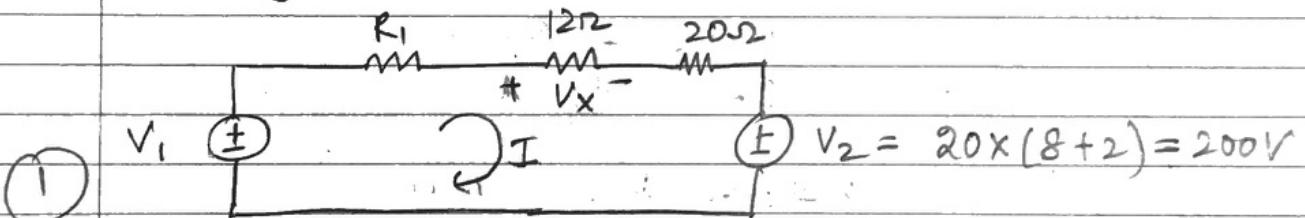Applying current-to-volt source transformation:



$$V_1 = 5 \times (10 \parallel 40) = 40V$$

$$R_1 = 10 \parallel 40 = 8 \Omega$$

Applying KVL around the loop:


$$-V_1 + R_1 I + 12I + 20I + 200 = 0$$

$$\Rightarrow -40 + 8I + 32I + 200 = 0$$


$$\Rightarrow I = -4 A$$

$$\text{Now, } V_x = 12I = -48 V$$

4.48

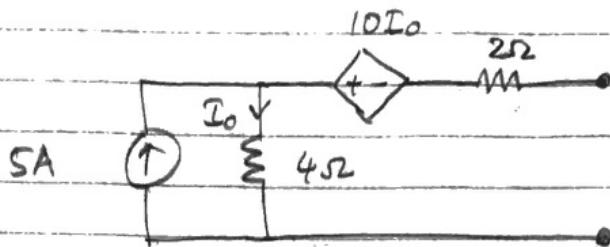

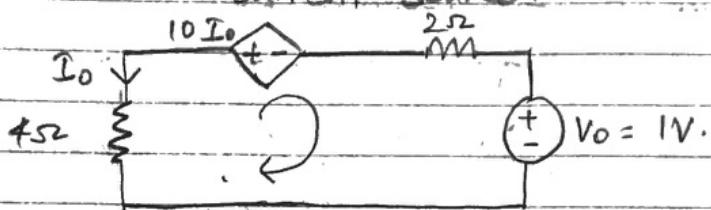Step I : Find R_N : Open ckt for independent current source




Applying KVL around the loop :

$$-4I_0 + 10I_0 - 2I_0 + 1V = 0 \\ \Rightarrow I_0 = \frac{1}{4} A$$

$$\therefore R_N = \frac{V_o}{I_0} = 4 \Omega$$

Step II : Solve for V_{oc}

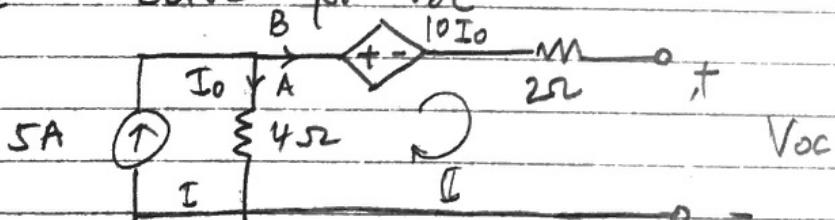

" loop II is open circuit, no current flows through branch B.

$$\therefore I_0 = 5A$$

Applying KVL around loop II :


$$\textcircled{1} \quad -4I_0 + 10I_0 = V_{oc}$$

$$\Rightarrow V_{oc} = \underline{\underline{30V}}$$


Step III : Find I_N :

$$\textcircled{2} \quad I_N = \frac{V_{oc}}{R_N} = \frac{30}{4} = \underline{\underline{7.5A}}$$


\therefore Norton equivalent ckt :

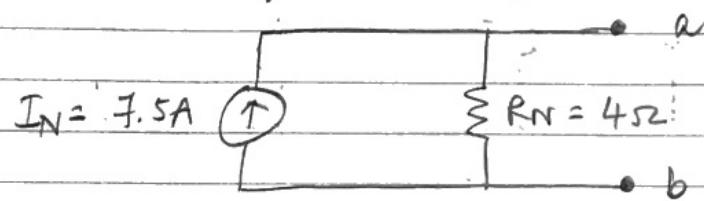

4.57

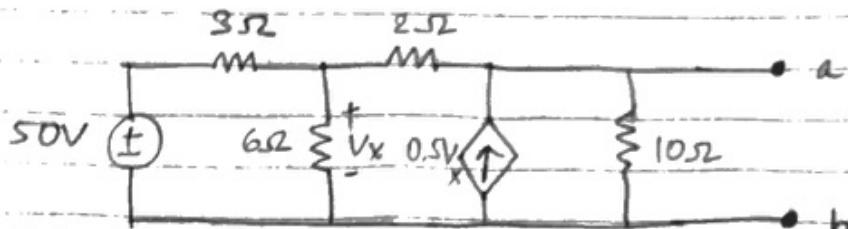

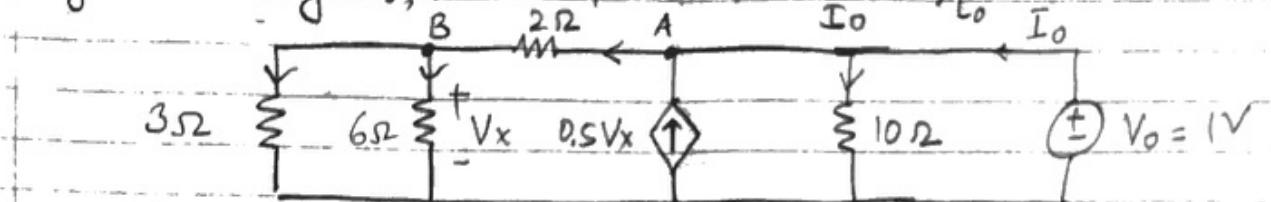Step I: Find R_N or R_{Th} : Since there is a dependent current source, we apply a V_{Th} source, $V_0 = 1V$, between a & b.
 \therefore By calculating I_0 , we can find $R_{Th} = \frac{V_0}{I_0} = \frac{1V}{I_0}$



Note, $V_x = V_B$ and $V_A = 1V$
 Applying KCL at node A:

$$\begin{aligned}
 \textcircled{1}_2: \quad & \frac{1-V_B}{2} + \frac{1}{10} = I_0 + 0.5V_B \\
 \Rightarrow \quad & 5 - 5V_B + 1 = 10I_0 + 5V_B \\
 \Rightarrow \quad & 6 - 10I_0 = 10V_B \\
 \Rightarrow \quad & 6 = 10V_B + 10I_0 \quad - \textcircled{1}
 \end{aligned}$$

Applying KCL at node B:


$$\begin{aligned}
 \textcircled{2}: \quad & \frac{V_B}{6} + \frac{V_B}{3} = \frac{1-V_B}{2} \\
 \Rightarrow \quad & V_B + 2V_B = 3 - 3V_B \\
 \Rightarrow \quad & V_B = 0.5V \quad - \textcircled{2}
 \end{aligned}$$

\therefore From $\textcircled{1}$ & $\textcircled{2}$

$$I_0 = 0.1A$$

$$\textcircled{3}: \quad R_N = R_{Th} = \frac{1}{0.1} = 10\Omega$$

Step II : Find V_{Th}

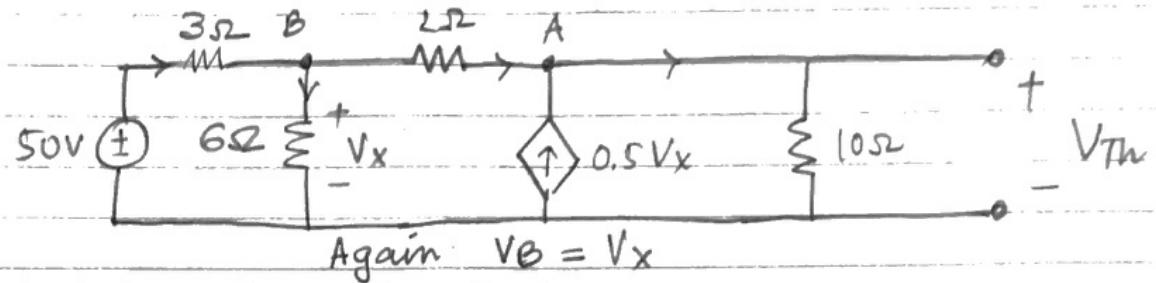

Applying KCL at node A :

$$\textcircled{1} \quad \frac{V_B - V_A}{2} + 0.5 V_B = \frac{V_A}{10}$$

$$\Rightarrow 5V_B + 5V_B - 5V_A - V_A = 0$$

$$\Rightarrow 10V_B - 6V_A = 0 \quad - \textcircled{3}$$

Applying KCL at node B :

$$\textcircled{2} \quad \frac{50 - V_B}{3} = \frac{V_B}{6} + \frac{V_B - V_A}{2}$$

$$100 - 2V_B = V_B + 3V_B - 3V_A$$

$$\Rightarrow 6V_B - 3V_A = 100 \quad - \textcircled{4}$$

Solving $\textcircled{3}$ & $\textcircled{4}$:


$$\textcircled{1} \quad V_A = V_{Th} = 166.67 \text{ V}$$

Step III : Find I_N


$$\textcircled{2} \quad I_N = \frac{V_{Th}}{R_{Th}} = 16.67 \text{ A}$$

Resulting equivalent cts:


* Thevenin equivalent:

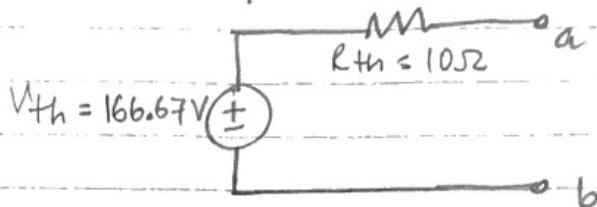


* Norton equivalent:

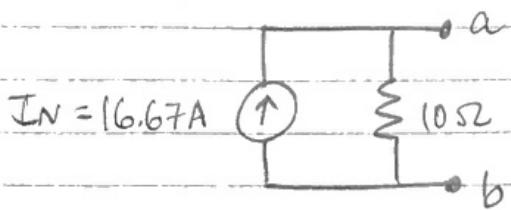

4.72

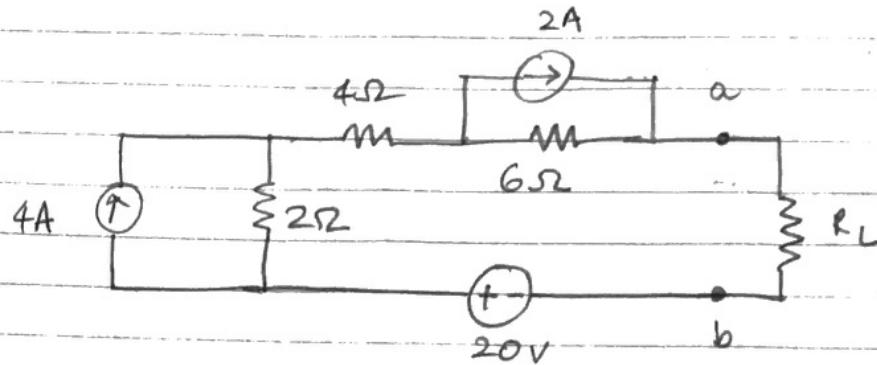


(a) Thevenin Equivalent:

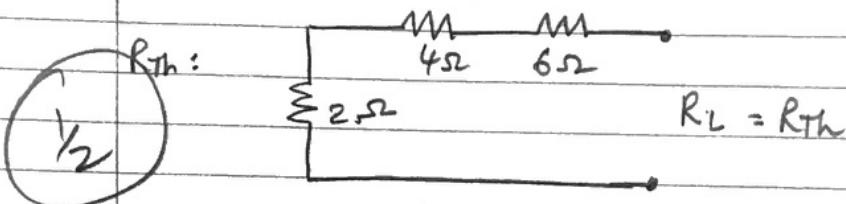

$$R_{th} = 12\Omega$$

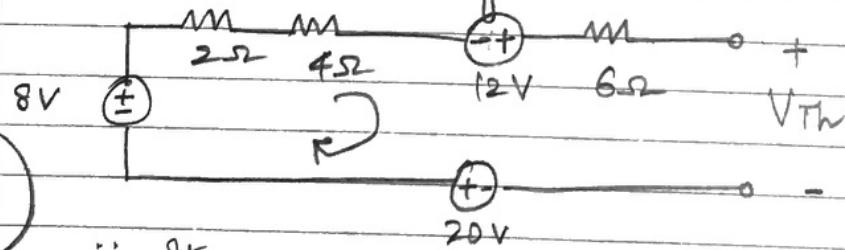
V_{th} : Applying current to voltage source transformation:



\therefore Since it's an open circuit, current = 0
Applying KVL in the loop:

$$\begin{aligned} -8 - 12 + V_{th} - 20 &= 0 \\ \Rightarrow V_{th} &= 40V \end{aligned}$$

Equivalent circuit:

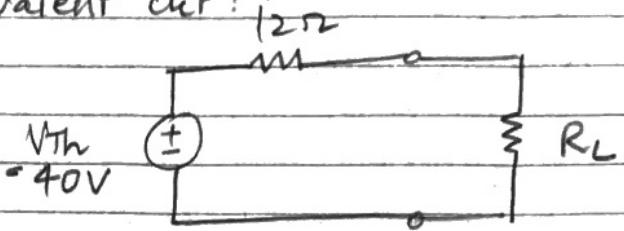

(b) \therefore if $R_L = 13$

$$i = \frac{V_{Th}}{R_{Th} + 13} = \frac{40}{25} = 1.6A$$


(c) For maximum power transfer:

$$R_L = R_{Th} = 12\ \Omega$$


(d)

$$P_{max} = \frac{V_{Th}^2}{4R_{Th}} = 33.33\ W$$

4.88

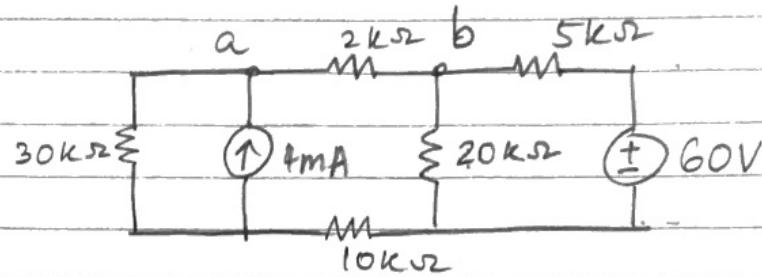


R_{Th} :

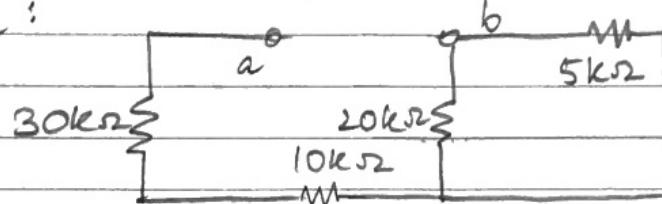

(1)

$$R_{Th} = [(20 \parallel 5) + 40] \\ = 44 \text{ k}\Omega$$

V_{Th} :

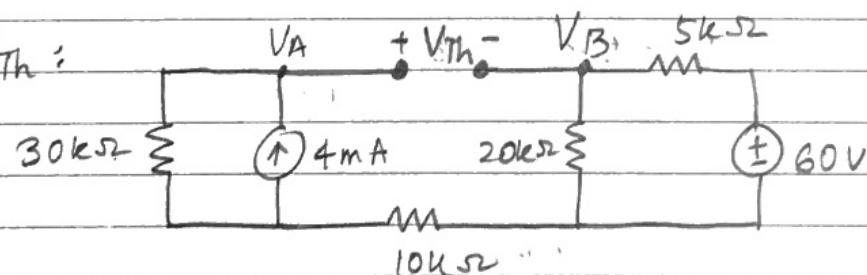

** Since there is an open ckt, no current to/from the left circuit flows from/to the right ckt.


$$\therefore V_A = 4 \times 30 = 120 \text{ V}$$

$$V_B = \frac{20}{25} \times 60 = 48 \text{ V}$$


(1)

$$\therefore V_{Th} = 72 \text{ V}$$

\therefore Eq ckt:

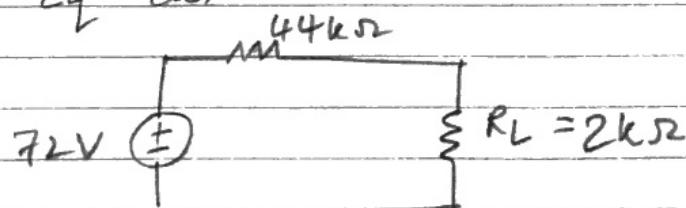

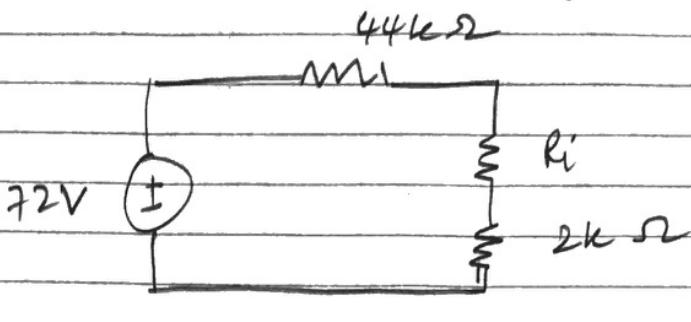Now if we insert ammeter in series with R_L , we get:



Here we substitute ammeter by its internal resistance R_i .

$$\therefore I = \frac{72}{46 + R_i}$$

(a) When $R_i = 500\Omega = 0.5\text{k}\Omega$

$$I = \frac{72}{46.5} = 1.548 \text{ mA}$$

(b) When $R_i = 0\Omega$

$$I = \frac{72}{46} = 1.565 \text{ mA}$$