

HW #10

* 10.8


* 10.38

* 10.48

* 10.52

* 10.56

* 10.62

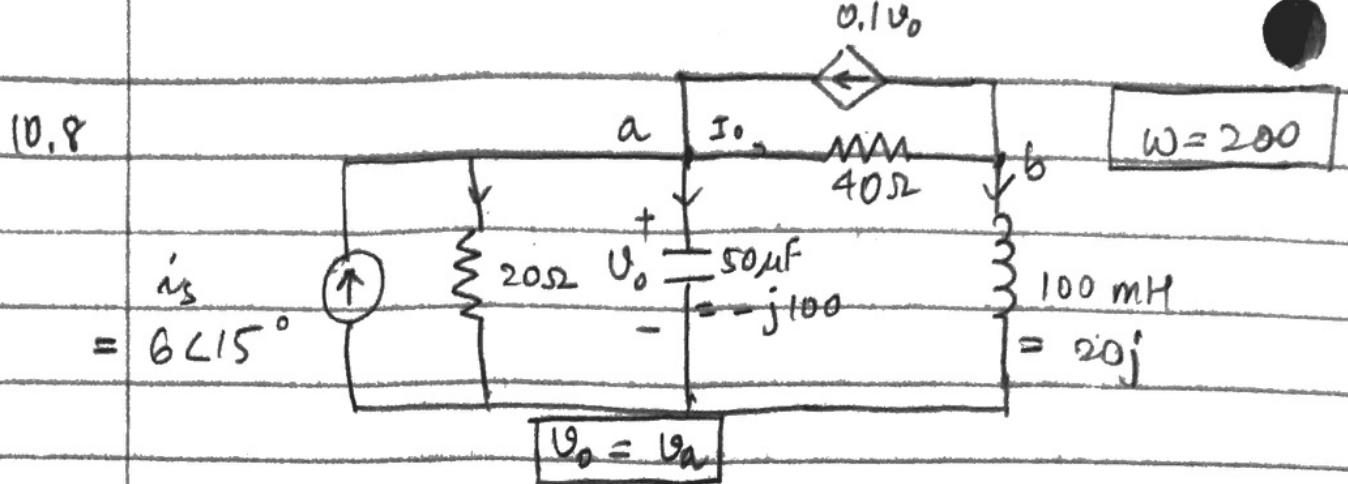

at Node a:

$$6 \angle 15^\circ + 0.1 V_a = \frac{V_a}{20} + \frac{V_a}{-100j} + \frac{V_a - V_b}{40}$$

(Y₂) or $5.8 + 1.55j = (-0.025 + 0.01j)V_a - 0.025V_b$ - (1)

at node b:

$$\frac{V_a - V_b}{40} = \frac{V_b}{20j} + 0.1 V_a$$

(Y₂) or $3V_a + (1-2j)V_b = 0$ - (2)

Solving eqⁿ: (1) + (2) :

$$V_a = -2.45 + 145.5j \text{ V}$$


$$V_b = -176.07 + 84.36j \text{ V}$$

$$\therefore I_o = \frac{V_a - V_b}{40}$$

$$= 7.27 \angle -52.129 \text{ A}$$

$$= 7.27 \cos(200t - 52.129) \text{ A}$$

10.38

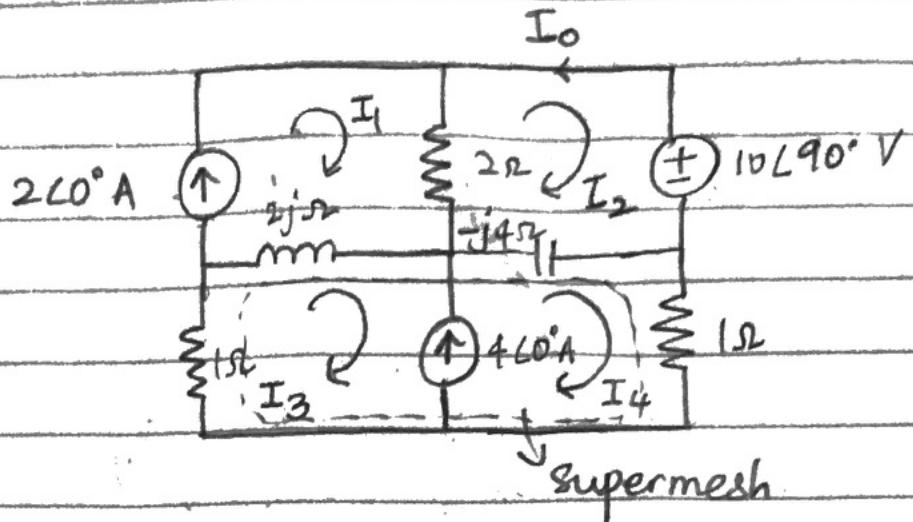

First, $I_1 = 2A$

For Mesh 2:

$$\begin{aligned} 2(I_2 - 2A) + 10\angle 90^\circ + (-4j)(I_2 - I_4) &= 0 \\ \Rightarrow 2(1 - 2j)I_2 + (4j)I_4 &= 4 - 10j \\ \Rightarrow (1 - 2j)I_2 + (2j)I_4 &= 2 - 5j \quad - \textcircled{1} \end{aligned}$$

For Supermesh:

$$(1+2j)I_3 - 2(2j) + (1-4j)I_4 + (4j)I_2 = 0$$

$$\textcircled{2} \Rightarrow (1+2j)I_3 + (1-4j)I_4 + (4j)I_2 = 4j \quad - \textcircled{2}$$

Constraint eqⁿ:

$$I_4 - I_3 = 4 \quad - \textcircled{3}$$

Substitute $\textcircled{3}$ in $\textcircled{2}$:

$$\begin{aligned} (2 - 2j)I_4 + (4j)I_2 &= 4j + 4 + 8j \quad - \textcircled{1} \\ (1 - j)I_4 + (2j)I_2 &= 2 + 6j \quad - \textcircled{4} \end{aligned}$$

Solving ① & ④ :


$$\textcircled{1} \quad I_2 = 3.33 - 0.33j \text{ A}$$

$$\therefore I_0 = -I_2$$


$$\therefore I_0 = (-3.33 + 0.33j) \text{ A}$$

$$\textcircled{2} \quad = 3.34 \angle 174.34^\circ \text{ A}$$

10.48

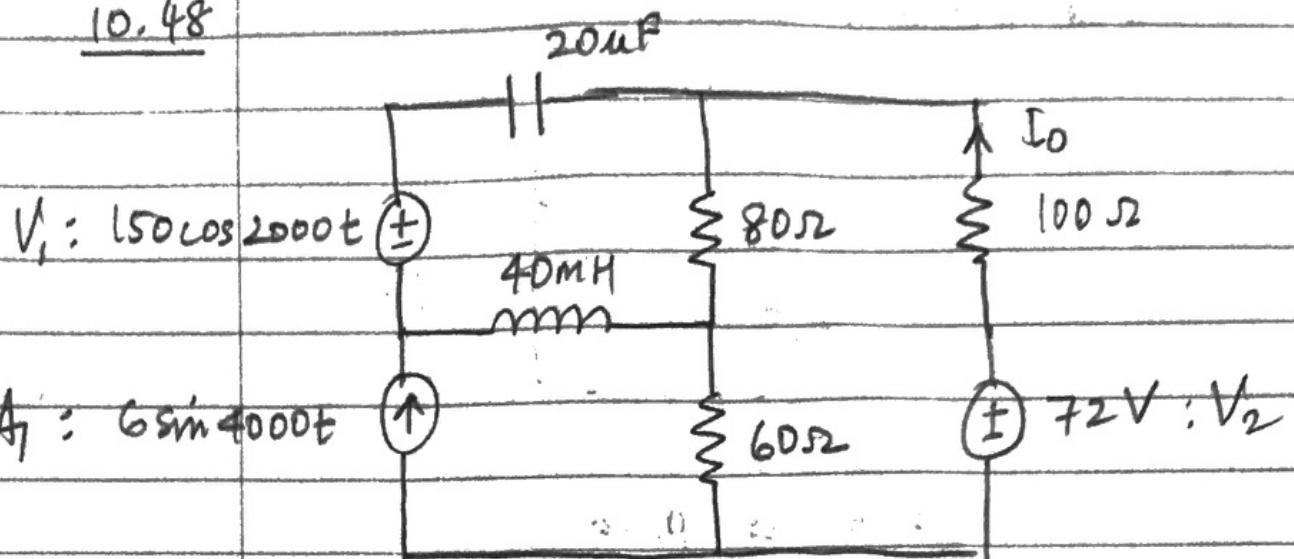


From voltage source V₁:

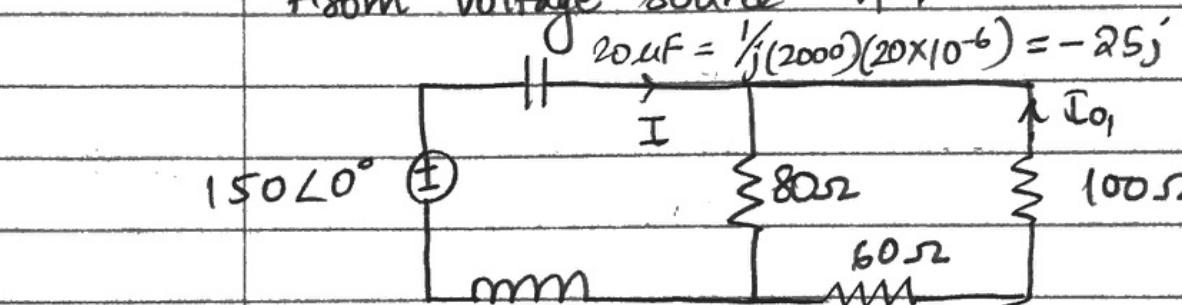

$$40 mH = j(2000)(40 \times 10^{-3}) \\ = 80j$$


$$\begin{aligned}
 \textcircled{1} \quad I_0 &= \frac{-80}{(80+160)} \quad I = -\frac{1}{3}(150) \left(\frac{1}{(80||160) + 55j} \right) \\
 &= -\frac{1}{3} \left(\frac{90}{32+33j} \right) \\
 &= -\frac{30}{32+33j} \\
 &= 0.652 \angle 134.118^\circ A
 \end{aligned}$$

For voltage source V_0 :

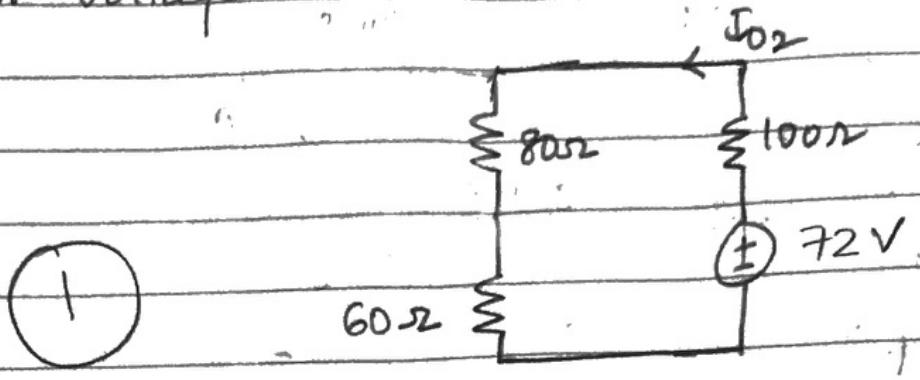

$$\therefore I_{02} = \frac{72V}{240\Omega} = 0.3A$$

For current source I_1 :

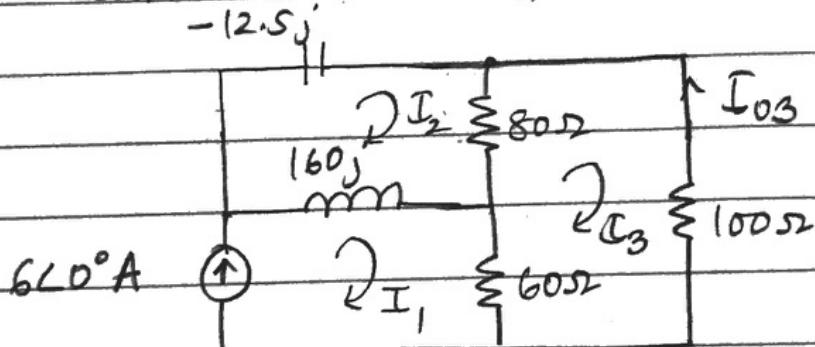

$$\text{First } I_1 = 6∠0^\circ A$$

Mesh 2:

$$(1) (80 + 147.5j) I_2 - 80 I_3 = (160j) 6 = 960j$$

- (1)

Mesh 3:

$$(2) 6240 I_3 - 80 I_2 = 360$$

$$6 I_3 - 2 I_2 = 9$$

- (2)

Solving ① and ② :


$$I_3 = 3.5 + 0.45j \text{ A}$$
$$= 3.52 \angle 7.38^\circ$$

①

$$\therefore I_{03} = -I_3 = 3.52 \angle -172.67^\circ \text{ A}$$

②

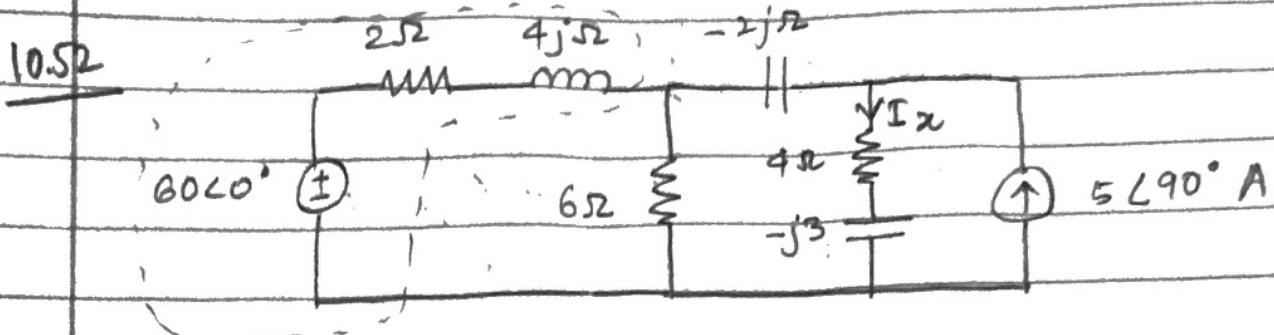
$$\therefore I_0 = I_{01} + I_{02} + I_{03}$$
$$= \{ 0.3 + 0.652 \cos(2000t + 134.118) \\ + 3.52 \sin(4000t - 172.67) \} \text{ A}$$



Source Transformation :

$$I_s = \frac{60}{2+4j} = 6 - 12j \text{ A}$$


equivalent ckt :

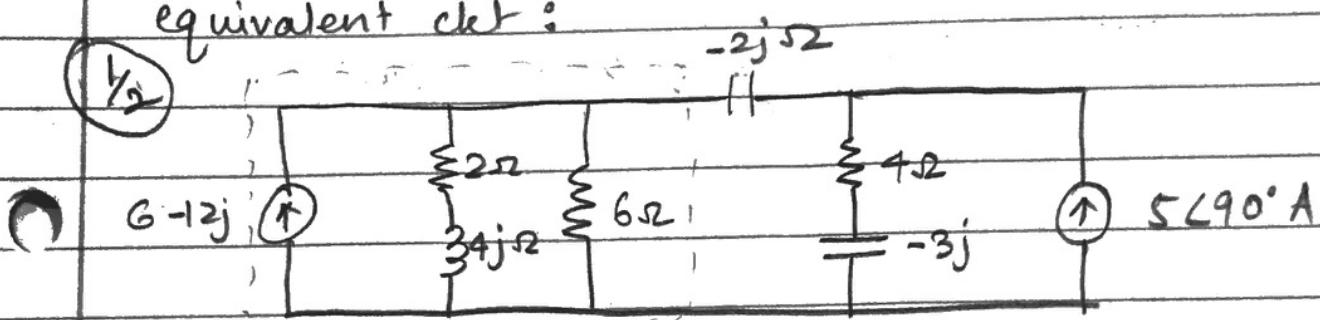

$$\left(\frac{1}{2}\right) Z_s = 6 \parallel (2+4j) = 2.4 + 1.8j$$

$$\left(\frac{1}{2}\right) V_s = (6-12j)(2.4+1.8j) = 18(2-j) \text{ V}$$


equivalent ckt :

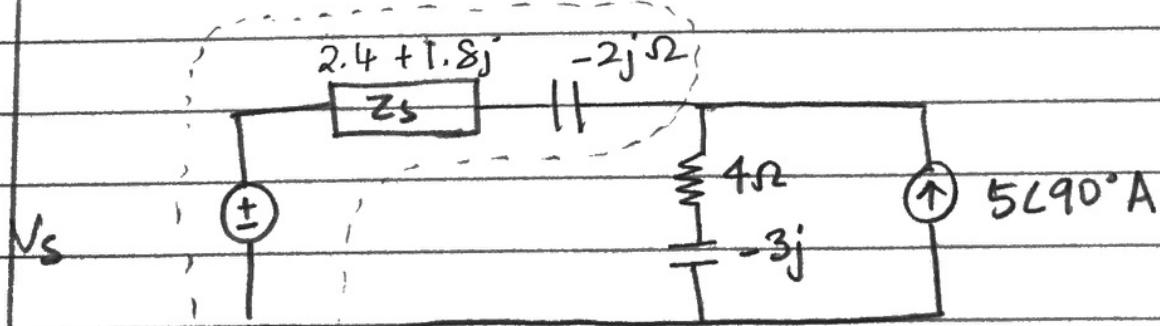

$$\left(\frac{1}{2}\right) Z_0 = 2.4 - 0.2j$$

$$\therefore I_0 = \frac{V_s}{Z_0} = \frac{18(2-j)}{(2.4-0.2j)} = 15.52 - 6.21j \text{ A}$$


equivalent circuit:

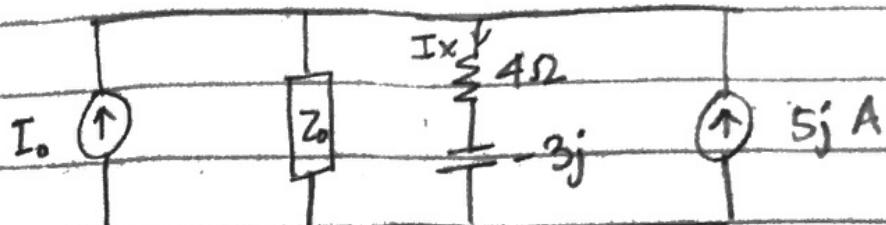

$$\begin{aligned} \textcircled{Y_2} \quad & I_x = \frac{Z_0}{Z_0 + 4 - 3j} (I_0 + 5j) \\ &= \frac{2.4 - 0.2j}{6.4 - 3.2j} (15.517 - 1.207j) \\ &= 4.99 + 1.562j \text{ A} \\ &= 5.23 \angle 17.38^\circ \text{ A} \end{aligned}$$

10.58

Approach I :

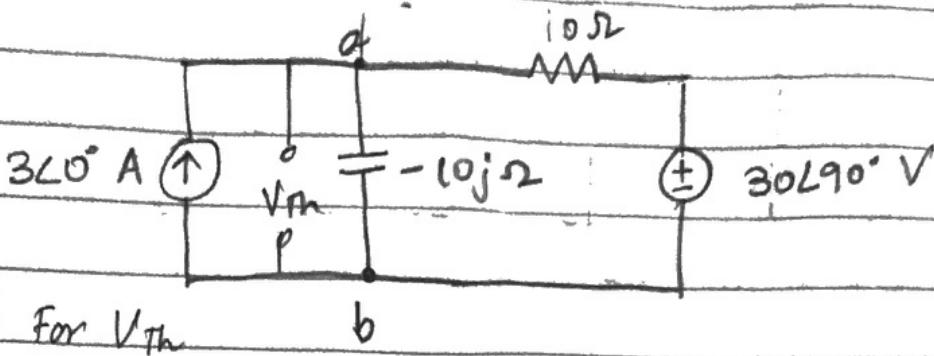

At node a :


$$3 = \frac{V_a - j30}{10} + \frac{V_a}{-10j} \quad (1)$$

$$\begin{aligned} 30 &= V_a - 30j + V_{aj} \\ \Rightarrow 30 + 30j &= V_a(1 + j) \\ \Rightarrow 30(1 + j) &= V_a(1 + j) \end{aligned}$$


$$\therefore V_a = 30V$$

$$\therefore V_{Th} = V_{ab} = \underline{30V}$$

Z_{Th} : equivalent ckt :

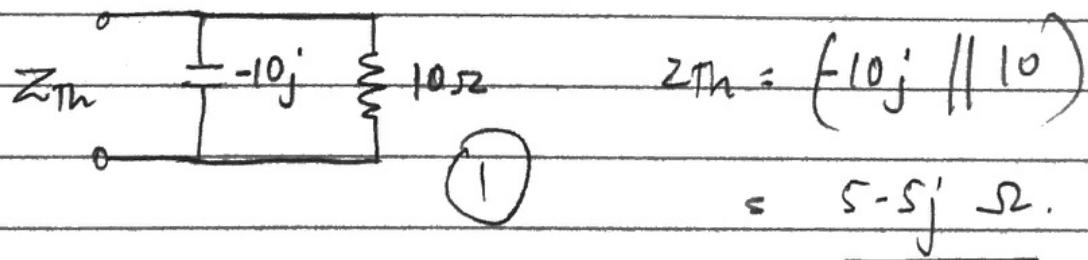


\therefore Thevenin equivalent :

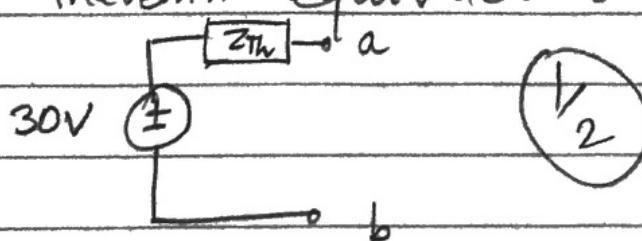

Approach I:

V_{Th} :

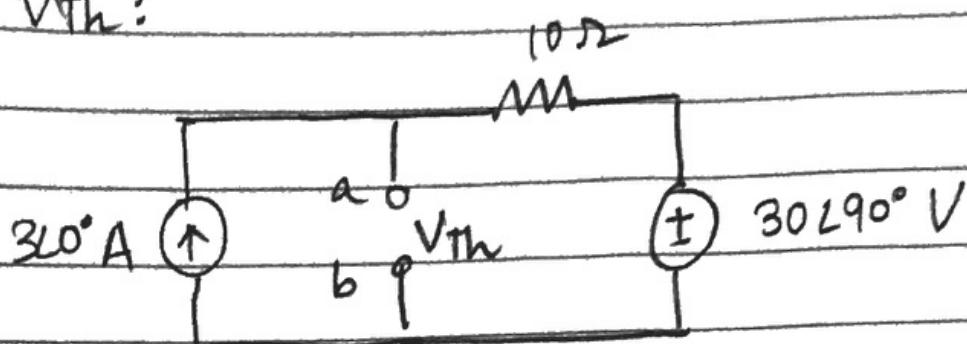


$$Z = \frac{V_{Th} - 30j}{10\Omega}$$

①


$$\therefore V_{Th} = 30(1+j) V$$


Z_{Th} :

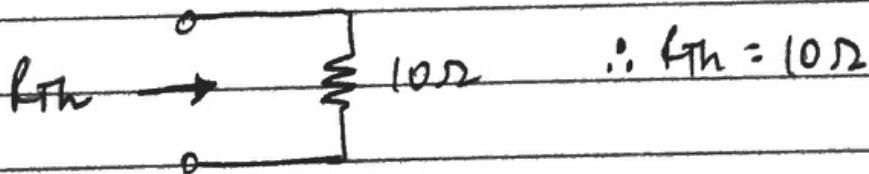

①

Equivalent ckt:

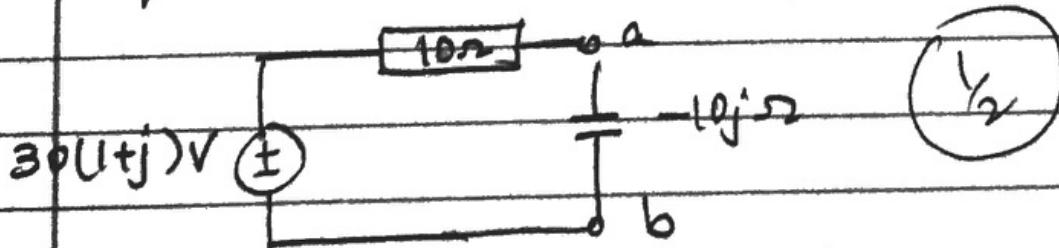

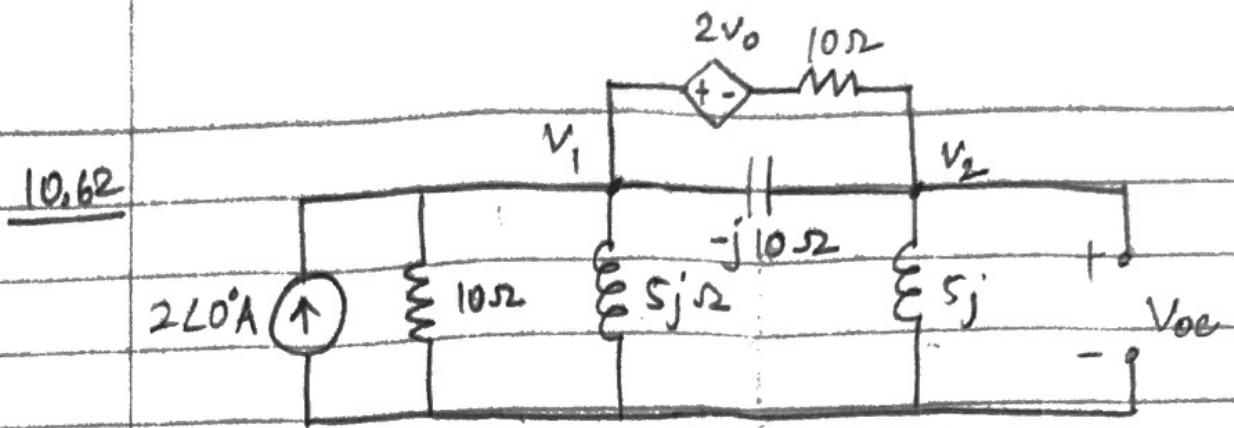

First : $V_0 = V_2$

At node 1 :

$$2 = \frac{V_1}{10} + \frac{V_1}{5j} + \frac{V_1 - V_2}{-j10} + \frac{V_1 - 2V_2 - V_2}{10}$$

$$= 0$$

$$\Rightarrow 20 = V_1 - 2V_1 j + (V_1 - V_2)j + V_1 - 3V_2$$

$$= 2V_1 - 3V_2 - (V_1 + V_2)j$$

$$= (2 - 1j)V_1 - (3 + 1j)V_2 \quad - \textcircled{1}$$

At node 2 :

$$\frac{V_2 - V_1}{(-10j)} + \frac{V_2 + 2V_2 - V_1}{10\Omega} + \frac{V_2}{5j} = 0$$

$$\Rightarrow (0.1j)(V_2 - V_1) + 0.1(3V_2 - V_1) - 0.2jV_2 = 0$$

$$(-0.1)(1+j)V_1 + (0.3 - 0.1j)V_2 = 0$$


$$- \textcircled{2}$$

Solving $\textcircled{1} \ \& \ \textcircled{2}$:

$$\textcircled{1} \quad V_2 = 2.98 \text{ or } 116.56V$$

$$= V_{Th}$$

Inc.

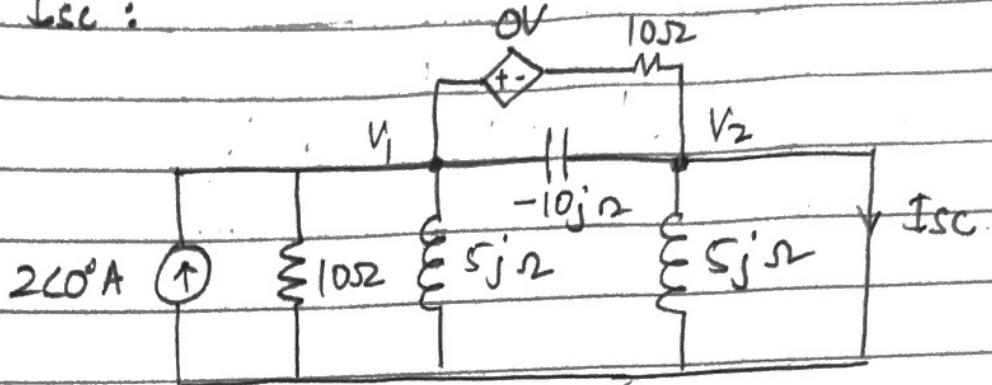

$$\therefore \underline{V_2 = 0}.$$

\therefore Substituting $V_2 = 0$ in ①

$$V_1 = 8 + 4j \text{ V} \quad (x_2)$$

At node 2:

$$\frac{V_2 - V_1}{-(10j)} + \frac{V_2 - V_1}{10} + I_{SC} = 0 \quad b_2$$

$$\begin{aligned}
 I_{SC} &= \frac{-V_1}{10j} + \frac{V_1}{10} \\
 &= -0.4 + 0.8j + 0.8 + 0.4j \\
 &= 0.4 + 1.2j \\
 &= 1.26 \angle 71.56^\circ \quad (1)
 \end{aligned}$$

$$\therefore Z_{Th} = \frac{V_{Th}}{I_{SL}}$$

$$= 2,357 \angle 45^\circ \Omega$$

